

Microsoft PowerPoint® Presentation Graphics for
EE 313: Basic Electrical Engineering I

Prepared by Brian Manhire, Ph.D.
 Professor of Electrical Engineering



*Stocker Center, home of Ohio University's
 Russ College of Engineering & Technology*

Microsoft PowerPoint® Presentation Graphics
 © Copyright 1998 Brian Manhire

For Part 1 of

**Introduction to Electrical
 Engineering, 2/e**

by **C.R. Paul, S.A. Nasar
 and L.E. Unnewehr**

© 1992, McGraw-Hill, Inc.

Chapter 2
Circuit Elements and Laws



Introduction to Electrical Engineering

Chapter 2: Circuit Elements and Laws

Introduction

- 2.1 Charge and Electric Forces
- 2.2 Voltage
- 2.3 Current and Magnetic Forces
- 2.4 Lumped-Circuit Elements
- 2.5 Kirchhoff's Voltage and Current Laws
- 2.6 The Resistor
- 2.7 Voltage and Current Sources
- 2.8 Signal Waveforms
- 2.9 Analysis of Simple Circuits

Chapter 2: Introduction (pp. 9-10)

- In electric circuit analysis the most fundamental quantities are voltages and currents
- Voltages and currents are interrelated and in many practical applications ideal (linear) relationships (e.g., $V = R \times I$) suffice
- Useful electromechanical devices have electric circuit counterparts (see next slide = text Figure 2.2)
- The ability to employ electric circuit analysis skills to these counterparts is essential in the analysis and design of electromechanical and electronic devices

Chapter 2: Introduction cont.


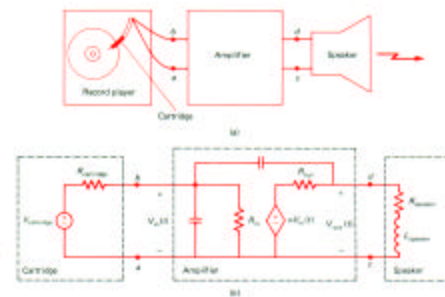


FIGURE 2.2
 Modeling a physical electric circuit using ideal electric circuit elements: (a) actual circuit; (b) circuit ideal model

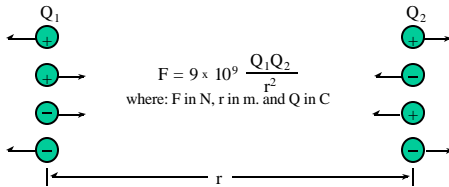2.1 Charge and Electric Forces (pp. 11-13)

- Charge (Q_1 & Q_2) is the “stuff” of electricity
- There are two kinds of charge: positive (+) and negative (-)
- Unlike charges attract, like charges repel




$$F = 9 \times 10^9 \frac{Q_1 Q_2}{r^2}$$

where: F in N, r in m, and Q in C

See Example 2.1 (pp. 12-13) for application

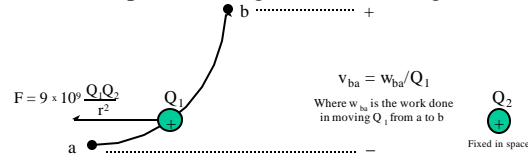2.2 Voltage

- Charges exert forces on one another
- \therefore Moving a charge Q_1 in the presence of another charge Q_2 entails doing work (expending energy) on that charge (Q_1)
- Work per unit charge (1 J/C) is voltage (1 V.)




See Example 2.2 (pp. 15-16 for application)

2.2 Voltage cont.: Example 2-1


Text Problem 2.7 (p. 49)

Calculate the voltage v_{ba}

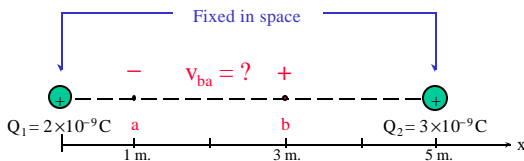

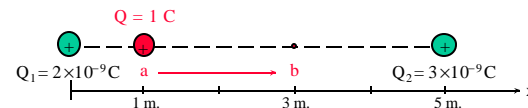2.2 Voltage cont.: Example 2-1 cont.

Solution strategy: Since $v_{ba} = W_{ba}/Q$, where W_{ba} is the work done (energy expended) in moving charge Q from a to b , conceptually move a “test” charge of $Q=1$ C from a to b (then evaluate the v_{ba} voltage paradigm above).




2.2 Voltage cont.: Example 2-1 cont.

The net force *opposing* the movement of Q is

$$F_{\text{net}} = F_2 - F_1 \text{ where:}$$

$$F_2(x) = + 9 \times 10^9 \frac{Q_2 Q}{(5-x)^2}$$

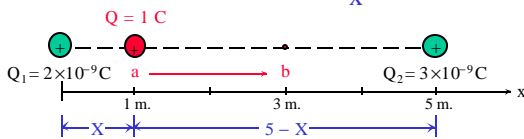
$$F_1(x) = - 9 \times 10^9 \frac{Q_1 Q}{x^2}$$



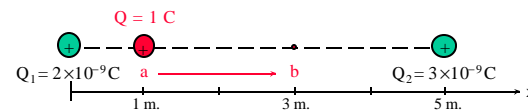2.2 Voltage cont.: Example 2-1 cont.

Which for the given charge values yields:

$$F_{\text{net}}(x) = + \frac{27}{(5-x)^2} - \frac{18}{x^2}$$



2.2 Voltage cont.: Example 2-1 cont.


Then the work done in moving Q is:

$$W_{ba} = \int_a^b F_{\text{net}}(x) dx = \int_1^3 \left[\frac{27}{(5-x)^2} - \frac{18}{x^2} \right] dx$$

Which yields $W_{ba} = -5.25 \text{ J}$

Ergo, $v_{ba} = W_{ba} / Q = -5.25 \text{ J} / 1 \text{ C} = -5.25 \text{ J/C}$
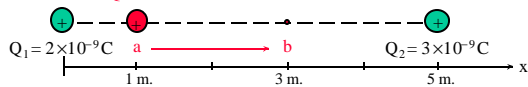
$$Q = 1 \text{ C} \therefore v_{ba} = -5.25 \text{ V.}$$



2.3 Current and Magnetic Forces

- Current is a measure of the rate of flow of (net positive) charge per unit time
- 1 Ampere = 1 Coulomb per second
- See next slide = Figure 2.10 (p. 17) for a graphical illustration of the charge/current relationship


$$i(t) = \frac{dq(t)}{dt} \quad (2.4)$$

$$q(t) = \int_{-\infty}^t i(\tau) d\tau \quad (2.5)$$

Units: $i(t)$ is in Amperes when $q(t)$ is in Coulombs and t is in seconds

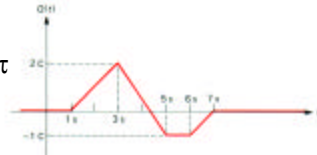2.3 Current and Magnetic Forces cont.

$$q(t) = \int_{-\infty}^t i(\tau) d\tau$$



$$i(t) = \frac{dq(t)}{dt}$$


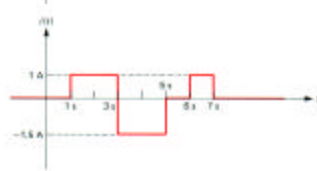


FIGURE 2.10 Relation between current and net positive charge flowing past a point.

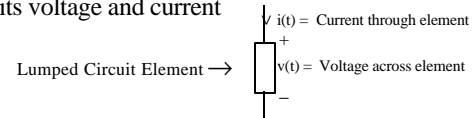
2.4 Lumped-Circuit Elements

- Macroscopic (big picture) treatment of electrophysics
- Physical behavior of a region of electrical activity is averaged (lumped together) into a so-called "lumped-circuit element"
- The overall electrical activity associated with the element is captured, inter alia, by its voltage and current




Voltage-Current Power Relationship

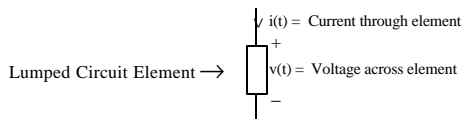- Voltage units are Joules / Coulomb
- Current units are Coulombs / second
- Voltage-Current product's units are ...
- (Joules / Coulomb) \times (Coulombs / second) ...
- = Joules / second = Watts
- Ergo, $P(t) = v(t)i(t)$ (which is Power)




Passive Sign Convention

- Given the passive sign convention shown below ...
- Then if at some time "t" both $i(t) > 0$ and $v(t) > 0$
- Then positive charge is moving through the element from top-to-bottom at the rate $i(t)$ (in C/sec.) and ...
- The rate (per unit charge) of work (energy) being done to push the charge through the element is $v(t)$ (in J/C)
- The power absorbed by the element is $p(t) = v(t)i(t)$ in Watts (1 W = 1 J/s)

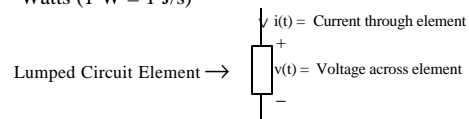


Voltage Polarity Meaning

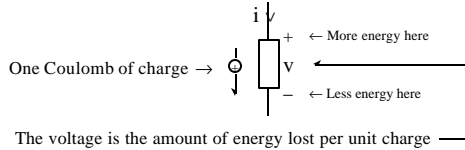- The amount of energy (in Joules) that *each* Coulomb of charge loses (expends), as a result of its journey from top-to-bottom through the element, is numerically equal to its voltage (in Volts)




8:43 PM Ohio University's Ross College of Engineering & Technology 19

Power Supplied vs. Power Absorbed

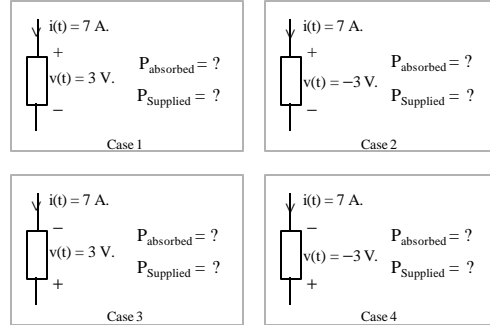


8:43 PM Ohio University's Ross College of Engineering & Technology 20

Power Supplied vs. Power Absorbed

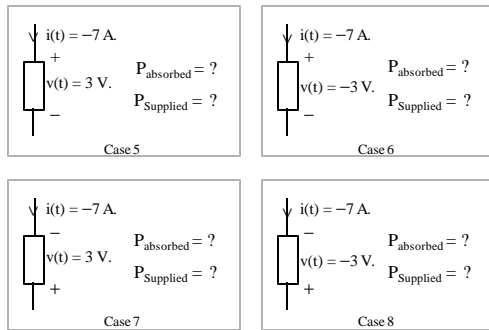


8:43 PM Ohio University's Ross College of Engineering & Technology 21

Power Supplied vs. Power Absorbed

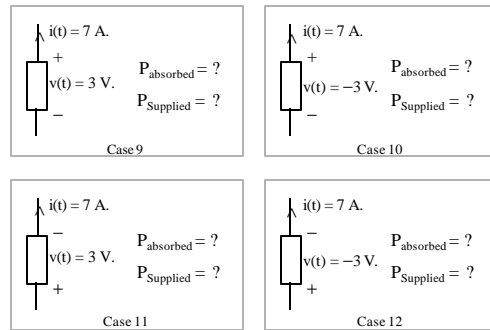

8:43 PM Ohio University's Ross College of Engineering & Technology 22

Power Supplied vs. Power Absorbed

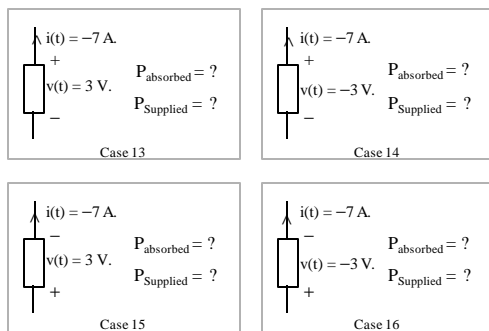

8:43 PM Ohio University's Ross College of Engineering & Technology 23


2.5 Kirchhoff's Voltage and Current Laws

- The behavior of electric-circuit currents and voltages are governed by these laws
- KCL is a statement of conservation of charge (see text p. 22)
- KVL is a statement of conservation of energy (see text p. 25)
- KCL and KVL are used in conjunction with circuit element laws; e.g., Ohm's Law (see text p. 28), etc. to perform electric circuit analysis

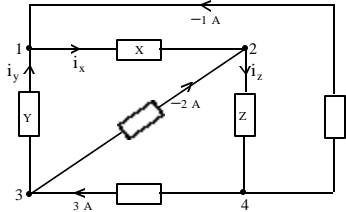8:43 PM Ohio University's Ross College of Engineering & Technology 24

Kirchhoff's Current Law (KCL)


- A circuit node is an electrical "location" of interest (see numbered black dots below)
- **KCL:** The sum-total of all currents entering (or leaving) each node equals zero



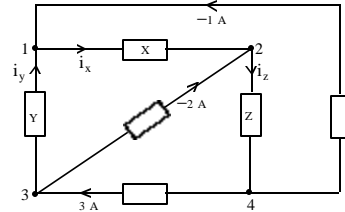8:43 PM Ohio University's Russ College of Engineering & Technology 25

Kirchhoff's Current Law (KCL) cont.


- **KCL Sum:** Each term in the sum is a current
- If summing *into* a node, each inbound current term has a positive sign and each outbound current term has a negative sign



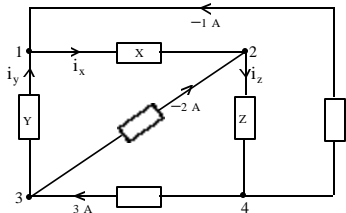8:43 PM Ohio University's Russ College of Engineering & Technology 26

Kirchhoff's Current Law (KCL) cont.


- **KCL at Node 1:** $+ i_y - i_x + (-1 \text{ A}) = 0 \text{ A}$ (I)
- **KCL at Node 2:** $+ i_x + (-2 \text{ A}) - i_z = 0 \text{ A}$ (II)
- **KCL at Node 3:** $- i_y - (-2 \text{ A}) + 3 \text{ A} = 0 \text{ A}$ (III)



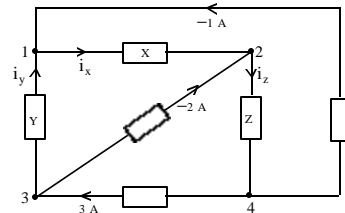8:43 PM Ohio University's Russ College of Engineering & Technology 27

Kirchhoff's Current Law (KCL) cont.


- (I), (II) & (III) have solution $i_x = 4 \text{ A}$, $i_y = 5 \text{ A}$ and $i_z = 2 \text{ A}$.
- Note that doing a KCL at node 4 is now redundant



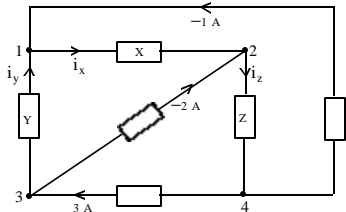8:43 PM Ohio University's Russ College of Engineering & Technology 28

Kirchhoff's Current Law (KCL) cont.


- **KCL Sum:** Each term in the sum is a current
- If summing *out of* a node, each outbound current term has a positive sign and each inbound current term has a negative sign



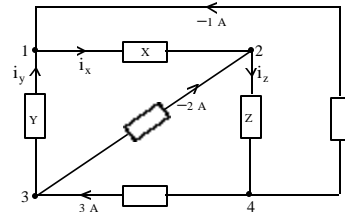8:43 PM Ohio University's Russ College of Engineering & Technology 29

Kirchhoff's Current Law (KCL) cont.


- **KCL at Node 1:** $- i_y + i_x - (-1 \text{ A}) = 0 \text{ A}$ (I)
- **KCL at Node 2:** $- i_x - (-2 \text{ A}) + i_z = 0 \text{ A}$ (II)
- **KCL at Node 3:** $+ i_y + (-2 \text{ A}) - 3 \text{ A} = 0 \text{ A}$ (III)



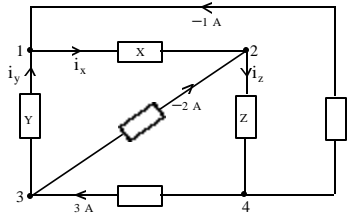8:43 PM Ohio University's Russ College of Engineering & Technology 30

Kirchhoff's Current Law (KCL) cont.


- Again, $i_x = 4$ A, $i_y = 5$ A, $i_z = 2$ A and KCL at Node 4 is redundant
- N.B.: See text Problem 2.15 (p. 50)



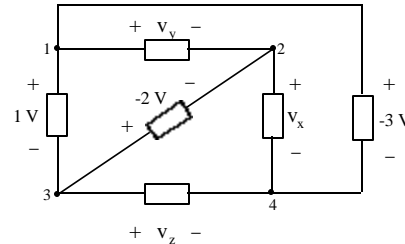8:43 PM Ohio University's Russ College of Engineering & Technology 31

Kirchhoff's Voltage Law (KVL)

- Relates a circuit's voltages to one another
- First must consider voltage *rise* vs. voltage *drop* concept




8:43 PM Ohio University's Russ College of Engineering & Technology 32

Voltage Rise vs. Voltage Drop

- Positive charge moving across a change of voltage from the positive polarity sign towards the negative polarity sign experiences a voltage *drop* (a decrease in its energy)
- Positive charge moving across a change of voltage from the negative polarity sign towards the positive sign experiences a voltage *rise* (an increase in its energy)

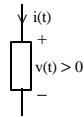
If $i(t) > 0$, the downward moving charge experiences a voltage *drop*. However, if $i(t) < 0$ then the upward moving charge experiences a voltage *rise*.



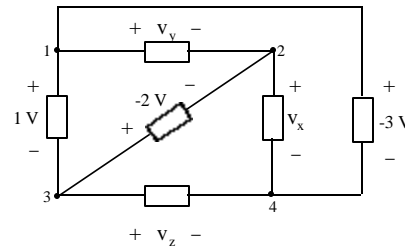8:43 PM Ohio University's Russ College of Engineering & Technology 33

Kirchhoff's Voltage Law (KVL)


- KVL: The sum-total of all voltage drops and voltages rises around any *closed* path—in any direction—equals zero



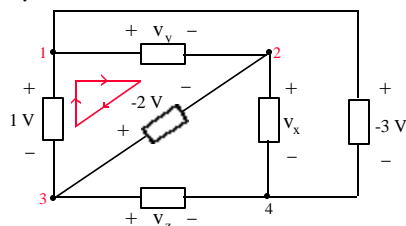8:43 PM Ohio University's Russ College of Engineering & Technology 34

Kirchhoff's Voltage Law (KVL)


- KVL for closed path $1 \rightarrow 2 \rightarrow 3 \rightarrow 1$ (using the "land on polarity sign" rule to determine the sign of each term in the sum):
- $-v_y + (-2\text{ V}) + 1\text{ V} = 0\text{ V}$ (I)



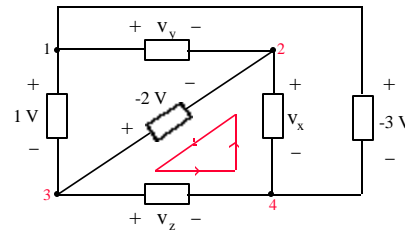8:43 PM Ohio University's Russ College of Engineering & Technology 35

Kirchhoff's Voltage Law (KVL)


- KVL for closed path $2 \rightarrow 3 \rightarrow 4 \rightarrow 2$ (using "land on polarity sign" rule to determine the sign of each term in the sum):
- $+(-2\text{ V}) - v_z + v_x = 0\text{ V}$ (II)



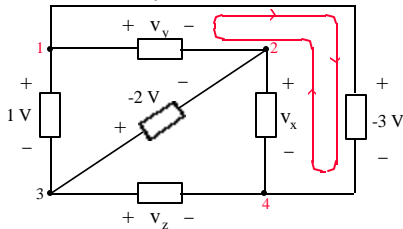8:43 PM Ohio University's Russ College of Engineering & Technology 36

Kirchhoff's Voltage Law (KVL)


- KVL for closed path 1→4→2→1 (using "land on polarity sign" rule to determine the sign of each term in the sum):
- $-(-3\text{ V}) + v_x + v_y = 0\text{ V}$ (III)



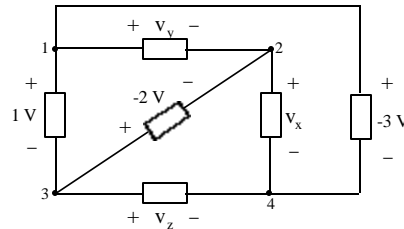8:43 PM Ohio University's Russ College of Engineering & Technology 37

Kirchhoff's Voltage Law (KVL)


- (I), (II) and (III) can be solved for v_x , v_y and v_z
- N.B.: There are other (now redundant) closed paths (also see Text Problem 2.23, p. 52)



8:43 PM Ohio University's Russ College of Engineering & Technology 38

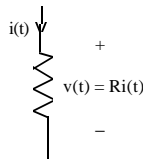2.6 The Resistor


- The (ideal) resistor is defined by Ohm's Law: $v(t) = Ri(t)$ where R is a positive constant *and*
- $v(t)$ and $i(t)$ are *also* related by the passive sign convention (this second requirement is implicitly built into the Ohm's Law equation)



8:43 PM Ohio University's Russ College of Engineering & Technology 39

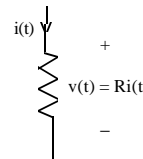2.6 The Resistor cont.


- If $i(t) > 0$ so too is $v(t) = Ri(t)$ and vice versa; i.e., if $i(t) < 0$ so is $v(t)$.
- So the resistor's absorbed power (voltage-current product) is always $P_{\text{absorbed}} = v(t)i(t) \geq 0$



8:43 PM Ohio University's Russ College of Engineering & Technology 40

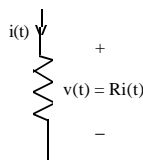2.6 The Resistor cont.

- $G = R^{-1}$ is called conductance (in S)
- $P_R(t) = vi = (Ri)i = i^2R$
- $P_R(t) = vi = v(v/R) = v^2/R$



8:43 PM Ohio University's Russ College of Engineering & Technology 41

2.6 The Resistor cont. (more about R)

- $R = \rho(L/A)$ where
- The resistivity (ρ) is material dependent (in $\Omega \cdot \text{m}$)
- The length (L) is in m.
- The cross-sectional area (A) is in m^2 .
- See Text Example 2.4 (p. 30) for an application



8:43 PM Ohio University's Russ College of Engineering & Technology 42

2.7 Voltage and Current Sources

- In circuit analysis, the ideal source concept is fundamental
- The ideal voltage source's terminal voltage is independent of the source's current
- The ideal current source's current is independent of the voltage across it

General: $v_s(t)$ or $i_s(t)$

DC: $v_s(t) = V$ or $i_s(t) = I$

$p(t)$ delivered = $v_s(t)i(t)$ (voltage source)
 $p(t)$ delivered = $v(t)i_s(t)$ (current source)

8:43 PM Ohio University's Russ College of Engineering & Technology 43

2.7 Source modeled via ideal source & resistor

- An actual source can be modeled using ideal circuit elements (e.g., ideal source & resistor—see below)
- KVL: $12 \text{ v.} - R_s i - v = 0 \text{ v.}$ or
- $v = 12 \text{ v.} - R_s i$ (linear equation)

8:43 PM Ohio University's Russ College of Engineering & Technology 44

2.7 Source modeled via ideal source & resistor

- $v = 12 \text{ v.} - R_s i$ can be solved for ...
- $i = (12 \text{ v.}/R_s) - v/R_s$ (linear equation)
- The above current equation corresponds to KCL at node n in the circuit shown below

8:43 PM Ohio University's Russ College of Engineering & Technology 45

2.7 Source modeled via ideal source & resistor

- The preceding *source transformation* analysis should be committed to memory, according to the text!

8:43 PM Ohio University's Russ College of Engineering & Technology 46

2.8 Signal waveforms

DC: $x(t) = X$ (constant)

Saw tooth $x(t) = x(t \pm nT)$ (periodic)

$n = 1, 2, 3, \dots$ (integer)
 $T =$ Period (in sec.)
 $f = 1/T$ Frequency (in Hz.)

8:43 PM Ohio University's Russ College of Engineering & Technology 47

2.8 Signal waveforms cont.

Sinusoid: $x(t) = A \sin(\omega t + \phi)$ (periodic)

8:43 PM Ohio University's Russ College of Engineering & Technology 48

2.8 Signal waveforms cont.

- Waveforms can be *numerically* compared (as opposed to *visually* compared) by way of numerical attributes which measure some meaningful waveform property
- Average value is intuitively appealing (it measures a waveform's DC content)

$$x_{AVE} = \frac{1}{T} \int_t^{t+T} x(\tau) d\tau$$

(Where T is x(t)'s period)

2.8 Signal waveforms cont.

- The RMS (Root-Mean-Square) value measures a *periodic* waveform's *average* power
- RMS values of sinusoidal voltages and currents are the vernacular of the electric power industry

$$x_{RMS} = \sqrt{\frac{1}{T} \int_t^{t+T} x^2(\tau) d\tau}$$

(Where T is x(t)'s period)

2.8 Signal waveforms cont.


- A *current* signal's RMS value is a measure of its *average* power

$$P_{AVE} = \frac{1}{T} \int_t^{t+T} p(\tau) d\tau$$

$$P_{AVE} = \frac{1}{T} \int_t^{t+T} Ri^2(\tau) d\tau = I_{RMS}^2$$

$$P_{AVE} = R \left[\frac{1}{T} \int_t^{t+T} i^2(\tau) d\tau \right]$$
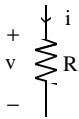
$$P_{AVE} = RI_{RMS}^2 \quad (\text{QED})$$



2.8 Signal waveforms cont.


- A *voltage* signal's RMS value is a measure of its *average* power

$$P_{AVE} = \frac{1}{T} \int_t^{t+T} p(\tau) d\tau$$

$$P_{AVE} = \frac{1}{T} \int_t^{t+T} v^2(\tau)/R d\tau = V_{RMS}^2$$

$$P_{AVE} = \frac{1}{R} \left[\frac{1}{T} \int_t^{t+T} v^2(\tau) d\tau \right]$$
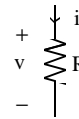
$$P_{AVE} = V_{RMS}^2 / R \quad (\text{QED})$$




2.8 Signal waveforms cont.

- Moral: A periodic signal's RMS value measures how powerful the signal is
- See text p. 38 for a sample RMS value calculation
- Another important RMS result (see text p. 39) is that the RMS value of the general sinusoidal waveform $x(t) = A\sin(\omega t + \phi)$ is $A/\sqrt{2} \approx 0.707A$
- Ergo, it is easy to program meters (e.g., VOMs, DVMs, etc.) to display the RMS values of the AC (sinusoidal) waveforms encountered in the electric power industry

2.8 Signal waveforms cont.

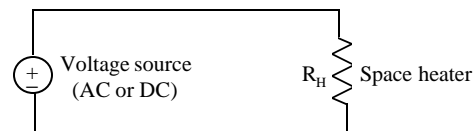
Example 2-2

The resistance space heater (of constant resistance R_H) when supplied by a $170 \sin(120\pi t)$ V. (t in seconds) sinusoidal (AC) voltage source takes 5 minutes to raise a room's temperature 3° F. If the same heater is supplied by a 48 Volt (DC) voltage source, how long will it take (in minutes) to do the same job?



2.8 Signal waveforms cont.

Example 2-2 cont.

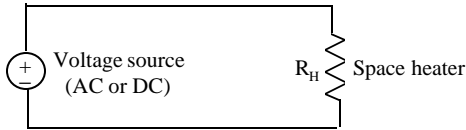

$$E_{AC} = \text{Energy for AC case} = P_{ave} \times T_{AC} = [(V_{RMS})^2/R_H] \times 5 \text{ Min.}$$

$$\therefore E_{AC} = [(170 \text{ V.}/\sqrt{2})^2/R_H] \times 5 \text{ Min.}$$


$$E_{DC} = \text{Energy for DC case} = P_{DC} \times T_{DC} = [(V_{DC})^2/R_H] \times T_{DC}$$

$$\therefore E_{DC} = [(48 \text{ V.})^2/R_H] \times T_{DC}$$

Then: $E_{AC} = [(170 \text{ V.}/\sqrt{2})^2/R_H] \times 5 \text{ Min.} = [(48 \text{ V.})^2/R_H] \times T_{DC} = E_{DC}$
which yields $T_{DC} \approx 31 \text{ Min.}$

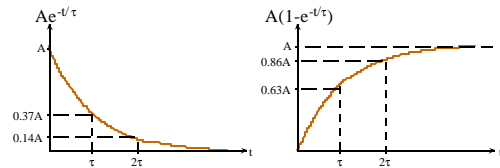2.8 Signal waveforms cont.


- Exponential waveform: $x(t) = Ae^{-t/\tau}$ (t is in seconds)
- Time constant (parameter) is τ (also in seconds)
- Captures transient behavior of many physical phenomena (e.g., radioactive decay, mechanical motion, electrical transients, etc.)



2.8 Signal waveforms cont.

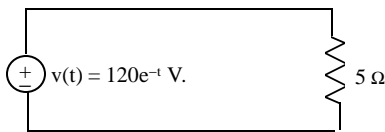
Example 2-3

An ideal exponential voltage source of $120e^{-t}$ V. supplies power to a 5Ω resistor. Calculate the following quantities for the time period $0 \leq t < \infty$: the total energy (in Joules) absorbed by the resistor, the total charge (in Coulombs) that flows through the resistor, the average voltage (in Volts) across the resistor and the time it takes an AC, 120 V. (RMS), 60 W., incandescent lamp to consume the same energy as the resistor.



2.8 Signal waveforms cont.

Example 2-3 cont.

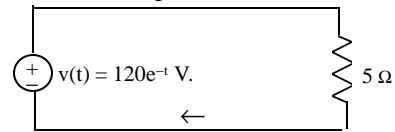

$$i(t) = v(t)/5\Omega = 24e^{-t} \text{ A.}$$


Power: $p(t) = v(t) \times i(t) = 5\Omega \times i^2(t) = v^2(t)/5\Omega = 2880e^{-2t} \text{ W.}$

Energy: $W_R = \int_0^{\infty} p(\tau) d\tau = \int_0^{\infty} 2880e^{-2\tau} d\tau = 1.44 \text{ kJ.}$

Charge: $Q = \int_0^{\infty} i(\tau) d\tau = \int_0^{\infty} 24e^{-\tau} d\tau = 24 \text{ C.}$

2.8 Signal waveforms cont.

Example 2-3 cont.

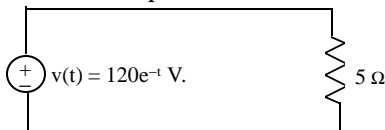


The average voltage is: $V_{ave.} = W/Q = 1.44 \text{ kJ.}/24\text{C.} = 60 \text{ J/C}$
 $\therefore V_{ave.} = 60 \text{ V.}$ (in what sense is this the voltage's average?)

Equating the lamp's energy to the resistor's energy yields:
 $P_{lamp} \times T_{lamp} = 1.44 \text{ kJ.} = W_{5\Omega}$ (where $P_{lamp} = 60 \text{ W.} = 60 \text{ J./Sec.}$)

Ergo, $T_{lamp} = 24 \text{ Seconds}$

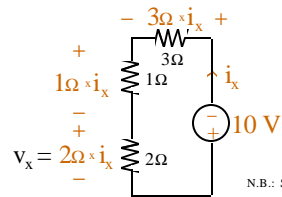2.9 Analysis of Simple Circuits


- *Single-loop circuit analysis* involves several applications of Ohm's Law ($1\Omega \times i_x$, $2\Omega \times i_x$ and $3\Omega \times i_x$ (note use of passive sign convention on schematic)) and ...
- One KVL: $2\Omega \times i_x + 1\Omega \times i_x + 3\Omega \times i_x + 10 \text{ V.} = 0 \text{ V.}$ which has solution $i_x = -5/3 \text{ A.}$



N.B.: See text Problem 2.31, p. 54.

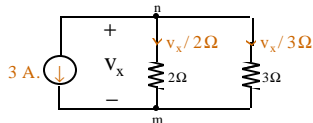2.9 Analysis of Simple Circuits cont.


- *Single-node-pair circuit analysis* involves several applications of Ohm's Law ($v_x / 2\Omega$ and $v_x / 3\Omega$)—note use of passive sign convention on schematic and ...
- One KCL (at node n or m): $3 \text{ A.} + v_x / 2\Omega + v_x / 3\Omega = 0 \text{ A.}$ which has solution $v_x = -3.6 \text{ V.}$



N.B.: See text Problem 2.30, p. 53.

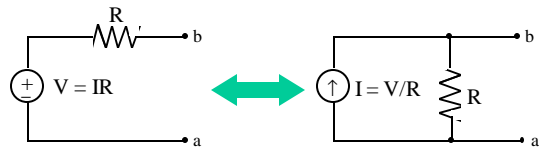2.9 Analysis of Simple Circuits cont.


- *Source transformations* (described earlier and repeated below) can be used to convert some circuits to either a *single-loop circuit* or *single-node-pair circuit*—which can then be analyzed as described earlier



2.9 Analysis of Simple Circuits cont.

Example 2-4


Find i_x and v_x

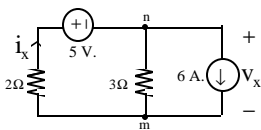

N.B.: See text Problem 2.39, p. 56.


Example 2-4 cont.

- Step 1: Create single-node-pair circuit using source conversion

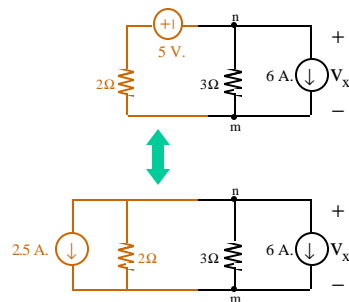


Example 2-4 cont.

- Step 2: Solve the single-node-pair circuit for v_x
- KCL at node n:
 $2.5 \text{ A.} + v_x / 2\Omega + v_x / 3\Omega + 6 \text{ A.} = 0 \text{ A.}$
- Which has solution $v_x = -10.2 \text{ V.}$

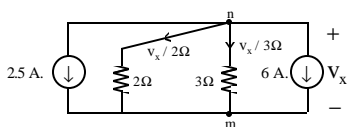

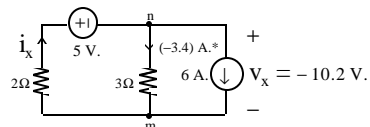Example 2-4 cont.


- Step 3: With v_x now known, solve the original circuit for i_x
- KCL at node n: $i_x - (-3.4 \text{ A.}) - 6 \text{ A.} = 0 \text{ A.}$
- Which has solution $i_x = 2.6 \text{ A.}$




N.B.: $(-10.2 \text{ V.} / 3\Omega) = -3.4 \text{ A.}$

2.9 Analysis of Simple Circuits cont.

Example 2-5: Find I_x and V_x

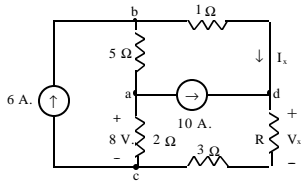


Example 2-5 cont.

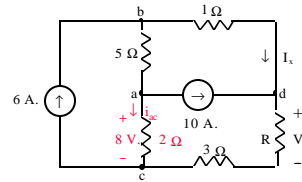


Ohm's Law: $i_{ac} = 8 \text{ V} / 2 \Omega = 4 \text{ A}$.

Example 2-5 cont.

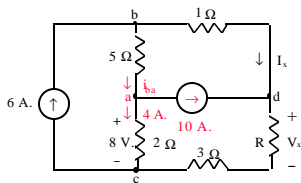


KCL at node a: $i_{ba} - 4 \text{ A} - 10 \text{ A} = 0 \text{ A}$
 $\therefore i_{ba} = 14 \text{ A}$.

Example 2-5 cont.

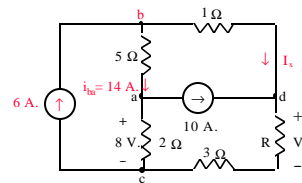


KCL at node b: $6 \text{ A} - 14 \text{ A} - I_x = 0 \text{ A}$
 $\therefore I_x = -8 \text{ A}$.

Example 2-5 cont.

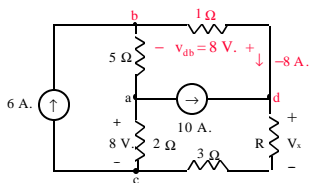


Ohm's Law: $v_{db} = 1 \Omega \times [-(-8 \text{ A})] = 8 \text{ V}$.

Example 2-5 cont.

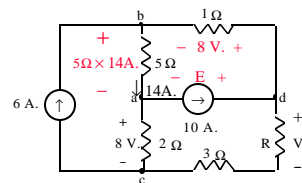


KVL (Top-right mesh): $5 \Omega \times 14 \text{ A} + 8 \text{ V} - E = 0 \text{ V}$
 $\therefore E = 78 \text{ V}$.

Example 2-5 cont.

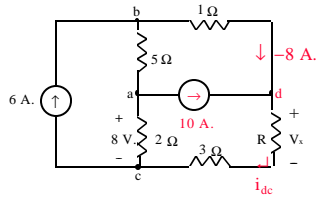


KCL at node d: $10 \text{ A.} + (-8 \text{ A.}) - i_{dc} = 0 \text{ A.}$
 $\therefore i_{dc} = 2 \text{ A.}$

Example 2-5 cont.

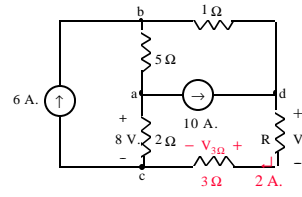

Ohm's Law: $V_{3\Omega} = 3 \Omega \times 2 \text{ A.} = 6 \text{ V.}$

Example 2-5 cont.

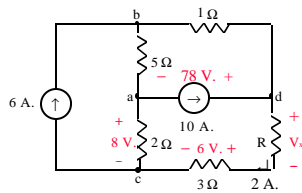

KVL (Bottom-right mesh):
 $8 \text{ V.} + 78 \text{ V.} - V_X - 6 \text{ V.} = 0 \text{ V.}$
 $\therefore V_X = 80 \text{ V.}$

We welcome your questions with Enthusiasm!!



Brian Manhire, Ph.D.
 Professor of Electrical Engineering
 OHIO UNIVERSITY
 School of Electrical Engineering & Computer Science
 Stocker Center
 Athens OH 45701-2270
 740-593-0179 phone
 740-593-0037 fax
 bmanhire1@ohio.edu

School of Electrical Engineering and Computer Science

