

Microsoft PowerPoint® Presentation Graphics for
EE 313: Basic Electrical Engineering I

Prepared by Brian Manhire, Ph.D.
 Professor of Electrical Engineering



*Stocker Center, home of Ohio University's
 Russ College of Engineering & Technology*

Microsoft PowerPoint® Presentation Graphics
 © Copyright 1998 Brian Manhire

For Part 1 of

**Introduction to Electrical
 Engineering, 2/e**

by **C.R. Paul, S.A. Nasar
 and L.E. Unnewehr**

© 1992, McGraw-Hill, Inc.

**Chapter 5
 AC Circuits**

Introduction to Electrical Engineering

Chapter 5: AC Circuits

- 5.1 Sinusoidal (AC) Sources
- 5.2 Response of Circuits to AC Sources
- 5.3 Complex Numbers and Complex Algebra
- 5.4 Use of the Complex Exponential Source
- 5.5 The Phasor Circuit
- 5.6 Average Power, Reactive Power and Power Factor
- 5.7 Frequency Response of Circuits

5.1 Sinusoidal (AC) Sources


$$f(t) = A \sin(\omega t + \phi)$$

where A = Amplitude, ω = Radian Frequency (Rad./Sec.),

f = Frequency (Hz., formerly cps) where $\omega = 2\pi f$,

T = 1/f = Period (in Sec., mSec., etc.) and

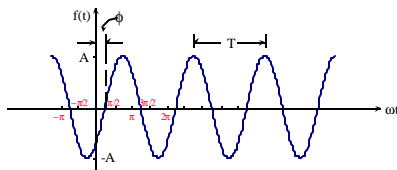ϕ = Phase angle (in Rad. or Degrees) where f(t) is said to
 "Lag" (time delay) its $\phi = 0$ counterpart if $\phi < 0$
 and "lead" (time advance) if $\phi > 0$



8:45 PM

5

5.1 Sinusoidal (AC) Sources cont.

Some useful identities

$$A \cos(\omega t) = A \sin(\omega t + \pi/2) = A \sin(\omega t + 90^\circ)$$

$$A \sin(\omega t) = A \cos(\omega t - \pi/2) = A \cos(\omega t - 90^\circ)$$

$$-A \cos(\omega t) = A \cos(\omega t \pm \pi) = A \cos(\omega t \pm 180^\circ)$$

$$-A \sin(\omega t) = A \sin(\omega t \pm \pi) = A \sin(\omega t \pm 180^\circ)$$

$$\sin(\omega t \pm \phi) = \sin(\omega t)\cos(\phi) \pm \cos(\omega t)\sin(\phi)$$

$$\cos(\omega t + \phi) = \cos(\omega t)\cos(\phi) - \sin(\omega t)\sin(\phi)$$

$$\cos(\omega t - \phi) = \cos(\omega t)\cos(\phi) + \sin(\omega t)\sin(\phi)$$

$$A \sin(\omega t + \phi) = A_1 \sin \omega t + A_2 \cos \omega t$$

$$\text{where: } A_1 = A \cos \phi \text{ and } A_2 = A \sin \phi$$

$$B \cos(\omega t + \phi) = B_1 \cos \omega t + B_2 \sin \omega t$$

$$\text{where: } B_1 = B \cos \phi \text{ and } B_2 = -B \sin \phi$$

8:45 PM

6


5.2 Steady-State Response of Circuits to AC Sources
KVL for the RL circuit below yields the differential equation:

$$2(di(t)/dt) + 3i(t) = 10\cos(3t)$$

The mathematical objective is to find a *particular solution* of the equation (i.e., *any* solution that will satisfy the equation)

The standard approach is to choose
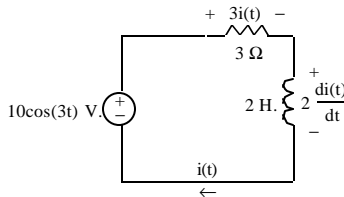
$$i(t) = I_C \cos 3t + I_S \sin 3t \text{ (an educated guess, but why?)}$$



5.2 Steady-State Response of Circuits to AC Sources

Substituting $i(t) = I_C \cos 3t + I_S \sin 3t$ into the differential equation $2(di(t)/dt) + 3i(t) = 10\cos(3t)$ yields:

$$2(-3I_C \sin 3t + 3I_S \cos 3t) + 3(I_C \cos 3t + I_S \sin 3t) = 10\cos(3t) \text{ or } \dots$$

$$(3I_C + 6I_S) \cos 3t + (-6I_C + 3I_S) \sin 3t = 10 \cos 3t + 0 \sin 3t$$

Equating coefficients yields:

$$3I_C + 6I_S = 10 \text{ and } -6I_C + 3I_S = 0$$

Which have solution $I_C \approx 0.667$ and $I_S \approx 1.33$

So a particular solution is $i(t) \approx 0.667 \cos 3t + 1.33 \sin 3t$

$$\text{However, } A \cos(\omega t) + B \sin(\omega t) = (A^2 + B^2)^{1/2} \cos(\omega t - \tan^{-1}(B/A))$$

$$\therefore i(t) \approx 1.491 \cos(3t - 63.43^\circ)$$

Moral: There's gotta be a better way!

5.3 Complex Numbers and Complex Arithmetic


The *phasor method* (invented in 1893 by Charles Proteus Steinmetz, 1865-1923) is the backbone of AC steady-state circuit analysis

The principle benefit of the phasor method is that its concepts essentially render AC steady-state circuit analysis analogous to DC steady-state analysis—by way of complex arithmetic

Ergo, in order to gainfully employ the phasor method, the electric circuit analyst must be proficient in working with complex numbers, complex arithmetic and complex algebra

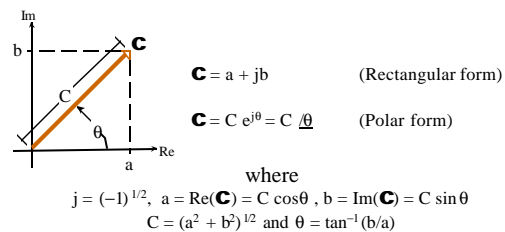5.3 Complex Numbers and Complex Arithmetic cont.

A complex number manifests itself in two forms—and consists of two numbers (per form) and presents itself as a vector in the complex plane as shown below



5.3 Complex Numbers and Complex Arithmetic cont.

Addition and subtraction of complex numbers is defined in rectangular form *only* as follows:

If $\mathbf{A} = a + jb$ and $\mathbf{B} = c + jd$ then

$$\mathbf{A} + \mathbf{B} = (a + c) + j(b + d) \text{ and}$$

$$\mathbf{A} - \mathbf{B} = (a - c) + j(b - d)$$

Multiplication and division is defined in polar form as follows:

If $\mathbf{A} = A \underline{\theta}_A$ and $\mathbf{B} = B \underline{\theta}_B$ then

$$\mathbf{AB} = AB \underline{\theta}_A + \underline{\theta}_B \text{ and}$$

$$\mathbf{A/B} = A/B \underline{\theta}_A - \underline{\theta}_B$$

and in rectangular form as follows ...

5.3 Complex Numbers and Complex Arithmetic cont.

Multiplication and division in rectangular form:

If $\mathbf{A} = a + jb$ and $\mathbf{B} = c + jd$ then

$$\mathbf{AB} = (a + jb)(c + jd)$$

$$= (ac - bd) + j(ad + bc) \text{ and}$$

$$\mathbf{A/B} = (a + jb)/(c + jd)$$

$$= [(ac + bd) + j(bc - ad)]/(c^2 + d^2)$$

Also, the *conjugate* of a phasor $\mathbf{A} = a + jb = C \underline{\theta}$ is

$$\mathbf{A}^* = a - jb = C \underline{-\theta} \text{ so that } \mathbf{AA}^* = (a + jb)(a - jb)$$

$$= a^2 + b^2 = C^2 \text{ also } \dots$$

$$1 = +1 + j0 = 1 \underline{0^\circ}; -1 = -1 + j0 = 1 \underline{\pm 180^\circ}$$

$$\text{and } j = 0 + j1 = 1 \underline{90^\circ}$$

5.3 Complex Numbers and Complex Arithmetic cont.

Given: $\mathbf{A} = 1 - j3$ and $\mathbf{B} = 2\angle -30^\circ$, the following complex arithmetic yields the following numerical results (see text Problem 5.7, p. 202):

$$\mathbf{A} + \mathbf{B} = (1 - j3) + 2\angle -30^\circ \approx (1 - j3) + (1.732 - j1) \approx 2.732 - j4 \approx 4.844\angle -55.67^\circ$$

$$\mathbf{A} - \mathbf{B} = (1 - j3) - 2\angle -30^\circ \approx (1 - j3) - (1.732 - j1) \approx -0.732 - j2 \approx 2.130\angle -110.1^\circ$$

$$\mathbf{AB} = (1 - j3)(2\angle -30^\circ) \approx (3.162\angle -71.57^\circ)(2\angle -30^\circ) \approx 6.324\angle -101.57^\circ \approx -1.268 - j6.195$$

$$\mathbf{A/B} \approx (3.162\angle -71.57^\circ)/(2\angle -30^\circ) \approx 1.581\angle -41.57^\circ \approx 1.183 - j1.049$$

$$1/\mathbf{A} \approx 1/0\angle (3.162\angle -71.57^\circ) \approx 0.3163\angle +71.57^\circ \approx 0.1 - j0.3 \text{ and } \mathbf{AA}^* \approx 3.162^2 \approx 10.0$$

8:45 PM Ohio University's Ross College of Engineering & Technology 13

5.4 Use of Complex Exponential Source

In AC steady-state circuit analysis, sinusoidal sources can be replaced by (mathematically) related complex exponential sources

Then the particular solution (steady-state response) for the exponential source(s) scenario is also a complex exponential that is *much* easier to determine than its sinusoidal-source counterpart—in fact, it can be found without (directly) using the time dependent portion of any source or response complex exponentials at all!

The particular solution for any sinusoidally driven (steady-state) scenario can be easily deduced from its complex exponential counterpart


All of the above logic depends on linearity—so it's the first item on our "phasor analysis" agenda

8:45 PM Ohio University's Ross College of Engineering & Technology 14

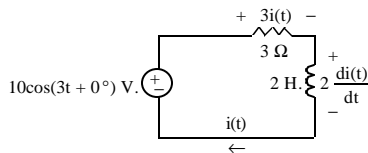5.4 Use of Complex Exponential Source cont.

However, before proceeding to linearity recall that for the circuit below the circuit's current response to the sinusoidal voltage source is $i(t) \approx 1.49\cos(3t - 63.43^\circ)$ A. How do the voltage source and current response differ mathematically?

They differ by only two numbers—magnitude (10 V. versus 1.49 A.) and phase angle (0° versus -63.43°)!




8:45 PM Ohio University's Ross College of Engineering & Technology 15

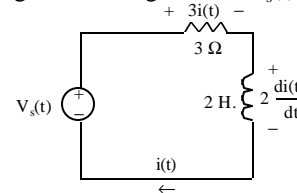5.4 Use of Complex Exponential Source cont.

Returning to linearity, consider the scenario shown below and analyzed earlier—where the original sinusoidal source $10\cos(3t)$ V. ($10\sin(3t)$ V. in text Section 5.2) has been replaced by the generic source $V_s(t)$

The differential equation relating the current $i(t)$ responding to the voltage source $V_s(t)$ is ...



8:45 PM Ohio University's Ross College of Engineering & Technology 16


5.4 Use of Complex Exponential Source cont.

$$2(di(t)/dt) + 3i(t) = V_s(t)$$

Is this source-response relationship linear?

How can this question be answered?

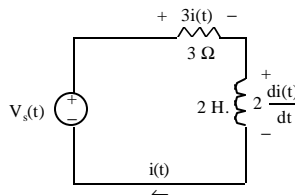Mathematically interrogate the differential equation to see if superposition applies!



8:45 PM Ohio University's Ross College of Engineering & Technology 17

5.4 Use of Complex Exponential Source cont.

Let $i_1(t)$ be a particular solution for source $V_{s1}(t)$ so that $2(di_1(t)/dt) + 3i_1(t) = V_{s1}(t)$ (I.)

Let $i_2(t)$ be a particular solution for source $V_{s2}(t)$ so that $2(di_2(t)/dt) + 3i_2(t) = V_{s2}(t)$ (II.)

Multiply (II.) by the constant K to obtain

$$2(d[Ki_2(t)]/dt) + 3[Ki_2(t)] = KV_{s2}(t) \quad \text{(III.)}$$

$\therefore Ki_2(t)$ is a particular solution for source $KV_{s2}(t)$

Add equations (I.) and (III.) to obtain

$$2(d[i_1(t) + Ki_2(t)]/dt) + 3[i_1(t) + Ki_2(t)] = [V_{s1}(t) + KV_{s2}(t)]$$

$\therefore [i_1(t) + Ki_2(t)]$ is a particular solution for $[V_{s1}(t) + KV_{s2}(t)]$

\therefore superposition applies (\therefore the circuit is linear)

8:45 PM Ohio University's Ross College of Engineering & Technology 18

5.4 Use of Complex Exponential Source cont.

Next consider time-shifting the circuit's voltage source by the time delay τ

This is achieved mathematically by replacing (renaming) the *independent* variable t with $t - \tau$ to obtain ...

$$2(di(t - \tau)/dt) + 3i(t - \tau) = V_s(t - \tau)$$

Which indicates that time-shifting the input by τ time-shifts the particular solution (output) by the same amount (τ)

So if $V_s(t) = 10\sin(3t)$ V. (= $10\cos(3t - \pi/2)$ V.), ...

What's $i(t)$?

$$i(t) \approx 1.49\cos(3t - 63.43^\circ - \pi/2)$$
 A. \therefore

$$i(t) \approx 1.49\sin(3t - 63.43^\circ)$$
 A.

(Which is verified on text p. 150)

5.4 Use of Complex Exponential Source cont.

Next consider the (Euler's Equation) ensemble of sources $10\cos(3t) + j10\sin(3t)$ V. = $10e^{j3t}$ V.

Note that the above equation is just $[V_{s1}(t) + KV_{s2}(t)]$ with $V_{s1}(t) = 10\cos(3t)$, $V_{s2}(t) = 10\sin(3t)$ and $K = j$

Superposition applies so from earlier results

$$i(t) = i_1(t) + ji_2(t)$$

$$\text{where } i_1(t) \approx 1.49 \cos(3t - 63.43^\circ)$$
 A.

$$\text{and } i_2(t) \approx 1.49 \sin(3t - 63.43^\circ)$$
 A.

Then $i(t) \approx 1.49\cos(3t - 63.43^\circ) + j1.49\sin(3t - 63.43^\circ)$ A.

Which by Euler's Equation is $i(t) \approx 1.49e^{j(3t - 63.43^\circ)}$ or ...

$i(t) \approx 1.49e^{-j63.43^\circ}e^{j3t}$ where the complex coefficient of the e^{j3t} time function is the *complex number I* $\gg 1.49e^{-j63.43^\circ}$

5.4 Use of Complex Exponential Source cont.

Recapitulation

If the source is $V_s(t) = 10e^{j3t}$ V.,
the response is $i(t) \approx 1.49e^{j(3t - 63.43^\circ)}$ A.

If the source is $V_{s1}(t) = 10\cos(3t) = \text{Re}[10e^{j3t}$ V.] = $\text{Re}[V_s(t)]$,
the response is $i_1(t) \approx 1.49\cos(3t - 63.43^\circ)$ A.
= $\text{Re}[1.49e^{j(3t - 63.43^\circ)}$ A.] = $\text{Re}[i(t)]$

If the source is $V_{s2}(t) = 10\sin(3t) = \text{Im}[10e^{j3t}$ V.] = $\text{Im}[V_s(t)]$,
the response is $i_2(t) \approx 1.49 \sin(3t - 63.43^\circ)$ A.
= $\text{Im}[1.49e^{j(3t - 63.43^\circ)}$ A.] = $\text{Im}[i(t)]$

Note that the interrelationship between all three sources and their current-response counterparts is *always* the same, namely Euler's Equation!

5.4 Use of Complex Exponential Source cont.

The last theoretical consideration to explore is why the exponential source case is worthy of consideration at all

The reason is that the exponential source case provides a computationally compact means for obtaining particular solutions for sinusoidally driven circuits—in other words, it's computationally expedient!


To see this, consider the circuit analyzed earlier—but now driven instead by the exponential counterpart of its original sinusoidal source, namely ...

5.4 Use of Complex Exponential Source cont.

The differential equation is: $2(di(t)/dt) + 3i(t) = V_s(t)$

Let the particular solution *resemble* the source so that it too is a complex exponential differing from the source only in magnitude and phase angle; i.e., let

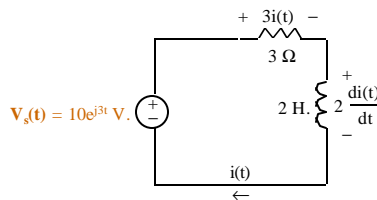$i(t) = Ie^{j3t}$ where I is a *complex number*




5.4 Use of Complex Exponential Source cont.

Then $2(d\mathbf{i}(t)/dt) + 3\mathbf{i}(t) = V_s(t)$ or ...

$$2(d(Ie^{j3t})/dt) + 3(Ie^{j3t}) = 10e^{j3t}$$
 V. or ...

$$2(j3)Ie^{j3t} + 3(Ie^{j3t}) = 10e^{j3t}$$
 V. or ...

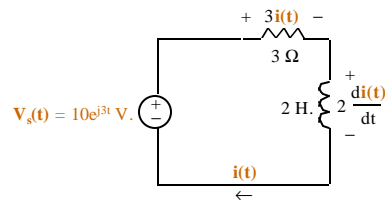$(3 + j6)Ie^{j3t} = 10e^{j3t}$ V. and the e^{j3t} factors (time functions) cancel leaving ...



5.4 Use of Complex Exponential Source cont.
 $\mathbf{I} = 10 \text{ V.}/(3 + j6)$ —which is an equation in complex numbers *only* (no time functions at all) which yields the magnitude and phase angle unique to the current response, namely ...

$\mathbf{I} = 10\angle 0^\circ \text{ V.}/(3 + j6) \approx (10\angle 0^\circ)/(6.71\angle 63.43^\circ)$
 $\approx 1.49\angle -63.43^\circ$ (Do these figures look familiar?)

8:45 PM Ohio University's Ross College of Engineering & Technology 25

5.4 Use of Complex Exponential Source cont.
 Therefore, $\mathbf{i}(t) = \mathbf{I}e^{j3t} \approx 1.49\angle -63.43^\circ e^{j3t} \text{ A.}$
 $\approx 1.49e^{-j63.43^\circ} e^{j3t} \text{ A.} \approx 1.49e^{j(3t-63.43^\circ)} \text{ A.}$
 and ...

If $V_s(t) = 10\cos(3t) \text{ V.} = \text{Re}[10e^{j3t} \text{ V.}]$, what's $i(t)$?
 $i(t) \approx \text{Re}[1.49e^{j(3t-63.43^\circ)}] \approx 1.49\cos(3t - 63.43^\circ) \text{ A.}$

Likewise

If $V_s(t) = 10\sin(3t) \text{ V.} = \text{Im}[10e^{j3t} \text{ V.}]$, what's $i(t)$?
 $i(t) \approx \text{Im}[1.49e^{j(3t-63.43^\circ)}] \approx 1.49\sin(3t - 63.43^\circ) \text{ A.}$

The final task is to develop a method to streamline the calculations even further
 This method is ...

8:45 PM Ohio University's Ross College of Engineering & Technology 26

5.5 The Phasor Circuit
 Recall that, $\mathbf{I} = 10 \text{ V.}/(3 + j6)$ which is an equation in complex numbers (no time functions at all!)
 How does this compare with the calculation of $\mathbf{I} = 10\angle 0^\circ \text{ V.}/(3 + j6) \Omega \approx (10\angle 0^\circ \text{ V.})/(6.71\angle 63.43^\circ \Omega)$
 $\approx 1.49\angle -63.43^\circ \text{ A.}$ for the *conceptual* circuit below;
 i.e., do these current results look familiar?

8:45 PM Ohio University's Ross College of Engineering & Technology 27

5.5 The Phasor Circuit cont.
 The phasor circuit can be redrawn as shown below
 Note that the phasor circuit provides a (*conceptual schematic tool*) for finding the magnitude and phase angle of the current (which are its only unique properties!)
 Of the complex numbers V_s , Z and I , which do not correspond to time functions?

By KVL, $\mathbf{I} = V_s / Z = (10\angle 0^\circ \text{ V.}) / (3 + j6)\Omega \approx 1.49\angle -63.43^\circ \text{ A.}$

8:45 PM Ohio University's Ross College of Engineering & Technology 28

5.5 The Phasor Circuit cont.
 Only currents and voltages are phasors (i.e., have time-function counterparts)
 Don't believe it? Then what's $Z(t)$ for the phasor circuit below if the phasors correspond to sinusoids (so that $V_s(t) = 10\cos(3t) \text{ V.}$ and $i(t) \approx 1.49\cos(3t - 63.43^\circ) \text{ A.}$)?
 Since $Z = (3 + j6) \Omega \approx 6.71\angle 63.43^\circ \Omega$,
 is $Z(t) = 6.71\cos(3t - 63.43^\circ) \Omega$ for example!!!

By KVL, $\mathbf{I} = V_s / Z = (10\angle 0^\circ \text{ V.}) / (3 + j6)\Omega \approx 1.49\angle -63.43^\circ \text{ A.}$

8:45 PM Ohio University's Ross College of Engineering & Technology 29

5.5 The Phasor Circuit cont.
 The "Rules and Regulations" for phasor sources and impedances are developed in text section 5.5 and are summarized below

| | |
|---|---|
| $Z_C = 1/j\omega C = -j(1/\omega C)$ $V = (1/j\omega C)I = -j(1/\omega C)I$ | |
| $Z_R = R$ $V = RI$ | $Z_L = j\omega L$ $V = j\omega LI$ |
| $V_s = V\angle\theta$ $V_s = V\angle\theta$ Can represent $V\sin(\omega t + \theta)$ or $V\cos(\omega t + \theta)$ —but <i>not</i> both at once! | $I_s = I\angle\theta$ $I_s = I\angle\theta$ Can represent $I\sin(\omega t + \theta)$ or $I\cos(\omega t + \theta)$ —but <i>not</i> both at once! |

8:45 PM Ohio University's Ross College of Engineering & Technology 30


5.5 The Phasor Circuit cont.


The following equations from text p.171 are useful in reconciling situations where both sinusoidal and cosinusoidal sources are present

$$\sin(\omega t + \theta) = \cos(\omega t + \theta - 90^\circ)$$

$$\cos(\omega t + \theta) = \sin(\omega t + \theta + 90^\circ)$$

(see example below)

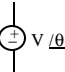If $V \cos(\omega t + \theta)$'s phasor representation is \Rightarrow 

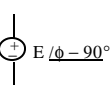Then $E \sin(\omega t + \phi)$'s phasor representation is \Rightarrow 

5.5 The Phasor Circuit cont.—Example 5-1


Find the AC steady-state current $i(t)$ —see text problem 5.26 (p.204)

Let the phasors represent cosinusoids so that the current source's phasor current is $3\angle 30^\circ$ A.

Then the voltage source's phasor voltage is $10\angle -90^\circ$ V.

The capacitor's impedance is $-j[1/(3 \text{ Rad./sec.})(1/9 \text{ F})] = -j3 \Omega$

So the phasor circuit becomes ...

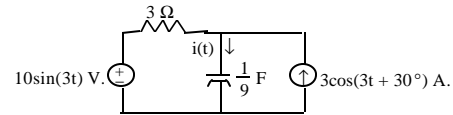

5.5 The Phasor Circuit cont.—Example 5-1 cont.


KCL at node n:

$$(10\angle -90^\circ \text{ V} - \mathbf{V}_n) / 3\Omega - \mathbf{V}_n / (-j3\Omega) + 3\angle 30^\circ \text{ A} = 0 \text{ A}.$$

Which has solution $\mathbf{V}_n \approx 6.745\angle -80.21^\circ$ V.

Then $\mathbf{I} = \mathbf{V}_n / (-j3\Omega) \approx 2.25\angle 9.79^\circ$ A.

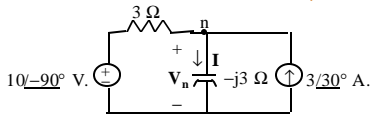
$$\therefore i(t) \approx 2.25\cos(3t + 9.79^\circ) \text{ A}.$$



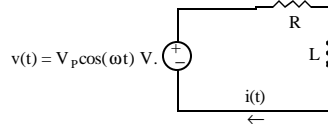5.6 Average Power, Reactive Power and Power Factor

What's the nature of power in AC steady-state circuits? Consider the following RL circuit ...


What's the circuit's *instantaneous* power $P(t)$?



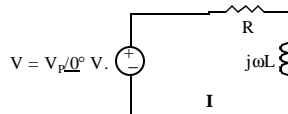5.6 Average Power, Reactive Power and Power Factor cont.

Applying KVL to the phasor circuit below yields the current's phasor from which $i(t)$ is deduced

Then the *instantaneous* power is $P(t) = v(t)i(t)$



$$\mathbf{I} = \frac{V_p \angle 0^\circ}{R + j\omega L} = \frac{V_p \angle 0^\circ}{Z \angle \theta} = \frac{V_p}{Z} \angle -\theta = I_p \angle -\theta \therefore i(t) = I_p \cos(\omega t - \theta) \text{ A}.$$

Where $Z = [R^2 + (\omega L)^2]^{1/2}$ and $\theta = \tan^{-1}(\omega L/R)$

5.6 Average Power, Reactive Power and Power Factor cont.

$$\begin{aligned} P(t) &= v(t)i(t) = V_p \cos(\omega t) I_p \cos(\omega t - \theta) \\ &= 0.5 V_p I_p [\cos(\theta) + \cos(2\omega t - \theta)] \\ &= 0.5 V_p I_p [\cos(\theta) + \cos(2\omega t)\cos(\theta) - \sin(2\omega t)\sin(\theta)] \\ &= 0.5 V_p I_p \cos(\theta) \{1 + \cos(2\omega t)\} + 0.5 V_p I_p \sin(\theta) \{-\sin(2\omega t)\} \end{aligned}$$

Recall from text p. 39 that $X_{\text{RMS}} = X_{\text{PEAK}}/\sqrt{2} \therefore$ since $2 = \sqrt{2}\sqrt{2}$

$$P(t) = V_{\text{RMS}} I_{\text{RMS}} \cos(\theta) \{1 + \cos(2\omega t)\} + V_{\text{RMS}} I_{\text{RMS}} \sin(\theta) \{-\sin(2\omega t)\}$$

$\therefore P(t) = P_f(t) + Q_f(t)$ Where ...

$P = V_{\text{RMS}} I_{\text{RMS}} \cos(\theta)$ and $Q = V_{\text{RMS}} I_{\text{RMS}} \sin(\theta)$ are *constants* and $f_p(t) = \{1 + \cos(2\omega t)\}$ and $f_q(t) = -\sin(2\omega t)$ are *time functions*

5.6 Average Power, Reactive Power and Power Factor cont.

What's the physical meaning of the plots shown below of each of the two terms in P(t)'s sum?

This waveform is never negative so its associated energy flows out of the source and does *not* return

Note double freq. $f_p(t) = P\{1 + \cos(2\omega t)\}$ Average = P

The energy associated with this waveform flows in and out of the source and its net value is zero

$f_q(t) = Q\{-\sin(2\omega t)\}$ Average = 0

N.B.: The average of $P(t) = P f_p(t) + Q f_q(t)$ is $P \therefore P$ is average power

8:45 PM Ohio University's Ross College of Engineering & Technology 37

5.6 Average Power, Reactive Power and Power Factor cont.

P and Q as sides of the *Power Triangle* and P and Q as the real and imaginary parts of *complex power S* (whose magnitude S is called *apparent power*)

$$S = P + jQ = V_{RMS} I_{RMS} \cos\theta + j V_{RMS} I_{RMS} \sin\theta$$

$$S = S e^{j\theta} = S \angle\theta = V_{RMS} I_{RMS} \angle\theta$$

N.B.: θ is called the *power factor angle* where the power factor is either $\cos(\theta)$ lag if $\theta > 0$, $\cos(\theta)$ lead if $\theta < 0$ or unity ($\theta = 0$)

8:45 PM Ohio University's Ross College of Engineering & Technology 38

5.6 Average Power, Reactive Power and Power Factor cont.

What's *complex power S* in terms of RMS voltage and current phasors

What are *RMS phasors*?

An *RMS phasor* is it's traditional (peak) phasor counterpart divided by $\sqrt{2}$ (see text p. 39)

Then *complex power S* = $V_{RMS} I_{RMS}^*$

Where $V_{RMS} = V/\sqrt{2}$ and $I_{RMS} = I/\sqrt{2}$

8:45 PM Ohio University's Ross College of Engineering & Technology 39

5.6 Average Power, Reactive Power and Power Factor cont.

Then since *complex power S* = $V_{RMS} I_{RMS}^*$ be sure to

Remember: Before making any power related calculations from phasors *always* convert traditional (peak) phasors to RMS phasors!!

8:45 PM Ohio University's Ross College of Engineering & Technology 40

5.6 Average Power, Reactive Power and Power Factor— some useful formulae

$$S_R = V_{RMS} I_{RMS}^* = (R I_{RMS}) I_{RMS}^* = V_{RMS} (V_{RMS}/R)^*$$

$$= R I_{RMS}^2 = V_{RMS}^2 / R = P_R + j0$$

$\therefore \text{Re}(S_R) = P_R \geq 0$ and $\text{Im}(S_R) = Q_R = 0$ for resistors

8:45 PM Ohio University's Ross College of Engineering & Technology 41

5.6 Average Power, Reactive Power and Power Factor— some useful formulae cont.


$$S_L = V_{RMS} I_{RMS}^* = (jX_L I_{RMS}) I_{RMS}^* = V_{RMS} [V_{RMS}/(jX_L)]^*$$

$$= jX_L I_{RMS}^2 = jV_{RMS}^2 / X_L = 0 + jQ_L$$

$\therefore \text{Re}(S_L) = P_L = 0$ and $\text{Im}(S_L) = Q_L \geq 0$ for inductors

8:45 PM Ohio University's Ross College of Engineering & Technology 42

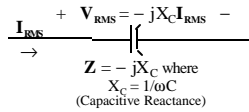5.6 Average Power, Reactive Power and Power Factor—
some useful formulae cont.




$$S_C = V_{RMS} I_{RMS}^*$$

$$= (-jX_C I_{RMS}) I_{RMS}^* = V_{RMS} (V_{RMS} / (-jX_C))^*$$

$$= -jX_C I_{RMS}^2 = -jV_{RMS}^2 / X_C = 0 + jQ_C$$

$$\therefore \text{Re}(S_C) = P_C = 0 \text{ and } \text{Im}(S_C) = Q_C \leq 0 \text{ for capacitors}$$

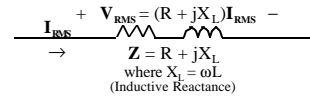5.6 Average Power, Reactive Power and Power Factor—
some useful formulae cont.




$$S = V_{RMS} I_{RMS}^*$$

$$= [(R + jX_L) I_{RMS}] I_{RMS}^* = (R + jX_L) I_{RMS}^2$$

$$= R I_{RMS}^2 + jX_L I_{RMS}^2 = P + jQ_L$$

$$\therefore P = R I_{RMS}^2 \text{ and } Q_L = X_L I_{RMS}^2 \text{ for this scenario}$$

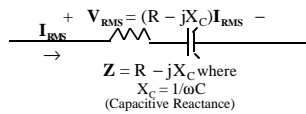5.6 Average Power, Reactive Power and Power Factor—
some useful formulae cont.




$$S = V_{RMS} I_{RMS}^*$$

$$= [(R - jX_C) I_{RMS}] I_{RMS}^* = (R - jX_C) I_{RMS}^2$$

$$= R I_{RMS}^2 + j(-X_C I_{RMS}^2) = P + jQ_C$$

$$\therefore P = R I_{RMS}^2 \text{ and } Q_C = -X_C I_{RMS}^2 \text{ for this scenario}$$

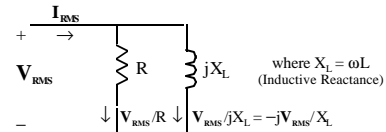5.6 Average Power, Reactive Power and Power Factor—
some useful formulae cont.




$$S = V_{RMS} I_{RMS}^*$$

$$= V_{RMS} (V_{RMS} / R - jV_{RMS} / X_L)^* = V_{RMS} (V_{RMS}^* / R + jV_{RMS}^* / X_L)$$

$$= V_{RMS}^2 / R + jV_{RMS}^2 / X_L = P + jQ_L$$

$$\therefore P = V_{RMS}^2 / R \text{ and } Q_L = V_{RMS}^2 / X_L \text{ for this scenario}$$

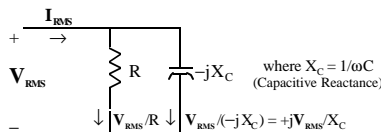5.6 Average Power, Reactive Power and Power Factor—
some useful formulae cont.



$$S = V_{RMS} I_{RMS}^*$$


$$= V_{RMS} (V_{RMS} / R + jV_{RMS} / X_C)^* = V_{RMS} (V_{RMS}^* / R - jV_{RMS}^* / X_C)$$

$$= V_{RMS}^2 / R + j(-V_{RMS}^2 / X_C) = P + jQ_C$$

$$\therefore P = V_{RMS}^2 / R \text{ and } Q_C = -V_{RMS}^2 / X_C \text{ for this scenario}$$

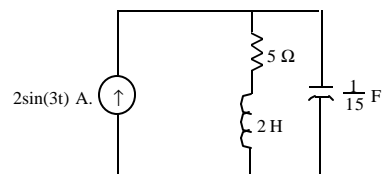5.6 Average Power, Reactive Power and Power Factor—**Example 5-2**


Calculate the complex power produced by the source and consumed by each passive element (see text problem 5.31, p. 205)



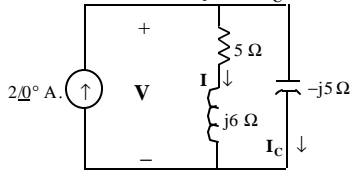5.6 Average Power, Reactive Power and Power Factor—Example 5-2 cont.


Phasor circuit: $\omega = 3 \text{ Rad./Sec.}$, $j\omega L = j3 \times 2 = j6 \Omega$, $-j(1/\omega C) = -j5 \Omega$, and the source phasor is $2\angle 0^\circ \text{ A}$.

By current \div , $\mathbf{I} = [-j5 \Omega / (5 \Omega + j6 \Omega - j5 \Omega)] 2\angle 0^\circ \text{ A}$. Ergo, $\mathbf{I} \approx 1.961\angle -101.3^\circ \text{ A}$. and by KCL, $\mathbf{I}_C = 2\angle 0^\circ \text{ A}$. $-\mathbf{I}$ Ergo $\mathbf{I}_C \approx 3.063\angle 38.89^\circ \text{ A}$. and $\mathbf{V} = -j5 \Omega \times \mathbf{I}_C \approx 15.32\angle -51.1^\circ \text{ V}$.



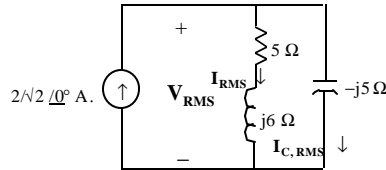5.6 Average Power, Reactive Power and Power Factor—Example 5-2 cont.

Dividing each current and voltage phasor by $\sqrt{2}$ yields the RMS phasors: $1.414\angle 0^\circ \text{ A}$. (source phasor), $\mathbf{I}_{\text{RMS}} \approx 1.387\angle -101.3^\circ \text{ A}$, $\mathbf{I}_{\text{C,RMS}} \approx 2.166\angle 38.89^\circ \text{ A}$ and $\mathbf{V}_{\text{RMS}} \approx 10.83\angle -51.1^\circ \text{ V}$.




5.6 Average Power, Reactive Power and Power Factor—Example 5-2 cont.

Then the source's complex power is $\mathbf{V}_{\text{RMS}} (1.414\angle 0^\circ \text{ A})^*$ $\approx 15.31\angle -51.1^\circ \text{ VA}$, $\approx 9.61 \text{ W} - j11.91 \text{ VAR}$

The complex power of the resistor, inductor and capacitor are respectively $(\mathbf{I}_{\text{RMS}})^2 R = (1.387 \text{ A})^2 (5\Omega) \approx 9.61 \text{ W}$, $j(\mathbf{I}_{\text{RMS}})^2 X_L = j(1.387 \text{ A})^2 (6\Omega) \approx j11.52 \text{ VAR}$ and $-j(\mathbf{V}_{\text{RMS}})^2 / X_C = -j(10.83 \text{ V})^2 / 5\Omega \approx -j23.46 \text{ VAR}$

Is complex power conserved here?

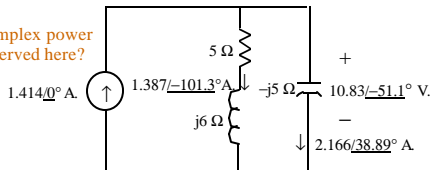


5.6 Average Power, Reactive Power and Power Factor Correction: An Application

$S = P/\cos(\theta) = 12 \text{ KW}/0.6 = 20 \text{ KVA} = \mathbf{V}_{\text{RMS}} \mathbf{I}_{\text{RMS}}$
 $\therefore \mathbf{I}_{\text{RMS}} = 20 \text{ KVA}/120 \text{ V} \approx 167 \text{ A. (RMS)}$

Ergo, Line losses $= \mathbf{P}_{\text{RMS}} R_{\text{Line}} \approx 2.78 \text{ KW}$
 $(\approx 23\% \text{ of load power})$

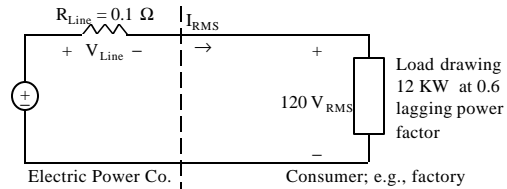
and $\mathbf{V}_{\text{Line}} = R_{\text{Line}} \mathbf{I}_{\text{RMS}} \approx 16.7 \text{ V} (\approx 14\% \text{ of load voltage})$



5.6 Average Power, Reactive Power and Power Factor Correction: An Application cont.

The load's complex power is $\mathbf{S}_{\text{Load}} = P + jQ$
 $= 12 \text{ KW} + j |S_{\text{Load}}| \sin(\theta) = 12 \text{ KW} + j20 \text{ KVA} \times 0.8$
 $= 12 \text{ KW} + j16 \text{ KVAR}$

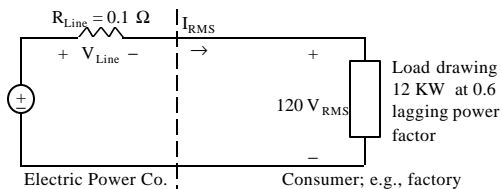Next, add $-j7 \text{ KVAR}$ of capacitance in parallel with the load to obtain ...




5.6 Average Power, Reactive Power and Power Factor Correction: An Application cont.

The net (load and capacitor) complex power is:

$\mathbf{S}_{\text{NET}} = \mathbf{S}_{\text{Load}} - j7 \text{ KVAR} = 12 \text{ KW} + j16 \text{ KVAR} - j7 \text{ KVAR}$
 $= 12 \text{ KW} + j9 \text{ KVAR} \approx 15\angle 36.87^\circ \text{ KVA}$

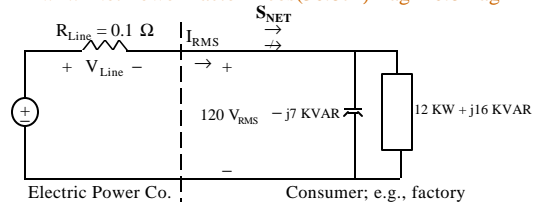N.B.: Net Power Factor $= \cos(36.87^\circ) \text{ Lag} = 0.8 \text{ Lag}$



5.6 Average Power, Reactive Power and Power Factor Correction: An Application cont.

Then $S_{NET} = 15 \text{ KVA} = V_{RMS} I_{RMS} = (120 \text{ V}_{RMS}) I_{RMS}$ yields $I_{RMS} = 15 \text{ KVA} / 120 \text{ V} = 125 \text{ A}$. (RMS) Ergo, ...

Line losses = $I_{RMS}^2 R_{Line} \approx 1.56 \text{ KW}$ ($\approx 13\%$ of load power) and $V_{Line} = R_{Line} I_{RMS} \approx 12.5 \text{ V}$ ($\approx 10.4\%$ of load voltage)

Who saves how much (annually) if electricity costs 10¢ per KWh?

Electric Power Co. | Consumer; e.g., factory

8:45 PM Ohio University's Ross College of Engineering & Technology 55

5.6 Average Power, Reactive Power and Power Factor Correction: An Application

Example 5-3

For the previous power factor correction application, what's the source's apparent power, power factor and voltage magnitude with and without the power factor correction?

Electric Power Co. | Consumer; e.g., factory

8:45 PM Ohio University's Ross College of Engineering & Technology 56

5.6 Average Power, Reactive Power and Power Factor Correction: An Application

Example 5-3 cont.

Without correction, the source produces $S_{Source} = S_{Load} + S_{Line} = (12 \text{ KW} + j16 \text{ KVAR}) + (2.78 \text{ KW} + j0 \text{ KVAR}) = 14.78 \text{ KW} + j16 \text{ KVAR} = 21.78 \angle 42.27^\circ \text{ KVA}$

\therefore the apparent power is 21.78 KVA and the power factor is $\cos(42.27^\circ)$ Lag = 0.74 Lag

Electric Power Co. | Consumer; e.g., factory

8:45 PM Ohio University's Ross College of Engineering & Technology 57

5.6 Average Power, Reactive Power and Power Factor Correction: An Application

Example 5-3 cont.

The current is $I_{RMS} = 167 \text{ A}$. and the apparent power ($V_{Source} \times I_{RMS}$) is 21.78 KVA

$\therefore V_{Source} = 21.78 \text{ KVA} / 167 \text{ A} = 130 \text{ V}$. (RMS)

Electric Power Co. | Consumer; e.g., factory

8:45 PM Ohio University's Ross College of Engineering & Technology 58

5.6 Average Power, Reactive Power and Power Factor Correction: An Application

Example 5-3 cont.

With correction, the source produces $S_{Source} = S_{Net} + S_{Line} = (12 \text{ KW} + j9 \text{ KVAR}) + (1.56 \text{ KW} + j0 \text{ KVAR}) = 13.56 \text{ KW} + j9 \text{ KVAR} = 16.27 \angle 33.57^\circ \text{ KVA}$

\therefore the apparent power is 16.27 KVA, the power factor is $\cos(33.57^\circ)$ Lag = 0.83 Lag and $I_{RMS} = 125 \text{ A}$. so that $V_{Source} = 16.27 \text{ KVA} / 125 \text{ A} = 130 \text{ V}$. (RMS)

Electric Power Co. | Consumer; e.g., factory

8:45 PM Ohio University's Ross College of Engineering & Technology 59

5.6 Average Power, Reactive Power and Power Factor Correction: An Application

Example 5-3 cont.

Summary

| PF Correction | Apparent Power ¹ | Power Factor ² | Source Voltage |
|---------------|-----------------------------|---------------------------|----------------|
| Without | 21.78 KVA | 0.74 Lag | 130 V. |
| With | 16.27 KVA | 0.83 Lag | 130 V. |

¹ Apparent power is germane to the source's size (rating) and therefore its capital cost

² The power factor indicates the percentage of the source's apparent power that is real power (83% versus 74%) and thus is a measure of the source's efficacy


8:45 PM Ohio University's Ross College of Engineering & Technology 60

5.6 Average Power, Reactive Power and Power Factor—Maximum Power Transfer

The steady-state AC version of the maximum power transfer theorem is similar to its DC counterpart (but the numbers are complex) and is shown below—see text pp. 183-185 for its (calculus) derivation


Note that both the (Thevenin) phasor circuit's voltage V_{Th} and impedance Z_{Th} are complex numbers

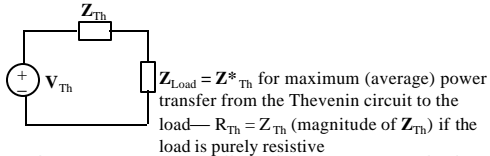The rules for obtaining the Thevenin circuit remain: $V_{Th} = V_{open\ circuit}$ and $Z_{Th} =$ circuit impedance remaining after all independent sources are deactivated




5.6 Average Power, Reactive Power and Power Factor—Maximum Power Transfer cont.

Example 5-4

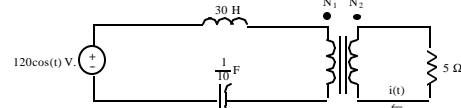


Calculate the turns ratio N_1/N_2 which will maximize the average power consumed by the resistor, the corresponding maximum average power and the resistor current $i(t)$

The phasor circuit is:

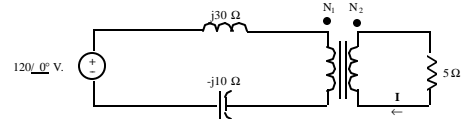


5.6 Average Power, Reactive Power and Power Factor—Maximum Power Transfer cont.

Example 5-4 cont.

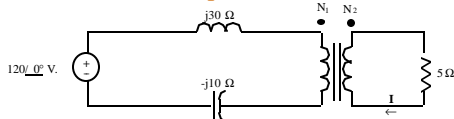


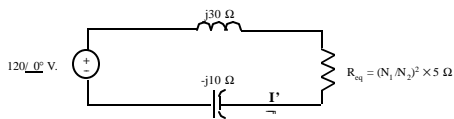Reflecting the resistor across the transformer yields:




5.6 Average Power, Reactive Power and Power Factor—Maximum Power Transfer cont.

Example 5-4 cont.

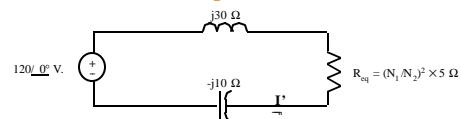


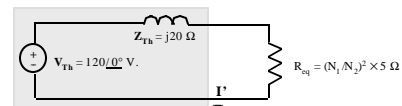Combining the two series reactances yields the (resistance-loaded) Thevenin circuit:



5.6 Average Power, Reactive Power and Power Factor—Maximum Power Transfer cont.

Example 5-4 cont.

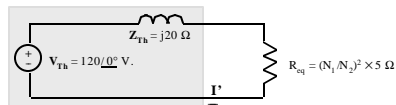


For maximum average power, $R_{eq} = (N_1/N_2)^2 \times 5 \Omega = |Z_{Th}| = 20 \Omega$

$$\therefore N_1/N_2 = 2$$

Then $I' = [V_{Th} = 120\angle 0^\circ \text{ V.}] / [Z_{Th} + R_{eq}] = 3\sqrt{2} \angle -45^\circ \text{ A.}$

5.6 Average Power, Reactive Power and Power Factor—Maximum Power Transfer cont.

Example 5-4 cont.

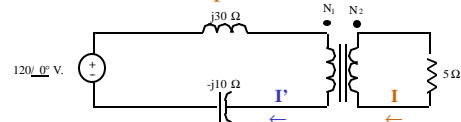

As a result of the transformer's turns ratio, $I = (N_1/N_2) I'$
 $\therefore I = (N_1/N_2) I' = 2 \times 3\sqrt{2} \angle -45^\circ \text{ A.} = (6\sqrt{2}) \angle -45^\circ \text{ A.}$ so that

$i(t) = (6\sqrt{2}) \cos(t - 45^\circ) \text{ A.} \Rightarrow 8.485 \cos(t - 45^\circ) \text{ A.}$
 and $I_{RMS} = |I|/\sqrt{2} = 6 \text{ A.}$ so that $P_{ave., max.} = (I_{RMS})^2 \times 5 \Omega$ yields:

$$P_{ave., max.} = 180 \text{ W.}$$

5.7 Frequency Response of Circuits

Time-domain signals have a frequency-domain counterpart; e.g., music is a time varying sound signal with, inter alia, bass, mid-range and treble characteristics (components)

The concomitant mathematical relationships were discovered in 1822 by Jean Baptiste Joseph Fourier (1768-1830)

See text equation 5.129 (p. 185) and its accompanying Figure 5.20 (p. 186) = next slide, as well as text Appendix C (p. 753)

Signals of all sorts (e.g., sound) can be converted to electrical signals (voltage and current waveforms) via transducers

Electrical signals can be “processed” by electric circuits because electric circuit behavior is frequency dependent

5.7 Frequency Response of Circuits cont.


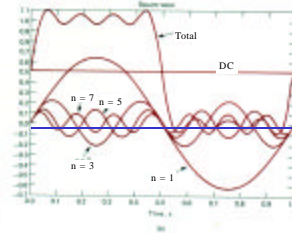


FIGURE 5.20
Convergence of
Fourier series
components to
half-waveform by
superposition


5.7 Frequency Response of Circuits cont.

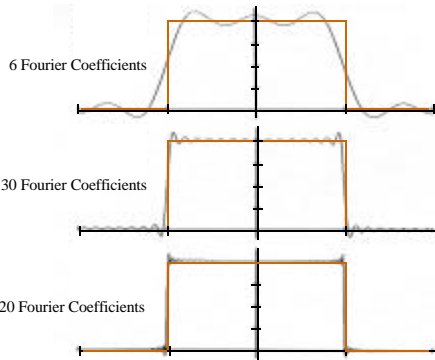

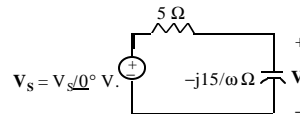5.7 Frequency Response of Circuits cont.

Consider the circuit of text Figure P5.39 (p. 207) whose phasor circuit is shown below

Voltage division produces the ratio (*transfer function*) $\mathbf{H}(j\omega) = \mathbf{V}/\mathbf{V}_s = (-j15/\omega)/(5 - j15/\omega) = 1/(1 + j\omega/3)$ which in this case is *gain* (i.e., what are \mathbf{H} 's units?)



5.7 Frequency Response of Circuits cont.

This *transfer function* can be written in polar form as $\mathbf{H}(j\omega) = M(\omega)/\theta(\omega)$ where:

$$M(\omega) = \{1/[1 + (\omega/3)^2]\}^{1/2} \text{ and } \theta(\omega) = -\tan^{-1}(\omega/3)$$

So both the gain's magnitude and phase angle depend on frequency; i.e., $M(0) = 1$ (which is also the M 's maximum) and $\theta(0) = 0^\circ$ whereas $\text{Lim}[M(\omega)]$ and $\text{Lim}[\theta(\omega)]$ as $\omega \rightarrow \infty$ are 0 and -90° respectively

Also, for $(\omega/3) \gg 1$, $M(\omega) \approx 3/\omega$

What's $M(\omega)$ and $\theta(\omega)$ when $\omega = 3$ Rad./Sec.?

5.7 Frequency Response of Circuits cont.

$M(3) = \{1/[1 + (3/3)^2]\}^{1/2} = 1/\sqrt{2}$ and $\theta(3) = -45^\circ$ which is the transfer function's *half-power point* Why the moniker *half-power point*?


Suppose $\mathbf{V}_s = V_s \angle 0^\circ$ V. for all frequencies (i.e., all ω) Then the maximum output voltage $V_{\text{max}} = V_s$ occurs at $\omega = 0$ since $V = M(\omega)V_s$ and $M_{\text{max}} = M(0) = 1$

Impressing this voltage across a load resistor yields the maximum output power $P_{\text{max}} = V_s^2/R_L$

The output voltage at $\omega = 3$ Rad./Sec. is $M(3)V_s = V_s/\sqrt{2}$ and the corresponding power is $(V_s/\sqrt{2})^2/R_L = [V_s^2/R_L]/2 = P_{\text{max}}/2$ (*half of P_{max}*)


5.7 Frequency Response of Circuits cont.

A plot of $M(\omega)$ is shown below

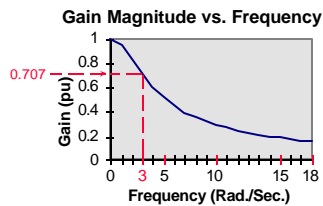

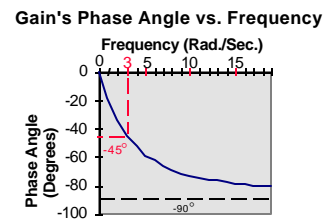
5.7 Frequency Response of Circuits cont.

A plot of $\theta(\omega)$ is shown below



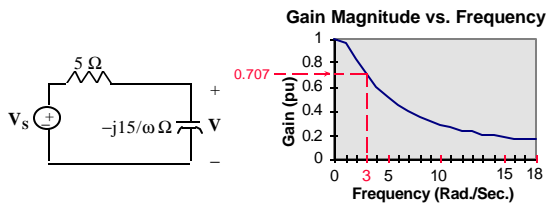5.7.2 Filters

The RC circuit just considered is a *low-pass filter* because the magnitude of its gain $M(\omega)$ favors lower frequencies




Transfer function's gain magnitude = $|H(j\omega)| = |V/V_S| = V/V_S = M(\omega)$
 N.B.: If the capacitor's voltage favors low frequencies, one can intuit that the resistor's voltage favors high frequencies (why?)

5.7.2 Filters cont.


Other types of filters are possible and are developed in text section 5.7.2 (pp. 190-200) using the generic prototype shown below

The *results* for each filter are ...

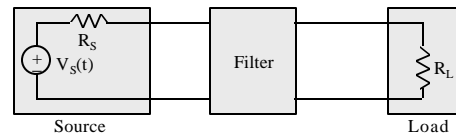

5.7.2 Filters cont.

Low-pass filter

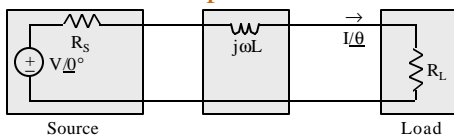

$$H(j\omega) = \frac{I/\theta}{V/0^\circ} = \frac{V/0^\circ}{(R_S + R_L + j\omega L)} \cdot \frac{1}{V/0^\circ}$$



for which

$$M(\omega) = \frac{1}{R_S + R_L} \cdot \frac{1}{(1 + [\omega L / (R_S + R_L)]^2)^{1/2}}$$

Which has a cut-off (half-power) frequency of $\omega_c = (R_S + R_L)/L$


5.7.2 Filters cont.

Low-pass filter

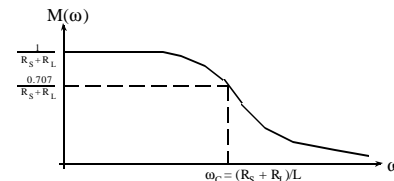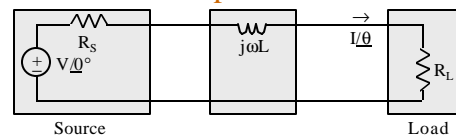

5.7.2 Filters cont.

High-pass filter

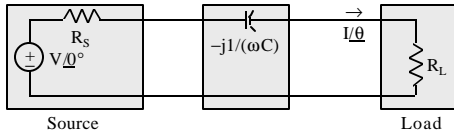

$$\mathbf{H}(j\omega) = \mathbf{I}\theta / \mathbf{V}\angle 0^\circ = \{ \mathbf{V}\angle 0^\circ / [R_S + R_L - j(1/\omega C)] \} / \mathbf{V}\angle 0^\circ$$



for which

$$M(\omega) = \frac{1}{R_S + R_L} \cdot \frac{1}{\{1 + [1/(\omega C(R_S + R_L))]^2\}^{1/2}}$$

Which has a cut-off (half-power) frequency of $\omega_c = 1/[C(R_S + R_L)]$


5.7.2 Filters cont.

High-pass filter

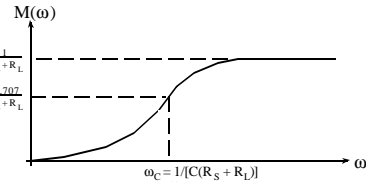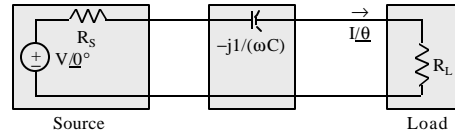

5.7.2 Filters cont.

Band-pass filter

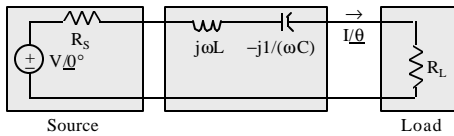


$$\mathbf{H}(j\omega) = \mathbf{I}\theta / \mathbf{V}\angle 0^\circ = \{ \mathbf{V}\angle 0^\circ / [R_S + R_L + j\omega L - j(1/\omega C)] \} / \mathbf{V}\angle 0^\circ$$

for which

$$M(\omega) = \frac{1}{R_S + R_L} \cdot \frac{1}{\{1 + \{[1 - \omega^2 LC] / [\omega C(R_S + R_L)]\}^2\}^{1/2}}$$


5.7.2 Filters cont.

Band-pass filter

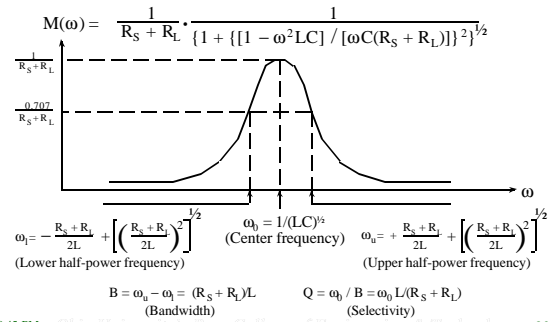

5.7.2 Filters cont.

Band-reject filter

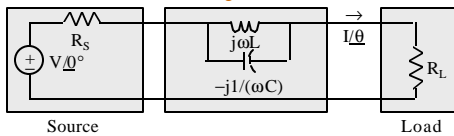


$$\mathbf{H}(j\omega) = \mathbf{I}\theta / \mathbf{V}\angle 0^\circ = \mathbf{V}\angle 0^\circ / [R_S + R_L + (j\omega L) \parallel (-j(1/\omega C))]$$

for which

$$M(\omega) = \frac{1}{R_S + R_L} \cdot \frac{1}{\{1 + \{[\omega L / (R_S + R_L)] / [1 - \omega^2 LC]\}^2\}^{1/2}}$$


5.7.2 Filters cont.

Band-reject filter

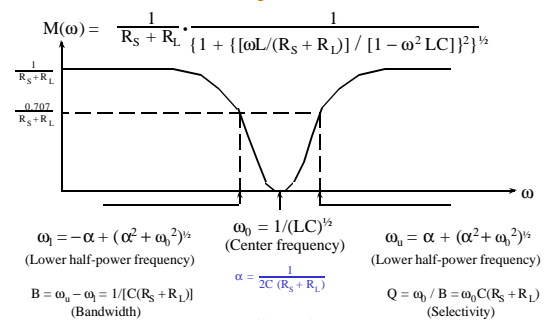

5.7.2 Filters cont.

Example 5-5

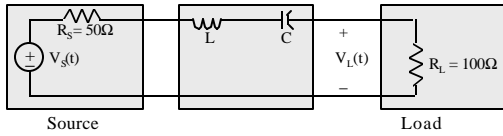

Design the band-pass filter to have a center frequency of 1 MHz. and a bandwidth of 10 kHz. What's this filter's Q?

$$\omega_0 = 2\pi f_0 = 2\pi \times 10^6 \text{ Rad./Sec.} = 1/(LC)^{1/2} = (\text{Center frequency})$$

$$B = 2\pi f_{BW} = 2\pi \times 10^4 \text{ Rad./Sec.} = (R_S + R_L)/L = 150 \Omega/L \text{ (Bandwidth)}$$

$$\therefore L = 150 \Omega / (2\pi \times 10^4 \text{ Rad./Sec.}) \approx 2.39 \text{ mH}$$

$$\text{and } C = 1 / (\omega_0^2 L) \approx 1 / [(2\pi \times 10^6 \text{ Rad./Sec.})^2 \times 2.39 \text{ mH}] \approx 10.6 \text{ pF}$$

$$\text{and } Q = \omega_0 / B = (2\pi \times 10^6 \text{ Rad./Sec.}) / (2\pi \times 10^4 \text{ Rad./Sec.}) = 100$$

8:45 PM Ohio University's Russ College of Engineering & Technology 85

We welcome your
questions with
Enthusiasm!!



School of Electrical Engineering
and
Computer Science



Russ College of Engineering & Technology