

**Microsoft PowerPoint[®] Presentation Graphics for
EE 315: Basic Electrical Engineering III**

Prepared by Brian Manhire, Ph.D.
Professor of Electrical Engineering



*Stocker Center, home of Ohio University's
Russ College of Engineering & Technology*


Microsoft PowerPoint[®] Presentation Graphics
© Copyright 1998 Brian Manhire

For Part 3 of


**Introduction to Electrical
Engineering, 2/e**

**by C.R. Paul, S.A. Nasar
and L.E. Unnewehr**

© 1992, McGraw-Hill, Inc.

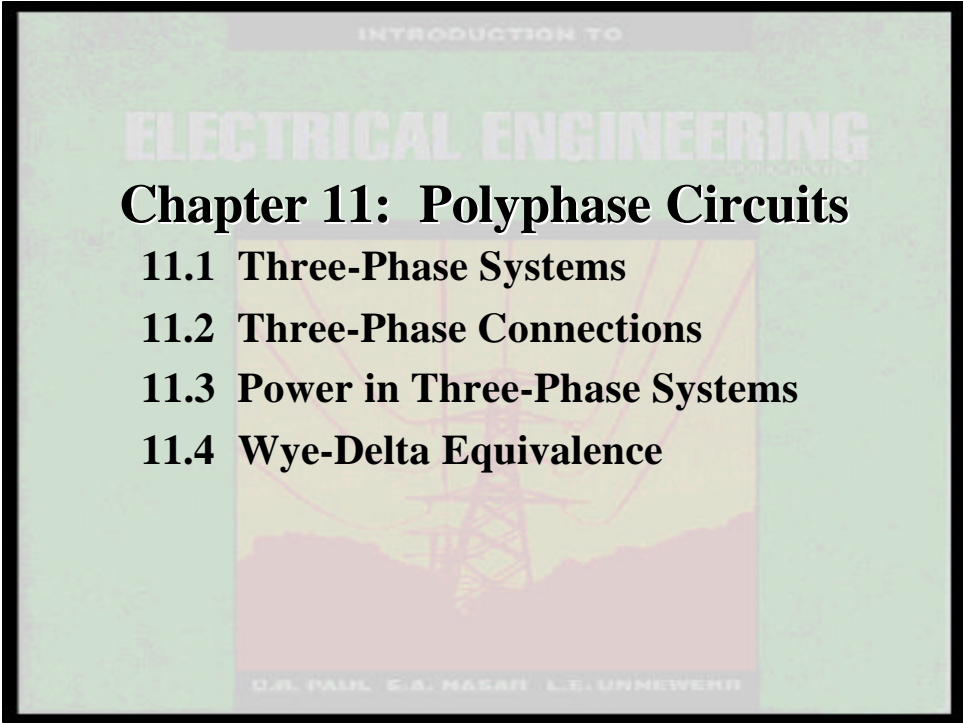

Section 11.1: Three-Phase Systems

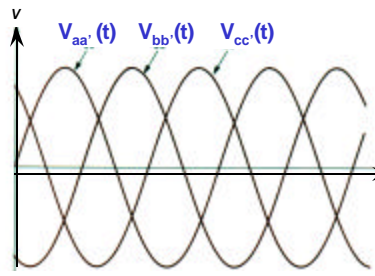

Balanced set of 3 voltages, i.e.;


$$V_{aa'}(t) + V_{bb'}(t) + V_{cc'}(t) = 0, \text{ where:}$$

$$V_{aa'}(t) = V_m \sin(\omega t)$$

$$V_{bb'}(t) = V_m \sin(\omega t - 120^\circ)$$

$$V_{cc'}(t) = V_m \sin(\omega t - 240^\circ)$$

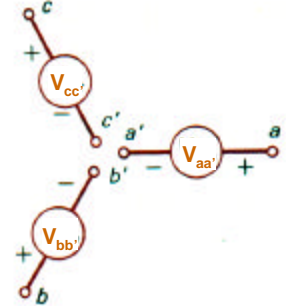Note the **positive** (phase) **sequence** (abc) of the voltage maxima





Voltage Phasors

$$V_{cc'} = V \angle -240^\circ = V \angle +120^\circ \Rightarrow V(-0.5 + j0.866)$$

$$V_{aa'} = V \angle 0^\circ = V(1 + j0)$$

$$V_{bb'} = V \angle -120^\circ \Rightarrow V(-0.5 - j0.866)$$

Section 11.2: Three-Phase Connections

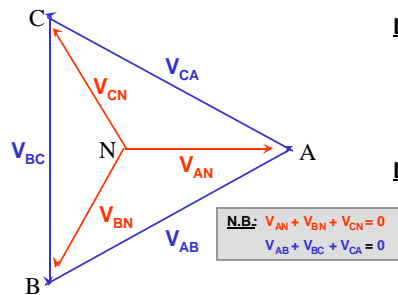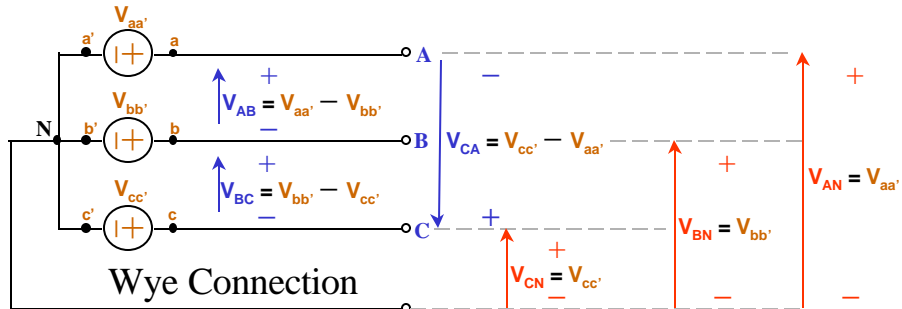

Line-to-Neutral Voltages = Phase Voltages

$$V_{AN} = V_{aa'} = V\angle 0^\circ = V(1 + j0)$$

$$V_{BN} = V_{bb'} = V\angle -120^\circ \Rightarrow V(-0.5 - j0.866)$$

$$V_{CN} = V_{cc'} = V\angle -240^\circ = V\angle +120^\circ \Rightarrow V(-0.5 + j0.866)$$


Line-to-Line Voltages:

$$V_{AB} = \sqrt{3}V\angle +30^\circ \Rightarrow \sqrt{3}V(+0.866 + j0.5)$$

$$V_{BC} = \sqrt{3}V\angle -90^\circ \Rightarrow \sqrt{3}V(0.0 - j1.0)$$

$$V_{CA} = \sqrt{3}V\angle +150^\circ \Rightarrow \sqrt{3}V(-0.866 + j0.5)$$

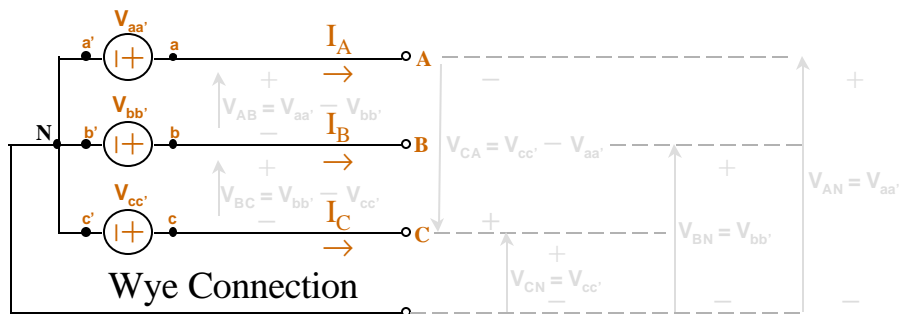Section 11.2: Three-Phase Connections cont.



Line Currents I_A , I_B and I_C
= Phase (Source) Currents

Line-to-Neutral Voltages = Phase Voltages

$$V_{AN} = V_{aa'} = V\angle 0^\circ = V(1 + j0)$$

$$V_{BN} = V_{bb'} = V\angle -120^\circ \Rightarrow V(-0.5 - j0.866)$$

$$V_{CN} = V_{cc'} = V\angle -240^\circ = V\angle +120^\circ \Rightarrow V(-0.5 + j0.866)$$



Line-to-Line Voltages:

$$V_{AB} = \sqrt{3}V\angle +30^\circ \Rightarrow \sqrt{3}V(+0.866 + j0.5)$$

$$V_{BC} = \sqrt{3}V\angle -90^\circ \Rightarrow \sqrt{3}V(+0.0 - j1.0)$$

$$V_{CA} = \sqrt{3}V\angle +150^\circ \Rightarrow \sqrt{3}V(-0.866 + j0.5)$$

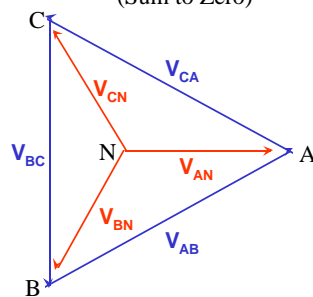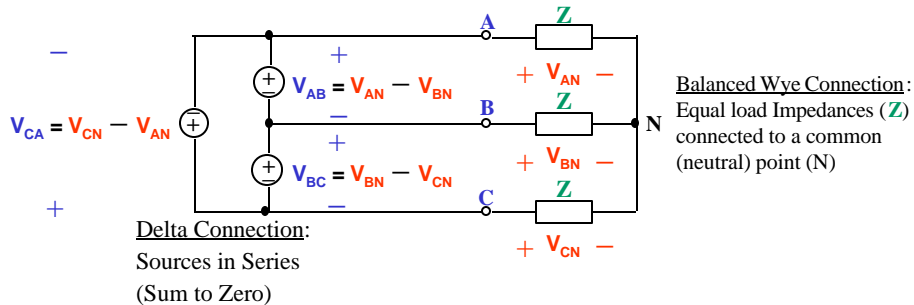Section 11.2: Three-Phase Connections cont.



Line-to-Line Voltages:

$$V_{AB} = \sqrt{3}V\angle 30^\circ \Rightarrow \sqrt{3}V(+0.866 - j0.5)$$

$$V_{BC} = \sqrt{3}V\angle -90^\circ \Rightarrow \sqrt{3}V(+0.0 - j1.0)$$

$$V_{CA} = \sqrt{3}V\angle 150^\circ \Rightarrow \sqrt{3}V(-0.866 + j0.5)$$


Line-to-Neutral Voltages = Phase Voltages

$$V_{AN} = V\angle 0^\circ = V(1 + j0)$$

$$V_{BN} = V\angle -120^\circ \Rightarrow V(-0.5 - j0.866)$$

$$V_{CN} = V\angle -240^\circ = V\angle 120^\circ \Rightarrow V(-0.5 + j0.866)$$

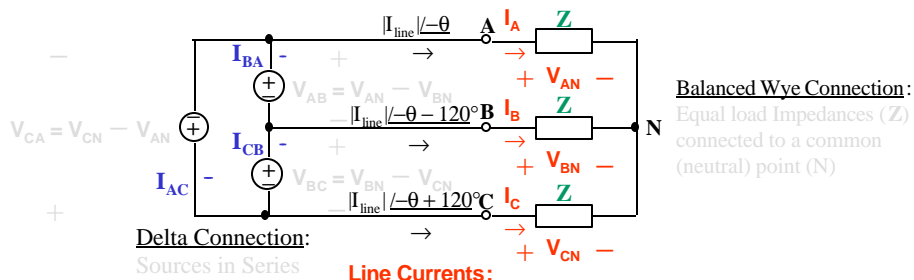Section 11.2: Three-Phase Connections cont.



Line Currents:

$$I_A = V_{AN}/Z = |V_{AN}\angle 0^\circ|/|Z|\angle \theta = |I_{line}|\angle -\theta \quad (= I_{BA} - I_{AC})$$

$$I_B = V_{BN}/Z = |V_{BN}\angle -120^\circ|/|Z|\angle \theta = |I_{line}|\angle -\theta - 120^\circ \quad (= I_{CB} - I_{BA})$$


$$I_C = V_{CN}/Z = |V_{CN}\angle +120^\circ|/|Z|\angle \theta = |I_{line}|\angle -\theta + 120^\circ \quad (= I_{AC} - I_{CB})$$

Delta's Phase Currents:

$$I_{BA} = (|I_{line}|/\sqrt{3})\angle -\theta + 30^\circ, I_{CB} = (|I_{line}|/\sqrt{3})\angle -\theta - 90^\circ \text{ and } I_{AC} = (|I_{line}|/\sqrt{3})\angle -\theta + 150^\circ$$

Where: $I_A + I_B + I_C = 0$ and $I_{BA} + I_{CB} + I_{AC} = 0$ (i.e., both sets of three-phase currents are balanced.)

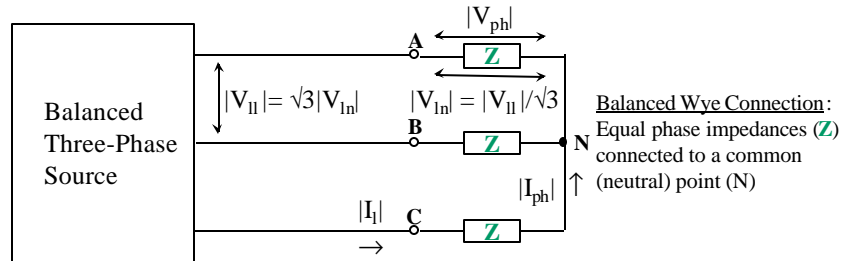Section 11.2: Three-Phase Connections cont.



Balanced-Wye Voltage and Current Magnitude Relationships


$$|I_l| = \text{line current magnitude} = \text{phase current magnitude} = |I_{ph}|$$

$$|V_{II}| = \sqrt{3}|V_{In}| \quad (= \sqrt{3}|V_{ph}|)$$

Three-Phase Apparent Power

$$|S_{3ph}| = 3|S_{ph}| = 3|V_{ph}||I_{ph}| = 3|V_{In}||I_l| = 3(|V_{II}|/\sqrt{3})|I_l| = \sqrt{3}|V_{II}||I_l|$$

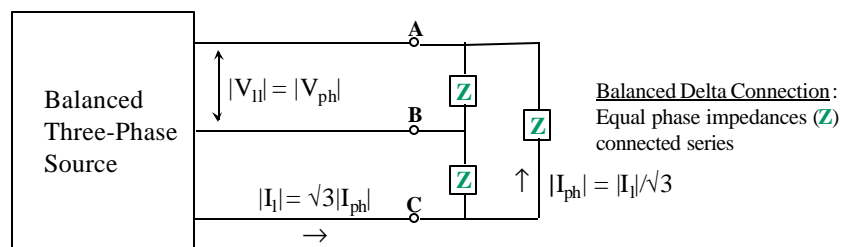Section 11.2: Three-Phase Connections cont.



Balanced-Delta Voltage and Current Magnitude Relationships

$$|V_{II}| = \text{line-to-line voltage magnitude} = \text{phase voltage magnitude} = |V_{ph}|$$

$$|I_l| = \sqrt{3}|I_{ph}|$$

Balanced Three-Phase Apparent Power

$$|S_{3ph}| = 3|S_{ph}| = 3|V_{ph}||I_{ph}| = 3|V_{II}||I_{ph}| = 3|V_{II}|(|I_l|/\sqrt{3}) = \sqrt{3}|V_{II}||I_l|$$

(Same as Wye result)

Section 11.3: Power in Three-Phase Systems

As demonstrated in text section 11.3 (p. 461, equation 11.18), in balanced three-phase systems, the total three-phase instantaneous power is *constant*.

This is analogous to the total power output of an automobile's multi-cylinder ICE (i.e., what would happen if all cylinders fired at the same time?)

Complex Power

$$S_{3ph} = 3S_{ph} = 3V_{ph}(I_{ph})^* = 3|V_{ph}||I_{ph}|(\cos\theta + j\sin\theta)$$

where θ is the power factor angle (e.g., Z 's angle)

But $3|V_{ph}||I_{ph}|$ is the three-phase apparent power $|S_{3ph}| = \sqrt{3}|V_{ll}||I_l|$

$$\text{Ergo, } S_{3ph} = \sqrt{3}|V_{ll}||I_l|(\cos\theta + j\sin\theta) = P_{3ph} + jQ_{3ph}$$


$$\therefore P_{3ph} = |S_{3ph}|\cos\theta = \sqrt{3}|V_{ll}||I_l|\cos\theta \quad \text{and}$$

$$Q_{3ph} = |S_{3ph}|\sin\theta = \sqrt{3}|V_{ll}||I_l|\sin\theta$$

12:18 PM Ohio University's Russ College of Engineering & Technology 11

Section 11.3: Power in Three-Phase Systems cont.

Example 11.1 (p. 462)

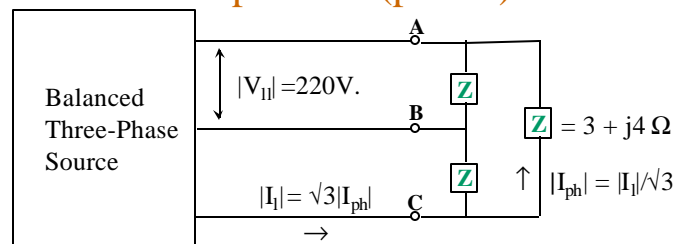

Calculate the magnitude of the line current and the total three-phase *complex* power supplied to the load.

$$|I_{ph}| = |V_{ll}| / |Z| = 220 \text{ V.} / |3 + j4| \Omega = 220 \text{ V.} / 5 \Omega = 44 \text{ A.}$$

$$|I_l| = \sqrt{3}|I_{ph}| = \sqrt{3} \times 44 \text{ A.} \approx \underline{76.21 \text{ A.}} \quad (\text{answer})$$

$$Z = 3 + j4 \Omega \approx 5 / \underline{53.13^\circ} \Omega \quad \therefore \theta \approx 53.13^\circ \quad \text{so that ...}$$


$$S_{3ph} = \sqrt{3}|V_{ll}||I_l|(\cos\theta + j\sin\theta) = \sqrt{3} \times 220 \text{ V.} \times 76.21 \text{ A.} \times (0.6 + j0.8)$$

$$S_{3ph} \approx \underline{17.4 \text{ KW} + j23.2 \text{ KVAR}} \quad (\text{answer}) \approx 29 / \underline{53.13^\circ} \text{ KVA}$$

12:18 PM Ohio University's Russ College of Engineering & Technology 12

Section 11.3: Power in Three-Phase Systems cont.

Example 11.2 (pp. 462-463)

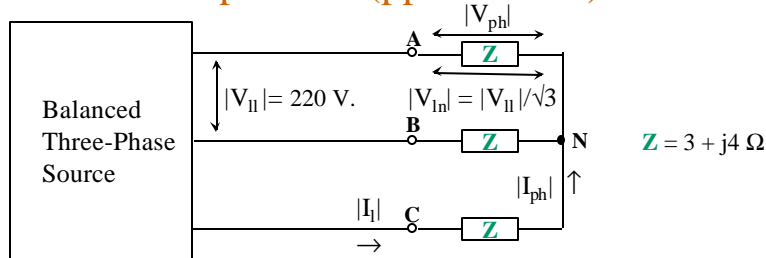

Calculate the magnitude of the phase voltage and the total three-phase *complex* power supplied to the load.

$$|V_{ph}| = |V_{ln}| = |V_{II}|/\sqrt{3} = 220 \text{ V.} / \sqrt{3} \approx \underline{127 \text{ V.}} \text{ (answer)}$$

$$\mathbf{Z} = 3 + j4 \Omega \approx \underline{5/53.13^\circ \Omega} \quad \therefore \theta \approx 53.13^\circ \text{ so that ...}$$


$$|I_1| = |I_{ph}| = |V_{ln}|/|Z| \approx 127 \text{ V.} / 5 \Omega \approx 25.4 \text{ A. so that ...}$$

$$S_{3ph} = \sqrt{3}|V_{II}||I_1|(\cos\theta + j\sin\theta) = \sqrt{3} \times 220 \text{ V.} \times 25.4 \text{ A.} \times (0.6 + j0.8)$$

$$S_{3ph} \approx \underline{5.81 \text{ KW} + j7.74 \text{ KVAR}} \text{ (answer)} \approx \underline{9.68/53.13^\circ \text{ KVA}}$$

Section 11.3: Power in Three-Phase Systems cont.

Example 11.3 (pp. 463-464)

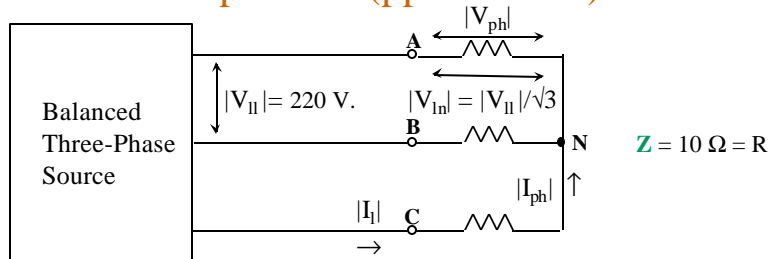

Calculate the total three-phase power supplied to the load.

$$|V_{ph}| = |V_{ln}| = |V_{II}|/\sqrt{3} = 220 \text{ V.} / \sqrt{3} \approx 127 \text{ V.}$$

$$\mathbf{Z} = 10 + j0 \Omega = \underline{10/0^\circ \Omega} \quad \therefore \theta = 0^\circ \text{ so that ...}$$


$$|I_1| = |I_{ph}| = |V_{ln}|/|Z| \approx 127 \text{ V.} / 10 \Omega \approx 12.7 \text{ A. so that ...}$$

$$S_{3ph} = \sqrt{3}|V_{II}||I_1|(\cos\theta + j\sin\theta) = \sqrt{3} \times 220 \text{ V.} \times 12.7 \text{ A.} \times (1 + j0)$$

$$S_{3ph} \approx \underline{4.84 \text{ KW} + j0 \text{ KVAR}} \quad \therefore P_{3ph} \approx \underline{4.84 \text{ KW}} \text{ (answer)}$$

Section 11.3: Power in Three-Phase Systems cont.

Example 11.3 (pp. 463-464) cont.

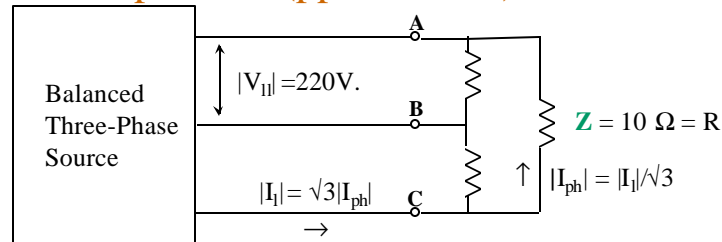

Calculate the total three-phase power supplied to the load.

$$|I_{ph}| = |V_{II}| / |Z| = 220\text{ V.} / 10\ \Omega = 220\text{ V.} / 10\ \Omega = 22\text{ A.}$$

$$|I_1| = \sqrt{3}|I_{ph}| = \sqrt{3} \times 22\text{ A.} \approx \underline{38.12\text{ A.}} \text{ (answer)}$$

$$Z = 10 + j0\ \Omega = 10\angle 0^\circ\ \Omega \quad \therefore \theta \approx 0^\circ \text{ so that ...}$$


$$S_{3ph} = \sqrt{3}|V_{II}||I_1|(\cos\theta + j\sin\theta) = \sqrt{3} \times 220\text{ V.} \times 38.12\text{ A.} \times (1 + j0)$$

$$S_{3ph} \approx 14.52\text{ KW} + j0\text{ KVAR} \quad \therefore P_{3ph} \approx \underline{14.52\text{ KW}} \text{ (answer)}$$

12:18 PM Ohio University's Russ College of Engineering & Technology 15

Section 11.3: Power in Three-Phase Systems cont.

Example 11.4 (p. 464)

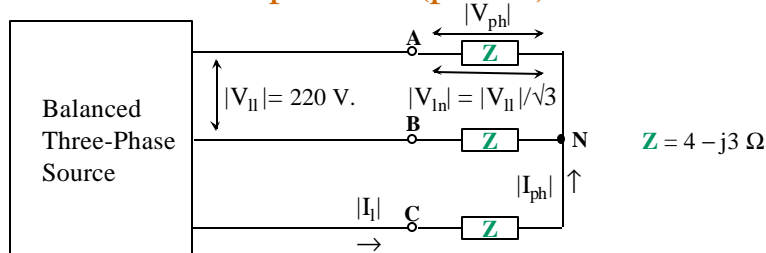

Calculate the line-to neutral voltage phasors, the line-to-line voltage phasors, the line current phasors and the load's three-phase complex power given V_{AN} is the reference phasor and the phase sequence is abc.

$$V_{AN} = (220\text{ V.}/\sqrt{3})\angle 0^\circ \approx 127\angle 0^\circ\text{ V. (Ref. Phasor)} \quad \therefore V_{BN} = 127\angle -120^\circ\text{ V.}$$

$$\text{and } V_{CN} = 127\angle +120^\circ\text{ V. (for abc sequence) and from the voltage "triangle,"}$$

$$V_{AB} = 220\angle +30^\circ\text{ V.}, V_{BC} = 220\angle -90^\circ\text{ V.} \text{ and } V_{CA} = 220\angle +150^\circ\text{ V.}$$


$$\text{The line-current phasors are } I_A = V_{AN}/Z = 127\angle 0^\circ\text{ V.}/(4 - j3)\ \Omega \text{ or}$$

$$I_A = 127\angle 0^\circ\text{ V.}/5\angle -36.87^\circ\ \Omega \approx 25.4\angle +36.87^\circ\text{ A.} \quad \text{Similarly ...}$$

$$I_B = 25.4\angle +83.13^\circ\text{ A.} \text{ and } I_C = 25.4\angle +156.87^\circ\text{ A.}$$

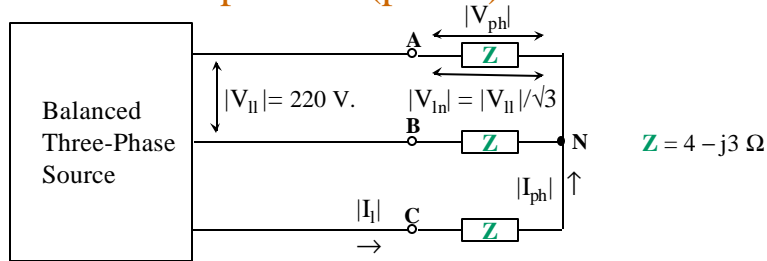12:18 PM Ohio University's Russ College of Engineering & Technology 16

Section 11.3: Power in Three-Phase Systems cont.
Example 11.4 (p. 464) cont.




The load's three-phase complex power is:

$$S_{3ph} = \sqrt{3}|V_{11}||I_l|(\cos\theta + j\sin\theta) = \sqrt{3} \times 220 \text{ V} \times 25.4 \text{ A} \times (0.8 - j0.6)$$

$$S_{3ph} \approx \underline{7.74 \text{ KW} - j5.81 \text{ KVAR}} \text{ (answer)} \approx 9.68 \angle -36.87^\circ \text{ KVA}$$

Section 11.4 Wye-Delta Equivalence

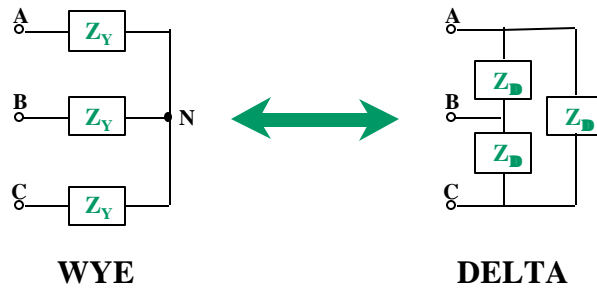


$$Z_D = 3Z_Y$$

(See text p. 465 for derivation)

Section 11.4 Wye-Delta Equivalence cont.


Example 11.5 (p. 466)

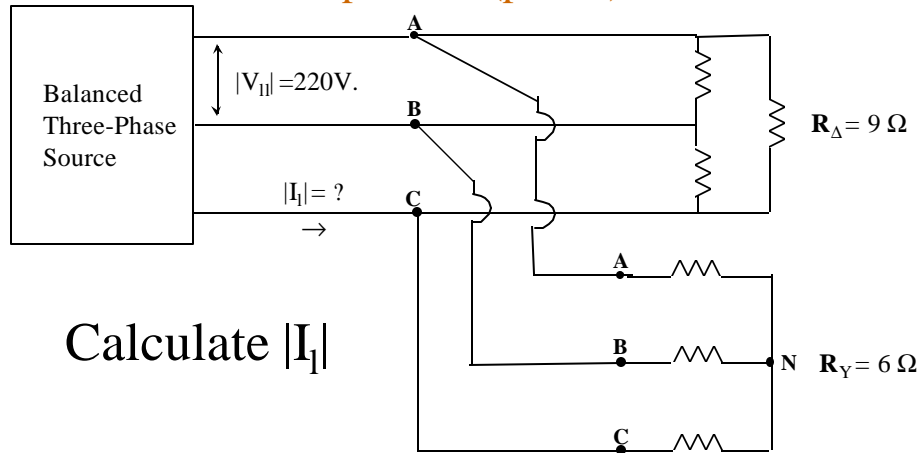

12:18 PM Ohio University's Russ College of Engineering & Technology 19

Section 11.4 Wye-Delta Equivalence cont.

Example 11.5 (p. 466) cont.

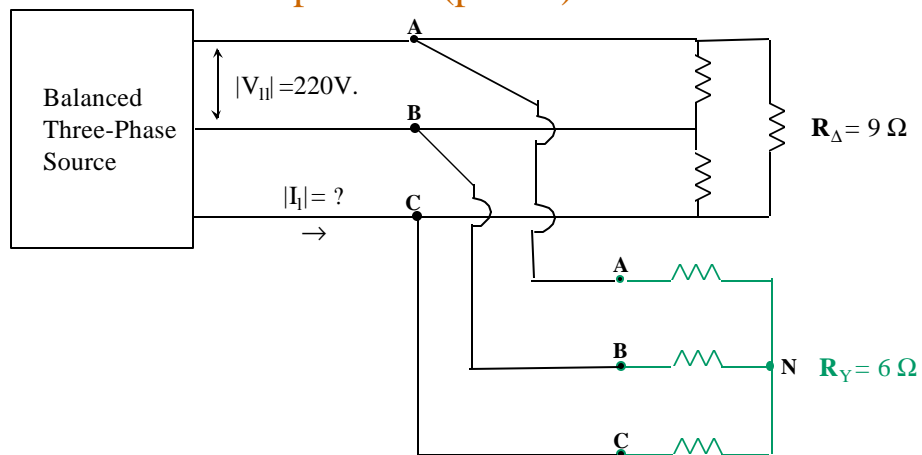


Step 1: Convert $R_Y = 6\ \Omega$ to its equivalent delta:

$$r_{\Delta} = 3R_Y = 18\ \Omega$$

12:18 PM Ohio University's Russ College of Engineering & Technology 20

Section 11.4 Wye-Delta Equivalence cont.

Example 11.5 (p. 466) cont.

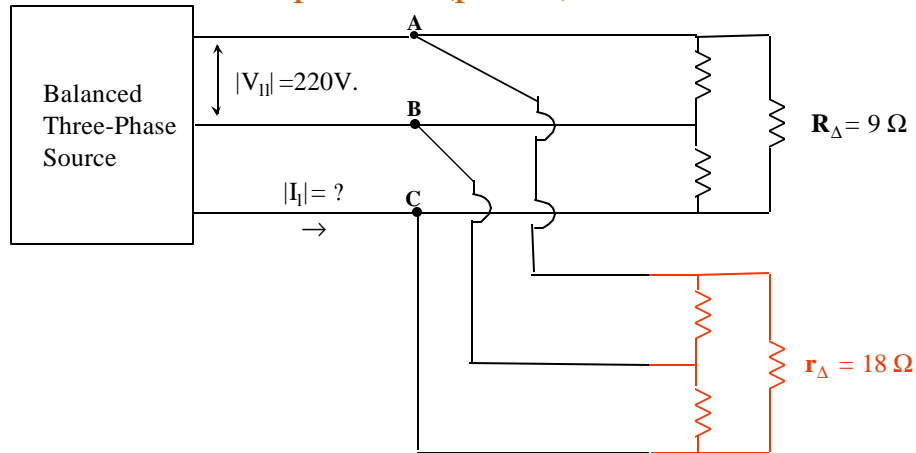


Step 2: Combine parallel (delta) resistors:

$$R_{\text{net}} = R_{\Delta} \parallel r_{\Delta} = 6\ \Omega$$

Section 11.4 Wye-Delta Equivalence cont.

Example 11.5 (p. 466) cont.

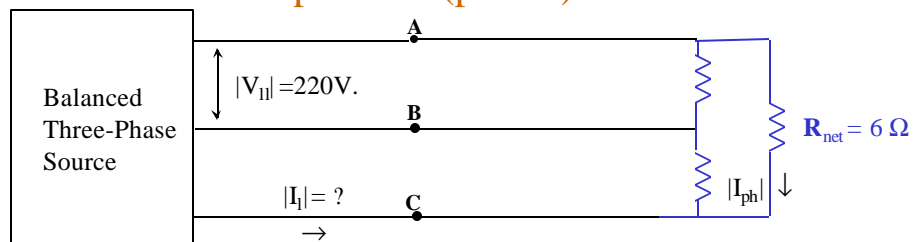


Step 3: $|I_{\text{ph}}| = |V_{II}|/R_{\text{net}} = 220\ \text{V}/6\ \Omega \approx 36.67\ \text{A}$.

$\therefore |I_l| = \sqrt{3}|I_{\text{ph}}| \approx 63.51\ \text{A}$.

(See text pp. 466-467 for an alternate approach)

Section 11.4 Wye-Delta Equivalence cont.


Example 11.6 (p. 467)

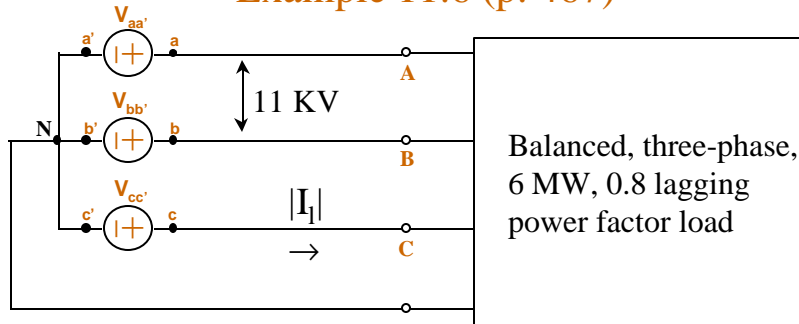

Find the total reactive power drawn by the load and the magnitude of the generator's line current ($|I_l|$)

Section 11.4 Wye-Delta Equivalence cont.

Example 11.6 (p. 467) cont.

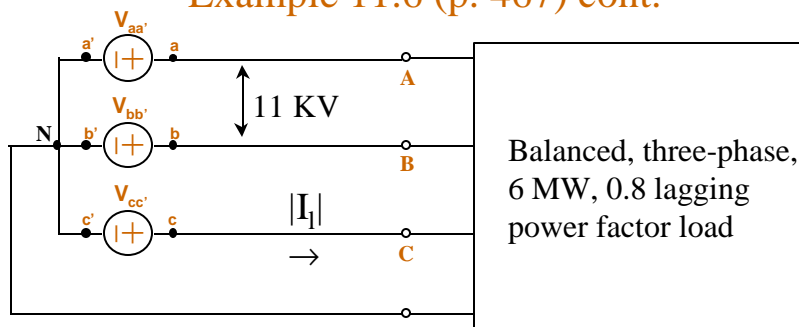

$$P_{3\text{ph}} = 6 \text{ MW} = \sqrt{3} \times 11 \text{ KV} \times |I_l| \times 0.8 \quad (= \sqrt{3} |V_{ll}| |I_l| \cos\theta)$$


$$\therefore |I_l| \approx 393.6 \text{ A. Then}$$

$$Q_{3\text{ph}} = \sqrt{3} |V_{ll}| |I_l| \sin\theta = \sqrt{3} \times 11 \text{ KV} \times 393.6 \text{ A.} \times 0.6 \approx +4.5 \text{ MVAR}$$

(Note that $Q_{3\text{ph}} > 0$ since the power factor is lagging)

Section 11.4 Wye-Delta Equivalence cont.


Example 11.7 (p. 467)

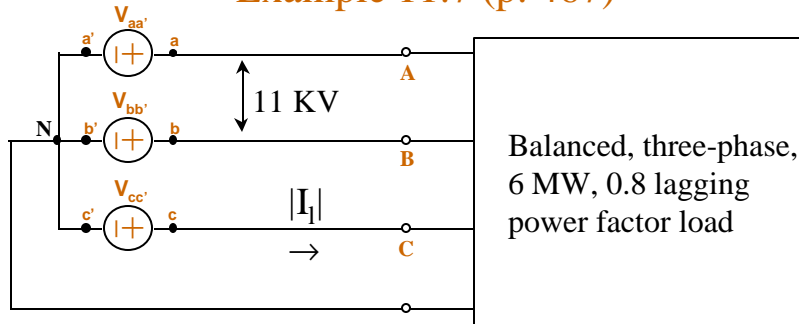

Find the total average power drawn by the load if the power factor of Example 11.6's load (shown above) is changed to 0.9 lagging and its line current is also reduced by 10% to 354.2 A.

Section 11.4 Wye-Delta Equivalence cont.

Example 11.7 (p. 467) cont.

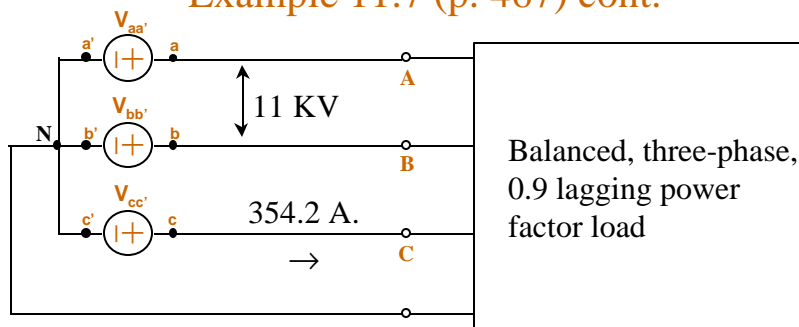

$$\begin{aligned}
 P_{3\text{ph}} &= \sqrt{3} |V_{ll}| |I_l| \cos\theta \\
 &= \sqrt{3} \times 11 \text{ kV} \times 354.2 \text{ A} \times 0.9 \\
 &= 6.074 \text{ MW}
 \end{aligned}$$

**We welcome your
questions with
Enthusiasm!!**



OHIO UNIVERSITY

Brian Manhire, Ph.D.

Professor of Electrical
Engineering

School of Electrical Engineering
& Computer Science
Stocker Center
Athens OH 45701-2979

740-593-1579 phone
740-593-0007 fax
bmanhire1@ohiou.edu

**School of Electrical Engineering
and
Computer Science**



Ohio University

Russ College of Engineering & Technology