



## Chapter 2 Synopsis


### Circuit Elements and Laws

- Introduction**
- 2.1 Charge and Electric Forces
  - 2.2 Voltage
  - 2.3 Current and Magnetic Forces
  - 2.4 Lumped-Circuit Elements
  - 2.5 Kirchhoff's Voltage and Current Laws
  - 2.6 The Resistor
  - 2.7 Voltage and Current Sources
  - 2.8 Signal Waveforms
  - 2.9 Analysis of Simple Circuits

### Chapter 2: Introduction (pp. 9-10)

- Useful electromechanical devices have electric circuit counterparts (see next slide = text Figure 2.2)
- Ergo, electric circuit analysis is fundamental to designing and understanding the behavior of electromechanical and electronic devices and systems

### Chapter 2: Introduction cont.

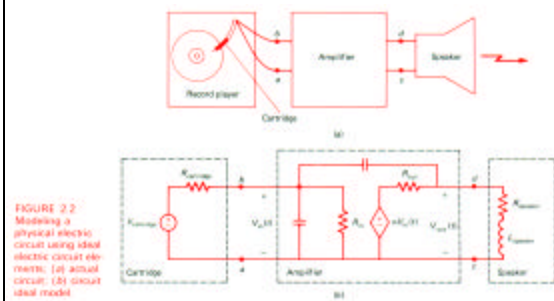


### Chapter 2: Introduction (pp. 9-10)

- In electric circuit analysis the most fundamental quantities are voltages and currents
- These are interrelated and in many practical applications ideal (linear) relationships e.g., Ohm's Law ( $V = R \times I$ ) apply

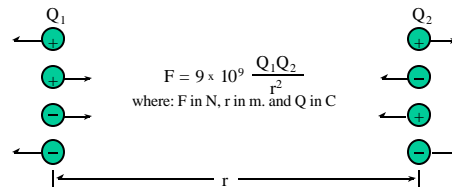
### 2.1 Charge and Electric Forces (pp. 11-13)

- Charge ( $Q_1$  &  $Q_2$ ) is the "stuff" of electricity
- There are two kinds of charge: positive (+) and negative (-)
- Unlike charges attract, like charges repel


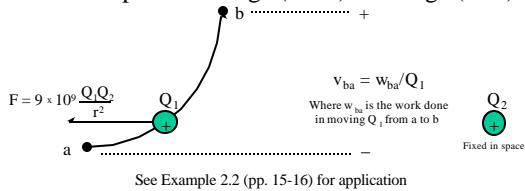
## 2.2 Voltage

- Charges exert *forces* on one another
- $\therefore$  *Moving* a charge  $Q_1$  in the presence of another charge  $Q_2$  entails doing *work* (expending energy) on that charge ( $Q_1$ )
- Work per unit charge (1 J/C) is voltage (1 V.)



Ohio University's Russ College of Engineering & Technology 7

## 2.2 Voltage cont.

- Another interpretation of voltage is: Charge carries energy: 1 J/C is 1 V.
- How much *energy* does a 12-V. automobile battery impart to each Coulomb of *charge* passing through it?



Ohio University's Russ College of Engineering & Technology 8

The **More Energy** per-unit charge,  
The **Higher** the **Voltage**




Ohio University's Russ College of Engineering & Technology 9
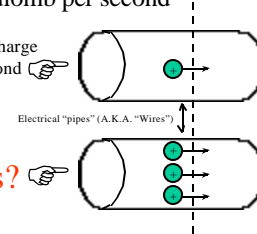
## 2.3 Current

- Current is a measure of the rate of flow of (net positive) charge per unit time
- 1 Ampere = 1 Coulomb per second

If this represents 1 C. of charge crossing the line each second  
A.K.A. **1 Ampere** . . .



What's this?

Ohio University's Russ College of Engineering & Technology 10

## 2.3 Current cont.

- Current is a measure of the rate of flow of (net positive) charge per unit time
- 1 Ampere = 1 Coulomb per second
- See next slide = Figure 2.10 (p. 17) for a graphical illustration of the charge/current relationship

$$i(t) = \frac{dq(t)}{dt} \quad (2.4)$$


$$q(t) = \int_{-\infty}^t i(\tau) d\tau \quad (2.5)$$

Units:  $i(t)$  is in Amperes when  $q(t)$  is in Coulombs and  $t$  is in seconds

Ohio University's Russ College of Engineering & Technology 11
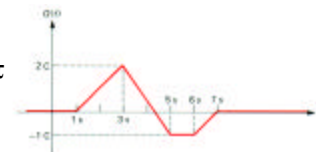
## 2.3 Current cont.

$$q(t) = \int_{-\infty}^t i(\tau) d\tau$$



$$i(t) = \frac{dq(t)}{dt}$$



FIGURE 2.10 Relation between current and net positive charge flowing past a point.

Ohio University's Russ College of Engineering & Technology 12

### 2.3 Voltage & Current Together

- Charge carries energy: 1 J/C is 1-V.
- Charge in motion is current: 1 C/Sec. is 1-A.
- How much *power* does the battery deliver to the automobile? (What's power?)
- How much *energy* does the battery deliver to the automobile? (Over what time interval?)

Technology 13

### 2.3 Voltage & Current Together cont.

How do the battery's power and energy compare to the lawnmower and the incandescent lamp?

Technology 14

### 2.3 Recapitulation: V & I Together

- Charge carries energy: 1 J/C is 1-V.
- Charge in motion is current: 1 C/Sec. is 1-A.

1. Where's the closed circuit?\*
2. Why is Mr. DVM upset?\*

\* Ergo, what's wrong with the cartoon's physics?

\*\* Give a quantitative answer in terms of the lawnmower & light bulb!  
 (Hint: What's the voltage and what's a reasonable current?)

Ohio University's Russ College of Engineering & Technology 15

### 2.3 Recapitulation: V & I Together

- Which scenario is more dangerous, HV or household?  
 (N.B.: The answer isn't as clear-cut as one might think.)

e.g., ~ 8-KV      120-V<sub>rms</sub>

Ohio University's Russ College of Engineering & Technology 16

### 2.4 Lumped-Circuit Elements

- Macroscopic (big picture) treatment of electrophysics
- Physical behavior of a region of electrical activity is averaged (lumped together) into a so-called "lumped-circuit element"
- The overall electrical activity associated with the element is captured, inter alia, by its voltage and current

Lumped Circuit Element →

Ohio University's Russ College of Engineering & Technology 17

### Voltage-Current -Power Relationship


- Voltage units are Joules / Coulomb
- Current units are Coulombs / second
- Voltage-Current product's units are ...
- (Joules / Coulomb) × (Coulombs / second) ...
- = Joules / second = Watts
- Ergo,  $P(t) = v(t)i(t)$  (which is Power)

Lumped Circuit Element →

Ohio University's Russ College of Engineering & Technology 18
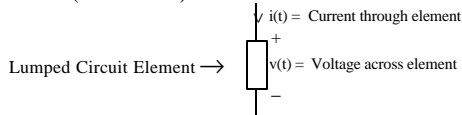
## Passive Sign Convention


- Given the passive sign convention shown below ...
- Then *if* at some time “*t*” both  $i(t) > 0$  and  $v(t) > 0$
- Then positive charge is moving through the element from top-to-bottom at the rate  $i(t)$  (in C/sec.) and ...
- The rate (per unit charge) of work (energy) being done to push the charge through the element is  $v(t)$  (in J/C)
- The power *absorbed* by the element is  $p(t) = v(t)i(t)$  in Watts (1 W = 1 J/s)



Ohio University's Russ College of Engineering & Technology 19

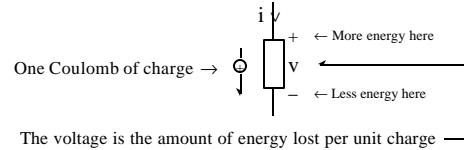
## Voltage Polarity Meaning

- The amount of energy (in Joules) that *each* Coulomb of charge loses (expends), as a result of its journey from top-to-bottom through the element, is numerically equal to its voltage (in Volts)



Ohio University's Russ College of Engineering & Technology 20

## Power Supplied vs. Power Absorbed

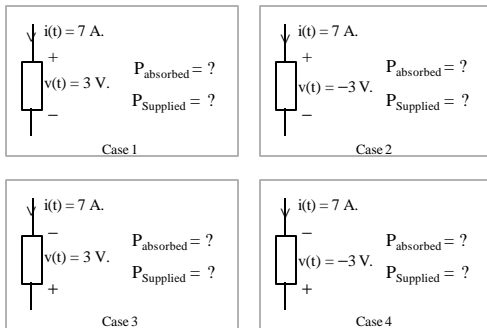

Ohio University's Russ College of Engineering & Technology 21


## 2.5 Kirchhoff's Voltage and Current Laws

- The behavior of electric-circuit currents and voltages are governed by these laws
- KCL is a manifestation of conservation of charge (see text p. 22)
- KVL is a manifestation of conservation of energy (see text p. 25)
- KCL and KVL are used in conjunction with circuit element laws; e.g., Ohm's Law (see text p. 28), etc. to perform electric circuit analysis

Ohio University's Russ College of Engineering & Technology 22
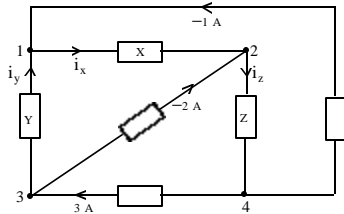
## Kirchhoff's Current Law (KCL)


- A circuit node is an electrical “location” of interest (see numbered black dots below)
- KCL: The sum-total of all currents entering (or leaving) each node equals zero



Ohio University's Russ College of Engineering & Technology 23
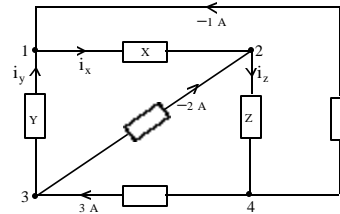
## Kirchhoff's Current Law (KCL) cont.


- KCL Sum: Each term in the sum is a current
- If summing *into* a node, each inbound current term has a positive sign and each outbound current term has a negative sign



Ohio University's Russ College of Engineering & Technology 24
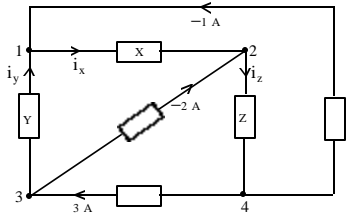
### Kirchhoff's Current Law (KCL) cont.


- **KCL at Node 1:**  $+i_y - i_x + (-1 \text{ A}) = 0 \text{ A}$  (I)
- **KCL at Node 2:**  $+i_x + (-2 \text{ A}) - i_z = 0 \text{ A}$  (II)
- **KCL at Node 3:**  $-i_y - (-2 \text{ A}) + 3 \text{ A} = 0 \text{ A}$  (III)



Ohio University's Russ College of Engineering & Technology 25
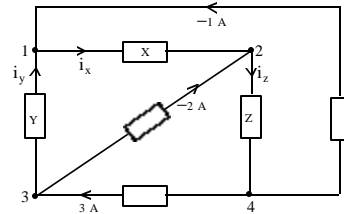
### Kirchhoff's Current Law (KCL) cont.


- (I), (II) & (III) have solution  $i_x = 4 \text{ A}$ ,  $i_y = 5 \text{ A}$  and  $i_z = 2 \text{ A}$ .
- Note that doing a KCL at node 4 is now redundant



Ohio University's Russ College of Engineering & Technology 26
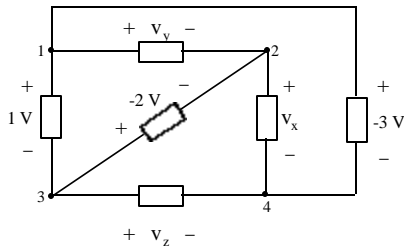
### Kirchhoff's Voltage Law (KVL)

- Relates a circuit's voltages to one another
- First must consider voltage *rise* vs. voltage *drop* concept




Ohio University's Russ College of Engineering & Technology 27
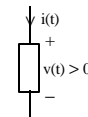
### Voltage Rise vs. Voltage Drop

- Positive charge moving across a change of voltage from the positive polarity sign towards the negative polarity sign experiences a voltage *drop* (a decrease in its energy)
- Positive charge moving across a change of voltage from the negative polarity sign towards the positive sign experiences a voltage *rise* (an increase in its energy)


If  $i(t) > 0$ , the downward moving charge experiences a voltage *drop*. However, if  $i(t) < 0$  then the upward moving charge experiences a voltage *rise*.



Ohio University's Russ College of Engineering & Technology 28
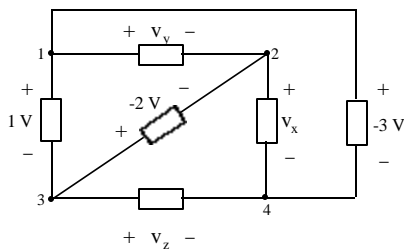
### Kirchhoff's Voltage Law (KVL)


- KVL: The sum-total of all voltage drops and voltages rises around any *closed path*—in any direction—equals zero



Ohio University's Russ College of Engineering & Technology 29
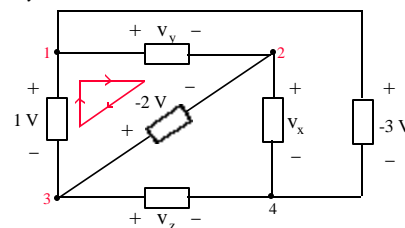
### Kirchhoff's Voltage Law (KVL)


- KVL for closed path  $1 \rightarrow 2 \rightarrow 3 \rightarrow 1$  (using the "land on polarity sign" rule to determine the sign of each term in the sum):
- $-v_y + (-2 \text{ V}) + 1 \text{ V} = 0 \text{ V}$  (I)



Ohio University's Russ College of Engineering & Technology 30
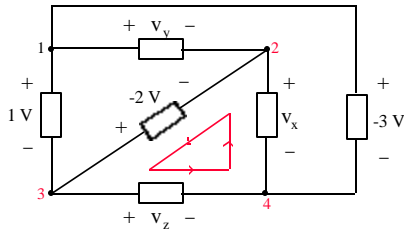
### Kirchhoff's Voltage Law (KVL)


- KVL for closed path  $2 \rightarrow 3 \rightarrow 4 \rightarrow 2$  (using "land on polarity sign" rule to determine the sign of each term in the sum):
- $+(-2\text{ V}) - v_z + v_x = 0\text{ V}$  (II)



Ohio University's Russ College of Engineering & Technology 31
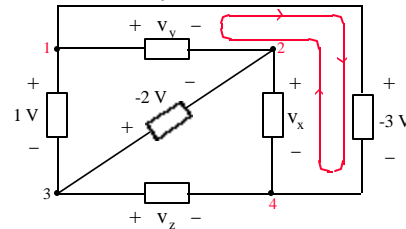
### Kirchhoff's Voltage Law (KVL)


- KVL for closed path  $1 \rightarrow 4 \rightarrow 2 \rightarrow 1$  (using "land on polarity sign" rule to determine the sign of each term in the sum):
- $-(-3\text{ V}) + v_x + v_y = 0\text{ V}$  (III)



Ohio University's Russ College of Engineering & Technology 32

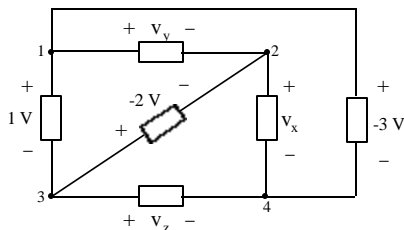
### Kirchhoff's Voltage Law (KVL)

- (I), (II) and (III) can be solved for  $v_x$ ,  $v_y$  and  $v_z$
- N.B.: There are other (now redundant) closed paths (also see Text Problem 2.23, p. 52)



Ohio University's Russ College of Engineering & Technology 33


### The Resistor Lumped-Circuit Element

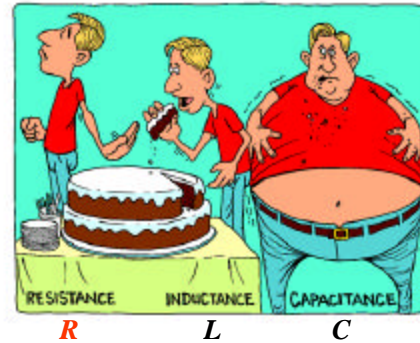

Ohio University's Russ College of Engineering & Technology 34
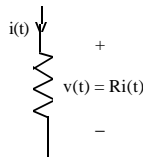
## 2.6 The Resistor


- The (ideal) resistor is defined by Ohm's Law:  $v(t) = Ri(t)$  where  $R$  is a positive constant *and*
- $v(t)$  and  $i(t)$  are *also* related by the passive sign convention (this second requirement is implicitly built into the Ohm's Law equation)



Ohio University's Russ College of Engineering & Technology 35
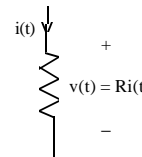
## 2.6 The Resistor cont.


- If  $i(t) > 0$  so too is  $v(t) = Ri(t)$  and vice versa; i.e., if  $i(t) < 0$  so is  $v(t)$ .
- So the resistor's absorbed power (voltage-current product) is always  $P_{\text{absorbed}} = v(t)i(t) \geq 0$



Ohio University's Russ College of Engineering & Technology 36

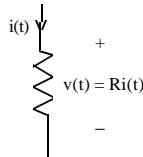
## 2.6 The Resistor cont.

- $G = R^{-1}$  is called conductance (in S)
- $P_R(t) = vi = (Ri)i = i^2R$
- $P_R(t) = vi = v(v/R) = v^2/R$




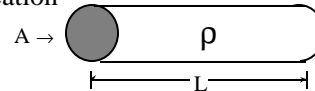
## 2.6 The Resistor cont. (more about R)

- $R = \rho(L/A)$  where
- The resistivity ( $\rho$ ) is material dependent (in  $\Omega \cdot m$ )
- The length ( $L$ ) is in m.
- The cross-sectional area ( $A$ ) is in  $m^2$ .
- See Text Example 2.4 (p. 30) for an application


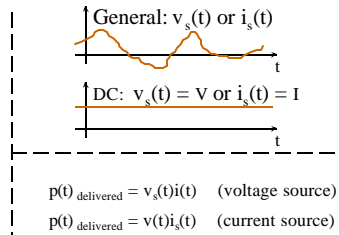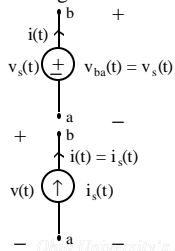
## 2.7 Voltage and Current Sources


- In circuit analysis, the ideal source concept is fundamental
- The ideal voltage source's terminal voltage is independent of the source's current
- The ideal current source's current is independent of the voltage across it



$p(t)_{\text{delivered}} = v_s(t)i(t)$  (voltage source)  
 $p(t)_{\text{delivered}} = v(t)i_s(t)$  (current source)

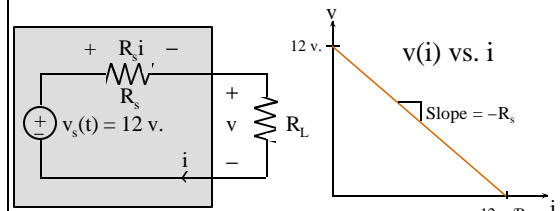
## 2.7 Source modeled via ideal source & resistor

- An actual source can be modeled using ideal circuit elements (e.g., ideal source & resistor—see below)



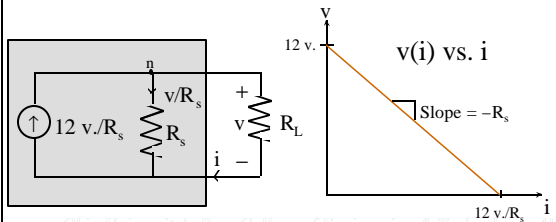
## 2.7 Source modeled via ideal source & resistor

- An actual source can be modeled using ideal circuit elements (e.g., ideal source & resistor—see below)




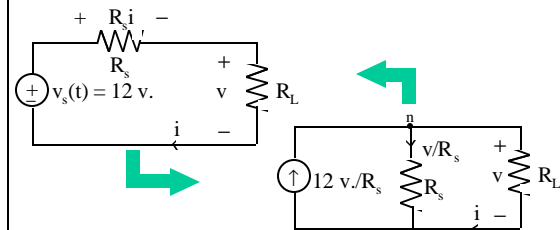
## 2.7 Source modeled via ideal source & resistor

- The preceding *source transformations* should be committed to memory, according to the text!




## 2.8 Signal waveforms

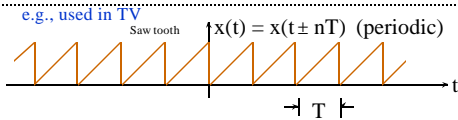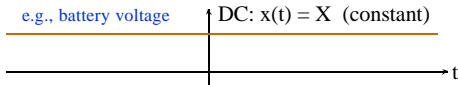

- $n = 1, 2, 3, \dots$  (integer)
- $T =$  Period (in sec.)
- $f = 1/T$  Frequency (in Hz.)

## 2.8 Signal waveforms cont.

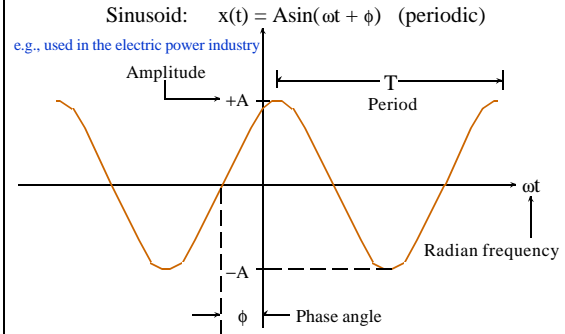

## 2.8 Signal waveforms cont.


- Waveforms can be *numerically* compared (as opposed to *visually* compared) by way of numerical attributes which measure some meaningful waveform property
- Average value is intuitively appealing (it measures a waveform's DC content)

$$x_{AVE} = \frac{1}{T} \int_t^{t+T} x(\tau) d\tau$$

(Where  $T$  is  $x(t)$ 's period)
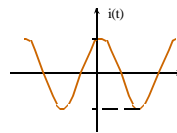
## 2.8 Signal waveforms cont.

If the AC's average is zero, why's Mr. DVM upset?\*



\* Moral: Average current isn't of much interest here (and is perhaps misleading).

## 2.8 Signal waveforms cont.

- The RMS (Root-Mean-Square) value measures a *periodic* waveform's *average* power
- RMS values of sinusoidal voltages and currents are the vernacular of the electric power industry

$$x_{RMS} = \sqrt{\frac{1}{T} \int_t^{t+T} x^2(\tau) d\tau}$$

(Where  $T$  is  $x(t)$ 's period)

## 2.8 Signal waveforms cont.


- A *current* signal's RMS value is a measure of its *average* power

$$P_{AVE} = \frac{1}{T} \int_t^{t+T} p(\tau) d\tau$$

$$P_{AVE} = \frac{1}{T} \int_t^{t+T} R i^2(\tau) d\tau = I_{RMS}^2$$


$$P_{AVE} = R \left[ \frac{1}{T} \int_t^{t+T} i^2(\tau) d\tau \right]$$
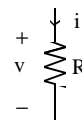
$$P_{AVE} = R I_{RMS}^2 \quad (\text{QED})$$


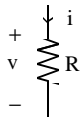
## 2.8 Signal waveforms cont.

- A *voltage* signal's RMS value is a measure of its *average* power



$$P_{AVE} = \frac{1}{T} \int_t^{t+T} p(\tau) d\tau$$

$$P_{AVE} = \frac{1}{T} \int_t^{t+T} v^2(\tau)/R d\tau = V_{RMS}^2$$

$$P_{AVE} = \frac{1}{R} \left[ \frac{1}{T} \int_t^{t+T} v^2(\tau) d\tau \right]$$

$$P_{AVE} = V_{RMS}^2 / R \text{ (QED)}$$

## 2.8 Signal waveforms cont.

- Moral:** A periodic signal's RMS value measures how powerful the signal is
- See text p. 38 for a sample RMS value calculation
- Another important RMS result (see text p. 39) is that the RMS value of the general sinusoidal waveform  $x(t) = A \sin(\omega t + \phi)$  is  $A/\sqrt{2} \approx 0.707A$
- Ergo, it is easy to program meters (e.g., VOMs, DVMs, etc.) to display the RMS values of the AC (sinusoidal) waveforms encountered in the electric power industry

## 2.8 Signal waveforms cont.


### Example 2-2

The resistance space heater (of constant resistance  $R_H$ ) when supplied by a  $170 \sin(120\pi t)$  V. (t in seconds) sinusoidal (AC) voltage source takes 5 minutes to raise a room's temperature  $3^\circ$  F. If the same heater is supplied by a 48 Volt (DC) voltage source, how long will it take (in minutes) to do the same job?



## 2.8 Signal waveforms cont.

### Example 2-2 cont.

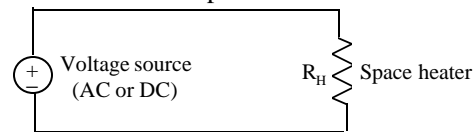

$$E_{AC} = \text{Energy for AC case} = P_{ave} \times T_{AC} = [(V_{RMS})^2/R_H] \times 5 \text{ Min.}$$

$$\therefore E_{AC} = [(170 \text{ V.}/\sqrt{2})^2/R_H] \times 5 \text{ Min.}$$

$$E_{DC} = \text{Energy for DC case} = P_{DC} \times T_{DC} = [(V_{DC})^2/R_H] \times T_{DC}$$


$$\therefore E_{DC} = [(48 \text{ V.})^2/R_H] \times T_{DC}$$

$$\text{Then: } E_{AC} = [(170 \text{ V.}/\sqrt{2})^2/R_H] \times 5 \text{ Min.} = [(48 \text{ V.})^2/R_H] \times T_{DC} = E_{DC}$$

which yields  $T_{DC} \approx 31 \text{ Min.}$
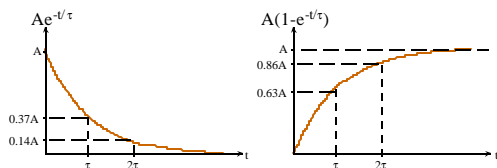
## 2.8 Signal waveforms cont.


- Exponential waveform:  $x(t) = Ae^{-t/\tau}$  (t is in seconds)
- Time constant (parameter) is  $\tau$  (also in seconds)
- Captures *transient* behavior of many physical phenomena (e.g., radioactive decay, mechanical motion, electrical transients, etc.)



## 2.8 Signal waveforms cont.

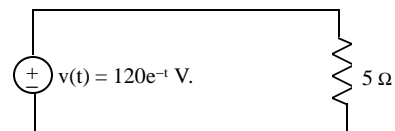
### Example 2-3

An ideal exponential voltage source of  $120e^{-t}$  V. supplies power to a  $5 \Omega$  resistor. Calculate the following quantities for the time period  $0 \leq t < \infty$ : the total energy (in Joules) absorbed by the resistor, the total charge (in Coulombs) that flows through the resistor, the average voltage (in Volts) across the resistor and the time it takes an AC, 120 V. (RMS), 60 W., incandescent lamp to consume the same energy as the resistor.



## 2.8 Signal waveforms cont.

Example 2-3 cont.

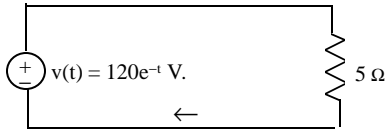

$$i(t) = v(t)/5\Omega = 24e^{-t} \text{ A.}$$


**Power:**  $p(t) = v(t) \times i(t) = 5\Omega \times i^2(t) = v^2(t)/5\Omega = 2880e^{-2t} \text{ W.}$

**Energy:**  $W_R = \int_0^{\infty} p(\tau) d\tau = \int_0^{\infty} 2880e^{-2\tau} d\tau = 1.44 \text{ kJ.}$

**Charge:**  $Q = \int_0^{\infty} i(\tau) d\tau = \int_0^{\infty} 24e^{-\tau} d\tau = 24 \text{ C.}$

## 2.8 Signal waveforms cont.

Example 2-3 cont.

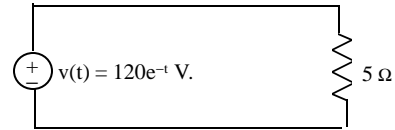


The average voltage is:  $V_{ave} = W/Q = 1.44 \text{ kJ}/24\text{C} = 60 \text{ J/C}$   
 $\therefore V_{ave} = 60 \text{ V.}$  (in what sense is this the voltage's *average*?)

Equating the lamp's energy to the resistor's energy yields:  
 $P_{lamp} \times T_{lamp} = 1.44 \text{ kJ} = W_{5\Omega}$  (where  $P_{lamp} = 60 \text{ W}$ ,  $W = 60 \text{ J/Sec.}$ )

Ergo,  $T_{lamp} = 24 \text{ Seconds}$
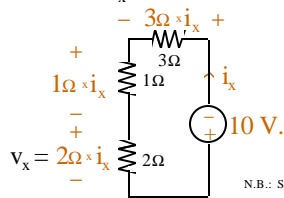
## 2.9 Analysis of Simple Circuits


- *Single-loop circuit analysis* involves several applications of Ohm's Law ( $1\Omega \times i_x$ ,  $2\Omega \times i_x$  and  $3\Omega \times i_x$  (note use of passive sign convention on schematic)) and ...
- One KVL:  $2\Omega \times i_x + 1\Omega \times i_x + 3\Omega \times i_x + 10 \text{ V} = 0 \text{ V}$ , which has solution  $i_x = -5/3 \text{ A}$ .



N.B.: See text Problem 2.31, p. 54.
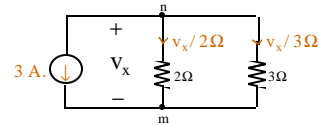
## 2.9 Analysis of Simple Circuits cont.


- *Single-node-pair circuit analysis* involves several applications of Ohm's Law ( $v_x / 2\Omega$  and  $v_x / 3\Omega$ ) — note use of passive sign convention on schematic and ...
- One KCL (at node n or m):  $3 \text{ A} + v_x / 2\Omega + v_x / 3\Omega = 0 \text{ A}$ , which has solution  $v_x = -3.6 \text{ V}$ .



N.B.: See text Problem 2.30, p. 53.
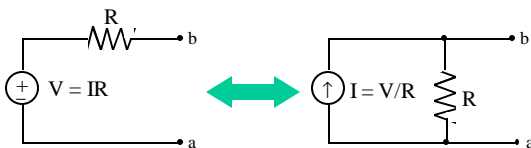
## 2.9 Analysis of Simple Circuits cont.


- *Source transformations* (described earlier and repeated below) can be used to convert some circuits to either a *single-loop circuit* or *single-node-pair circuit* — which can then be analyzed as described earlier



## 2.9 Analysis of Simple Circuits cont.

Example 2-4


Find  $i_x$  and  $v_x$

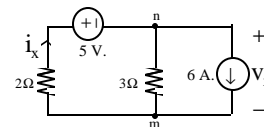

N.B.: See text Problem 2.39, p. 56.
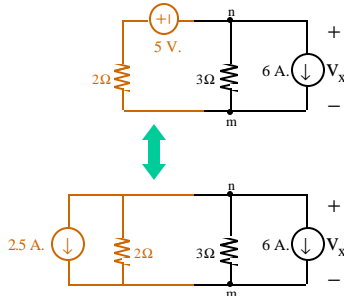
### Example 2-4 cont.


- Step 1: Create single-node-pair circuit using source conversion



Ohio University's Russ College of Engineering & Technology 61
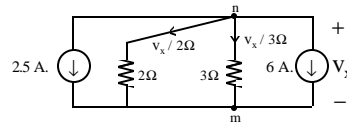
### Example 2-4 cont.


- Step 2: Solve the single-node-pair circuit for  $v_x$
- KCL at node n:  
 $2.5 \text{ A.} + v_x / 2\Omega + v_x / 3\Omega + 6 \text{ A.} = 0 \text{ A.}$
- Which has solution  $v_x = -10.2 \text{ V.}$



Ohio University's Russ College of Engineering & Technology 62
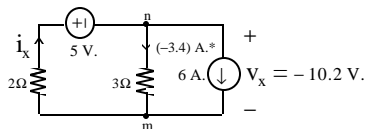
### Example 2-4 cont.

- Step 3: With  $v_x$  now known, solve the original circuit for  $i_x$
- KCL at node n:  $i_x - (-3.4) \text{ A.} - 6 \text{ A.} = 0 \text{ A.}$
- Which has solution  $i_x = 2.6 \text{ A.}$




\*N.B.:  $(-10.2 \text{ V.} / 3\Omega) = -3.4 \text{ A.}$

Ohio University's Russ College of Engineering & Technology 63


## 2.9 Analysis of Simple Circuits cont.

Example 2-5: Find  $I_x$  and  $V_x$

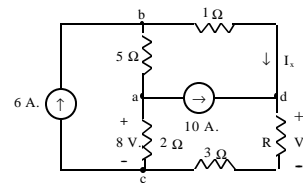

Ohio University's Russ College of Engineering & Technology 64


### Example 2-5 cont.

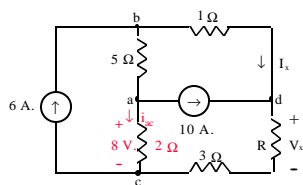

Ohm's Law:  $i_{ac} = 8 \text{ V.} / 2 \Omega = 4 \text{ A.}$

Ohio University's Russ College of Engineering & Technology 65


### Example 2-5 cont.

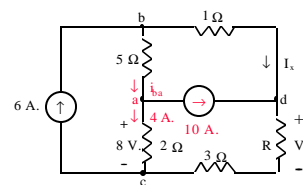

KCL at node a:  $i_{ba} - 4 \text{ A.} - 10 \text{ A.} = 0 \text{ A.}$   
 $\therefore i_{ba} = 14 \text{ A.}$


Ohio University's Russ College of Engineering & Technology 66

Example 2-5 cont.

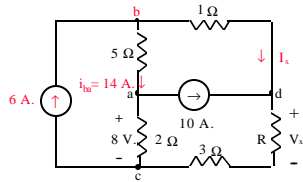


**KCL at node b:**  $6 \text{ A.} - 14 \text{ A.} - I_X = 0 \text{ A.}$   
 $\therefore I_X = -8 \text{ A.}$

Example 2-5 cont.

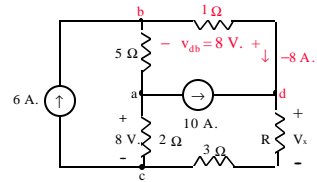


**Ohm's Law:**  $v_{db} = 1 \Omega \times [ -(-8 \text{ A.}) ] = 8 \text{ V.}$

Example 2-5 cont.

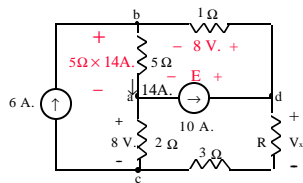


**KVL (Top-right mesh):**  $5 \Omega \times 14 \text{ A.} + 8 \text{ V.} - E = 0 \text{ V.}$   
 $\therefore E = 78 \text{ V.}$

Example 2-5 cont.

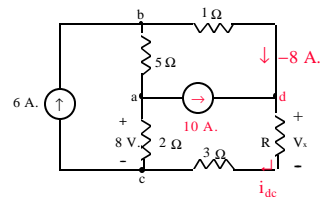


**KCL at node d:**  $10 \text{ A.} + (-8 \text{ A.}) - i_{dc} = 0 \text{ A.}$   
 $\therefore i_{dc} = 2 \text{ A.}$

Example 2-5 cont.

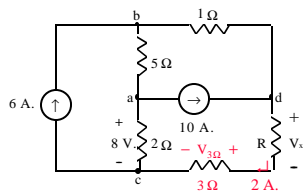

**Ohm's Law:**  $V_{3\Omega} = 3 \Omega \times 2 \text{ A.} = 6 \text{ V.}$


Example 2-5 cont.

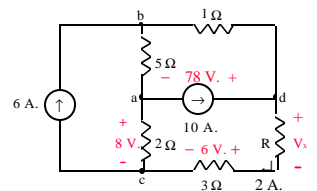

**KVL (Bottom-right mesh):**  
 $8 \text{ V.} + 78 \text{ V.} - V_X - 6 \text{ V.} = 0 \text{ V.}$   
 $\therefore V_X = 80 \text{ V.}$

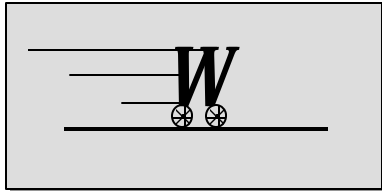
## Examination

Identify the *dynamic* EE object shown below



Ohio University's Russ College of Engineering & Technology 73

**HO  
ME  
WO  
RK**

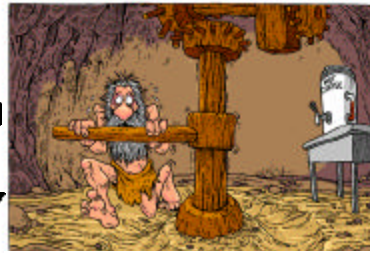

**Ex  
am  
P  
ay  
o  
f**

105 Problems  $\therefore$   $\approx$  11 per week

**Teamwork!**

Ohio University's Russ College of Engineering & Technology 74

## Acknowledgement: Cartoons courtesy of

Test & Measurement  
**Educator's Corner**  
HEWLETT  
PACKARD  
Search  
Hewlett-Packard  
Test & Measurement  
Sharing Hewlett-Packard's Resources  
With Engineering Educators  
<http://www.EducatorsCorner.com>

Ohio University's Russ College of Engineering & Technology 75

**We welcome your  
questions with  
Enthusiasm!!**



**Brian Manhire, Ph.D.**  
Professor of Electrical  
Engineering  
**OHIO UNIVERSITY**  
School of Electrical Engineering  
& Computer Science  
Stocker Center  
Athens OH 45701-2270  
740-593-8179 phone  
740-593-0007 fax  
bmanhire1@ohio.edu

Ohio University's Russ College of Engineering & Technology 76