

EE 313: Basic EE
Chapter 4 Synopsis
© Copyright 1999 Brian Manhire



Ohio University's Russ College of Engineering & Technology


Chapter 4 Synopsis

Energy Storage Elements

- 4.1 The Capacitor
- 4.2 The Inductor
- 4.3 Continuity of Capacitor Voltages and Inductor Currents
- 4.4 Transformers and Coupled Coils
- 4.5 Circuit Differential Equations for Circuits Containing Energy Storage Elements
- 4.6 Response of Energy Storage Elements to DC Sources

Ohio University's Russ College of Engineering & Technology

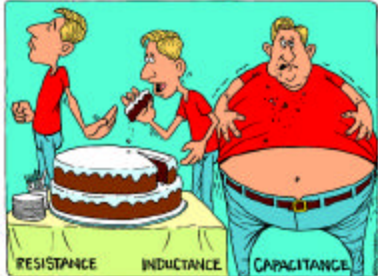4.1 Energy Storage Elements: The Capacitor



R L C

Ohio University's Russ College of Engineering & Technology

4.1 Energy Storage Elements: The Capacitor


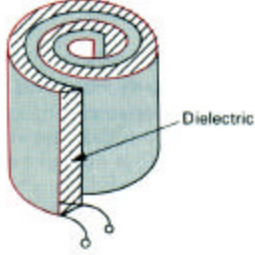


FIGURE 4.2
Physical construction of a capacitor to occupy a small space.

Ohio University's Russ College of Engineering & Technology

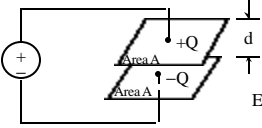4.1 Energy Storage Elements: The Capacitor

- Voltage V (in Volts) applied to the conceptual capacitor shown causes a charge Q in Coulombs to be deposited on the top plate
- The top plate's charge pushes an equal amount of (displacement) charge off of the bottom plate, leaving a negative (absence of) charge $-Q$ on the bottom plate
- The relationship between the applied voltage and charge is $Q = CV$ (C is in Farads when V is in Volts and Q is in Coulombs; i.e., $1\text{ F} = 1\text{ Coulomb per Volt}$)



$Q = CV$
 $C = 8.84 \times 10^{-12} \text{ (A/d)}$
 Energy is stored in the electric field existing between the plates

Ohio University's Russ College of Engineering & Technology

4.1 The Capacitor cont.

- $Q(t) = Cv(t)$, where C is constant
- Differentiate both sides with respect to time to obtain $dQ(t)/dt = C \times dv(t)/dt$
- However, $dQ(t)/dt = i(t)$ (current) $\therefore i(t) = C \times dv(t)/dt$, where the passive sign convention is built into the formula (see below)

$$\begin{aligned}
 \downarrow i(t) &= C \frac{dv(t)}{dt} \quad \text{and} \\
 \begin{array}{c} + \\ | \\ C \\ | \\ - \end{array} v(t) &= \frac{1}{C} \int_{-\infty}^t i(\tau) d\tau = \frac{1}{C} \int_{-\infty}^t i(\tau) d\tau + \frac{1}{C} \int_t^t i(\tau) d\tau \\
 &= v(t_0) + \frac{1}{C} \int_{t_0}^t i(\tau) d\tau
 \end{aligned}$$

Ohio University's Russ College of Engineering & Technology


4.1 The Capacitor cont.

- Stored energy = $W(t) = CV^2/2$ (see below)



$$\begin{aligned} W(t) &= \int_{-\infty}^t p(\tau) d\tau = \int_{-\infty}^t v(\tau) i(\tau) d\tau \\ &= \int_{-\infty}^t v(\tau) C \frac{dv(\tau)}{d\tau} d\tau \\ &= C \int_{v(-\infty)}^{v(t)} v(\tau) dv(\tau) = \frac{1}{2} C v(t)^2 - \frac{1}{2} C v(-\infty)^2 \\ \therefore W(t) &= \frac{1}{2} C v(t)^2 \quad (\text{Assuming no initial stored energy}) \end{aligned}$$

Ohio University's Russ College of Engineering & Technology 7

4.1 The Capacitor cont.

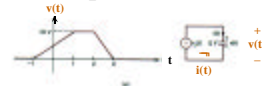


Text Example 4.1
(pp. 108-109)

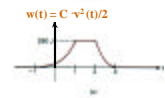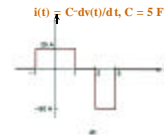

Ohio University's Russ College of Engineering & Technology 8

4.1 The Capacitor cont.

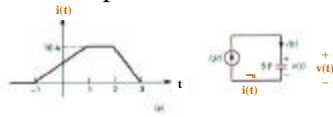


Text Example 4.2
(pp. 109-110)

FIGURE 4.6
Example 4.2
Illustration of a
capacitor driven
by a current
source

Ohio University's Russ College of Engineering & Technology 9

4.1 The Capacitor cont.

Example 4-1

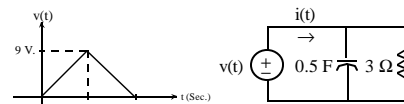


Sketch the source current $i(t)$ and calculate the following:

- The capacitor's maximum stored energy
- The total energy consumed by the resistor
- The total energy supplied by the source
- The total charge that flows through the resistor
- The resistor's average voltage

Ohio University's Russ College of Engineering & Technology 10

4.1 The Capacitor cont.

Example 4-1 cont.

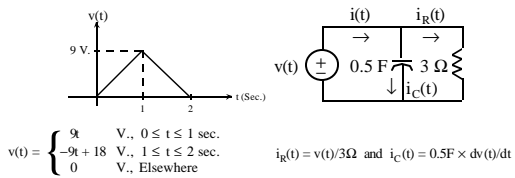

$$v(t) = \begin{cases} 9 & \text{V., } 0 \leq t \leq 1 \text{ sec.} \\ -9t + 18 & \text{V., } 1 \leq t \leq 2 \text{ sec.} \\ 0 & \text{V., Elsewhere} \end{cases} \quad i_R(t) = v(t)/3\Omega \text{ and } i_C(t) = 0.5F \times dv(t)/dt$$

Therefore


$$i_R(t) = \begin{cases} 3 & \text{A., } 0 \leq t \leq 1 \text{ sec.} \\ -3t + 6 & \text{A., } 1 \leq t \leq 2 \text{ sec.} \\ 0 & \text{A., Elsewhere} \end{cases} \quad \text{and} \quad i_C(t) = \begin{cases} +4.5 & \text{A., } 0 < t < 1 \text{ sec.} \\ -4.5 & \text{A., } 1 < t < 2 \text{ sec.} \\ 0 & \text{A., Elsewhere} \end{cases}$$

and KCL yields: $i(t) = i_R(t) + i_C(t)$

Ohio University's Russ College of Engineering & Technology 11

4.1 The Capacitor cont.


Example 4-1 cont.

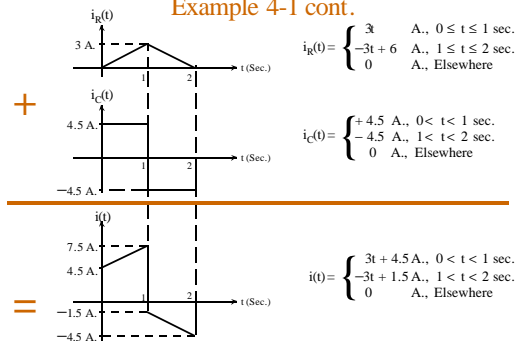

Ohio University's Russ College of Engineering & Technology 12

4.1 The Capacitor cont.

Example 4-1 cont.

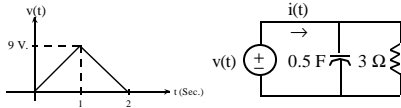


$$W_C = \frac{1}{2} C \times v^2$$

So the capacitor's maximum stored energy is $0.5 \times C \times (v_{\max})^2 = 0.5 \times 0.5 \text{ F} \times (9 \text{ V})^2 = 20.25 \text{ J}$.

4.1 The Capacitor cont.

Example 4-1 cont.

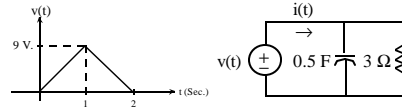


$$W_R = \int_{-\infty}^{\infty} P_R(t) dt = \int_0^2 v(t)^2 / 3\Omega dt$$

$$= \int_0^1 (9t \text{ V})^2 / 3\Omega dt + \int_1^2 (-9t + 18 \text{ V})^2 / 3\Omega dt = 18 \text{ J}$$

4.1 The Capacitor cont.

Example 4-1 cont.

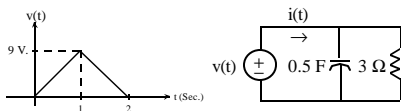

The capacitor can neither consume nor create energy—it can only store energy


The voltage is nil for $0 \geq t \geq 2$ seconds so there is no net stored energy in the capacitor over the time interval $0 \leq t \leq 2$ seconds

Therefore it follows that the energy supplied (produced) by the source equals the energy consumed by the resistor (which is 18 J.)

What is the temporal behavior of the capacitor's stored energy?

4.1 The Capacitor cont.

Example 4-1 cont.

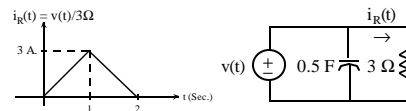

$$Q_R = \int_{-\infty}^{\infty} i_R(t) dt = \int_0^2 v(t) / 3\Omega dt$$


$$= \int_0^1 (3t \text{ A}) dt + \int_1^2 (-3t + 6 \text{ A}) dt = 3 \text{ C}$$

and $V_{\text{ave.}} = W_R / Q_R = 18 \text{ J} / 3 \text{ C} = 6 \text{ J/C} = 6 \text{ V}$.

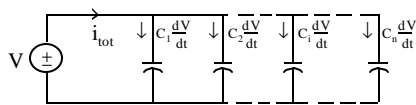4.1 The Capacitor cont.

- Capacitance in parallel adds:

$$C_{\text{tot}} = C_1 + C_2 + \dots + C_n$$




$$\text{KCL: } i_{\text{tot}} = \sum_{j=1}^{j=n} C_j \frac{dV}{dt} = \frac{dV}{dt} \sum_{j=1}^{j=n} C_j = C_{\text{tot}} \frac{dV}{dt}$$

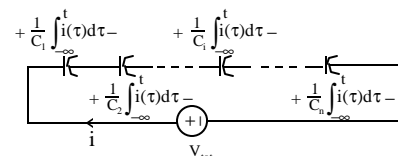4.1 The Capacitor cont.


- Capacitance in series adds reciprocally:

$$C_{\text{tot}}^{-1} = C_1^{-1} + C_2^{-1} + \dots + C_n^{-1}$$




$$\text{KVL: } V_{\text{tot}} = \sum_{j=1}^{j=n} \frac{1}{C_j} \int_{-\infty}^t i(\tau) d\tau = \frac{1}{C_{\text{tot}}} \int_{-\infty}^t i(\tau) d\tau$$

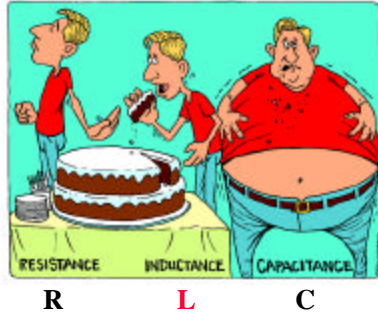4.2 Energy Storage Elements: The Inductor



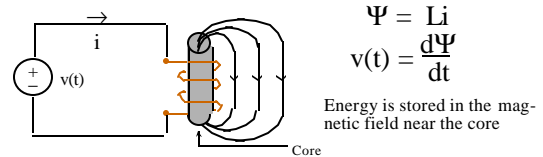4.2 Energy Storage Elements: The Inductor

- Energy is stored in the magnetic field created by the current flowing in the coil (wrapped around a Ferromagnetic core)



4.2 Energy Storage Elements: The Inductor



The Unit of Inductance (**L**) is the Henry

4.2 The Inductor cont.

$\psi = Li(t)$, where L is constant

- Differentiate both sides with respect to time to obtain $d\psi(t)/dt = L \times di(t)/dt$
- However, $d\psi(t)/dt = v(t)$ (voltage) $\therefore v(t) = L \times di(t)/dt$, where the passive sign convention is built into the formula (see below)

$$L \frac{di(t)}{dt} = v(t) \quad \text{and}$$

$$i(t) = \frac{1}{L} \int_{-\infty}^t v(\tau) d\tau = \frac{1}{L} \int_{-\infty}^{t_0} v(\tau) d\tau + \frac{1}{L} \int_{t_0}^t v(\tau) d\tau$$

$$= i(t_0) + \frac{1}{L} \int_{t_0}^t v(\tau) d\tau$$

4.2 The Inductor cont.

- Stored energy = $W(t) = Li^2/2$ (see below)

$$W(t) = \int_{-\infty}^t p(\tau) d\tau = \int_{-\infty}^t v(\tau) i(\tau) d\tau$$


$$= \int_{-\infty}^t L \frac{di(\tau)}{d\tau} i(\tau) d\tau$$

$$= L \int_{i(-\infty)}^{i(t)} i(\tau) di(\tau) = \frac{1}{2} Li(t)^2 - \frac{1}{2} Li(-\infty)^2$$


$$\therefore W(t) = \frac{1}{2} Li(t)^2 \quad (\text{Assuming no initial stored energy})$$

4.2 The Inductor cont.


Text Example 4.3 (p. 117)

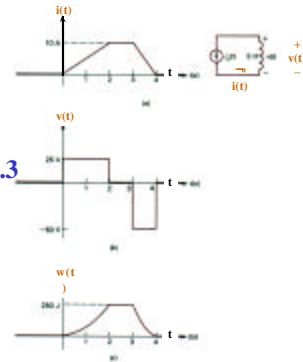

4.2 The Inductor cont.

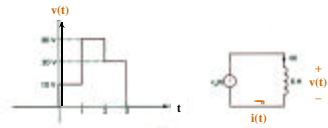


Text Example 4.4
(p. 118)

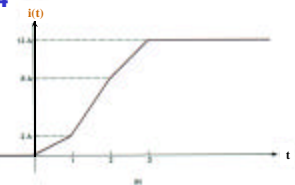

4.2 The Inductor cont.

- Inductance in series adds:

$$L_{tot} = L_1 + L_2 + \dots + L_n$$

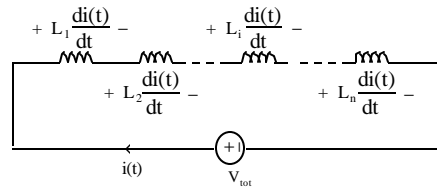


$$\text{KVL: } V_{tot} = \sum_{j=1}^{j=n} L_j \frac{di(t)}{dt} = L_{tot} \frac{di(t)}{dt}$$

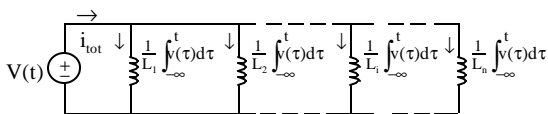4.2 The Inductor cont.

- Inductance in parallel adds reciprocally:

$$L_{tot}^{-1} = L_1^{-1} + L_2^{-1} + \dots + L_n^{-1}$$



$$\text{KCL: } i_{tot} = \sum_{j=1}^{j=n} \frac{1}{L_j} \int_{-\infty}^t v(\tau) d\tau = \frac{1}{L_{tot}} \int_{-\infty}^t v(\tau) d\tau$$


4.3 Continuity of Capacitor Voltage and Inductor Current

$$C \begin{matrix} \downarrow \\ i(t) \\ + \\ v(t) \\ - \end{matrix} \quad \begin{matrix} \text{Finite } i(t) \text{ requires finite } \frac{dv(t)}{dt} \\ \text{Finite } \frac{dv(t)}{dt} \text{ requires continuous } v(t) \end{matrix}$$


$$L \begin{matrix} \downarrow \\ i(t) \\ + \\ v(t) \\ - \end{matrix} \quad \begin{matrix} \text{Finite } v(t) \text{ requires finite } \frac{di(t)}{dt} \\ \text{Finite } \frac{di(t)}{dt} \text{ requires continuous } i(t) \end{matrix}$$

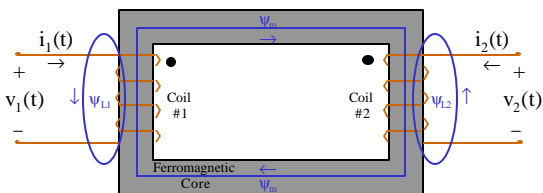4.4 Transformers and Coupled Coils


- Coil currents produce two types of magnetic flux (leakage & mutual)
- The (black) "dot" convention is used to indicate the configuration of how each coil is wound on the core



4.4 Transformers and Coupled Coils cont.

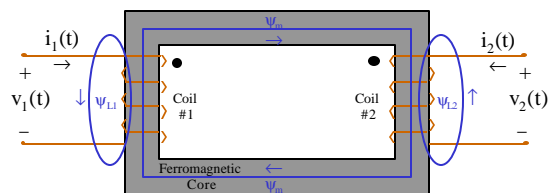

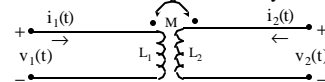The coil-core arrangement shown (physically) above is shown schematically below



4.4 Transformers and Coupled Coils cont.

Without mutual induction, the coils are merely two independent inductors having the *decoupled* equations given below

$$v_1(t) = L_1 \frac{di_1(t)}{dt} \quad \text{and} \quad v_2(t) = L_2 \frac{di_2(t)}{dt}$$

Ohio University's Russ College of Engineering & Technology 31

4.4 Transformers and Coupled Coils cont.

With mutual induction, the coils become dependent inductors having the *coupled* equations given below

$$v_1(t) = L_1 \frac{di_1(t)}{dt} + M \frac{di_2(t)}{dt} \quad \text{and} \quad v_2(t) = L_2 \frac{di_2(t)}{dt} + M \frac{di_1(t)}{dt}$$

Ohio University's Russ College of Engineering & Technology 32

4.4 Transformers and Coupled Coils cont.

Each term in the KVLs below is a voltage

$$v_1(t) = L_1 \frac{di_1(t)}{dt} + M \frac{di_2(t)}{dt} \quad \text{and} \quad v_2(t) = L_2 \frac{di_2(t)}{dt} + M \frac{di_1(t)}{dt}$$

Ohio University's Russ College of Engineering & Technology 33

4.4 Transformers and Coupled Coils cont.

The voltage induced in each coil by the other coil's field can be represented using *dependent* voltage sources as shown below

KVL: $v_1(t) = L_1 \frac{di_1(t)}{dt} + M \frac{di_2(t)}{dt}$ KVL: $v_2(t) = L_2 \frac{di_2(t)}{dt} + M \frac{di_1(t)}{dt}$

Ohio University's Russ College of Engineering & Technology 34

4.4 Transformers and Coupled Coils cont.

The lumped-circuit model can be developed in stages as follows:
Step 1: Draw the circuit showing self- and mutual-inductance voltages *without* their polarities (see below)

N.B.: The terminal voltages and currents *are* included in this first step's schematic but the polarities of the four voltages associated with the transformer *aren't*

Ohio University's Russ College of Engineering & Technology 35

4.4 Transformers and Coupled Coils cont.


Step 2: Assign self-inductance voltage polarities using the passive sign convention in conjunction with the directions of $i_1(t)$ and $i_2(t)$

N.B.: $i_1(t)$ flows into the positive sign of the $L_1(di_1(t)/dt)$ voltage drop and $i_2(t)$ flows into the positive sign of the $L_2(di_2(t)/dt)$ voltage drop

Ohio University's Russ College of Engineering & Technology 36

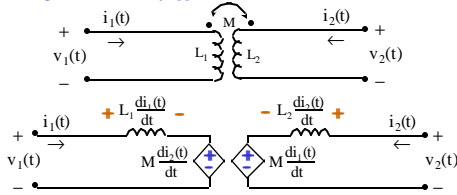4.4 Transformers and Coupled Coils cont.


Step 3: Assign the (mutual inductance) dependent voltage source polarities using the rule: "If both currents flow into the dots or if both currents flow out of the dots, then the mutual voltages aid (boost) the self-inductance voltage drops—otherwise they oppose (buck)"



N.B.: Here, *aid (boost)* applies since *both* currents flow from the terminals (ports) *into* transformer dots

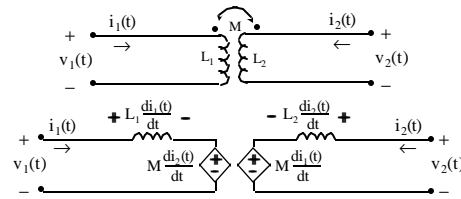
4.4 Transformers and Coupled Coils cont.

The transformer, its corresponding lumped-circuit (dependent-sources based) model and associated KVLs are shown below




$$\text{KVL: } v_1(t) = L_1 \frac{di_1(t)}{dt} + M \frac{di_2(t)}{dt} \quad \text{KVL: } v_2(t) = L_2 \frac{di_2(t)}{dt} + M \frac{di_1(t)}{dt}$$

4.4 Ideal Transformer

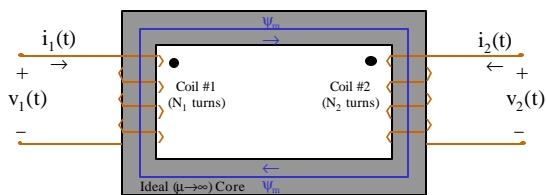

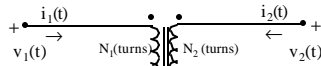
If the core is a *perfect* conductor of (magnetic) flux, there is no leakage flux and the transformer is ideal (see text pp. 124-126)



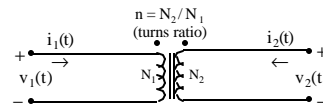4.4 Ideal Transformer Properties

$$v_2(t) = n v_1(t) \text{ and } i_1(t) = -n i_2(t) \text{ so that ...}$$

$$p_1(t) = v_1(t) i_1(t) = -v_2(t) i_2(t) = -p_2(t) \text{ (i.e., } p_1(t) + p_2(t) = 0 \text{)} \therefore \textit{lossless}$$




4.4 Ideal Transformer Properties cont.

$$v_2(t) = n v_1(t) \text{ and } i_1(t) = -n i_2(t) \text{ so that ...}$$


$$R_{eq2} = -v_2(t)/i_2(t) = n^2(v_1(t)/i_1(t)) = n^2 R_{eq1}$$

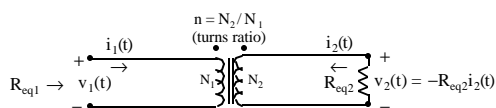(i.e., *reflected* impedance concept—see text Example 4.6, pp. 127-128)



4.4 Ideal Transformer Properties cont.


Example 4-2 (Text Problem 4.25)

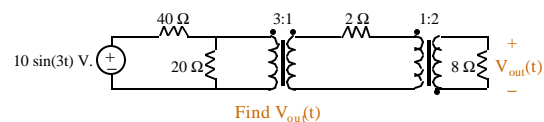

Find $V_{out}(t)$


Solution

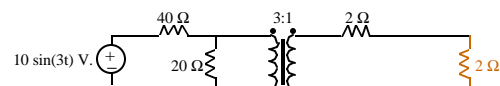Begin by reflecting the 8 Ω resistor across the right transformer using $R_{eq} = (1/2)^2 \times 8 \Omega = 2 \Omega$ to obtain the equivalent circuit below




4.4 Ideal Transformer Properties cont.

Example 4-2 cont.

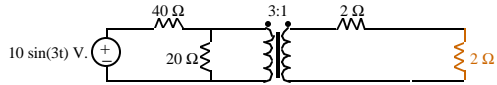


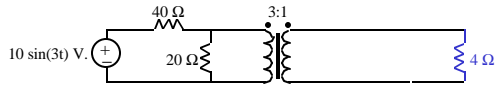Next add the two series resistors ($2\ \Omega + 2\ \Omega = 4\ \Omega$) to obtain the circuit below




4.4 Ideal Transformer Properties cont.

Example 4-2 cont.

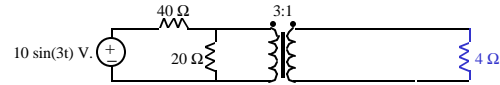


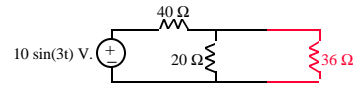Reflect the $4\ \Omega$ resistor across the transformer using $R_{eq} = (3/1)^2 \times 4\ \Omega = 36\ \Omega$ to obtain the equivalent circuit below



4.4 Ideal Transformer Properties cont.

Example 4-2 cont.

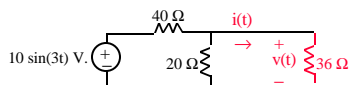


$20\ \Omega \parallel 36\ \Omega \approx 12.86\ \Omega$ along with voltage division yields:

$$v(t) \approx [12.86\ \Omega / (40 + 12.86)\ \Omega] \times 10\ \sin(3t)\ \text{V} \approx 2.43\ \sin(3t)\ \text{V}$$


Then by Ohm's Law, $i(t) = v(t) / 36\ \Omega \approx 0.0675\ \sin(3t)\ \text{A}$.

4.4 Ideal Transformer Properties cont.

Example 4-2 cont.

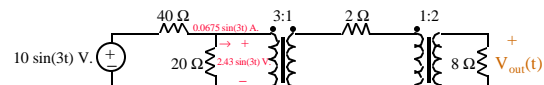


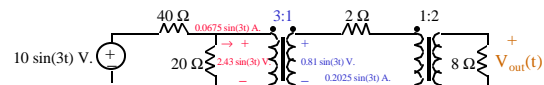$v(t)$ and $i(t)$ as shown on the original schematic above, are next reflected to the right side of the left transformer as indicated below



4.4 Ideal Transformer Properties cont.

Example 4-2 cont.

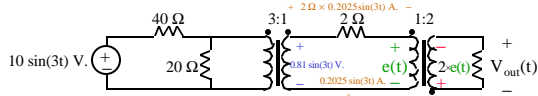

KVL: $e(t) = 0.81\ \sin(3t)\ \text{V} - 2\ \Omega \times 0.2025\ \sin(3t)\ \text{A} \approx 0.405\ \sin(3t)\ \text{V}$.

As a result of the right transformer's turns ratio and the arrangement of its polarity dots (and KVL), the relationship between $V_{out}(t)$ and $e(t)$ is:

$$V_{out}(t) = -2 \times e(t)$$


$$\therefore V_{out}(t) \approx -0.81\ \sin(3t)\ \text{V}$$

4.4 Ideal Transformer Properties cont.

Gear analogy


Transformer: $v_2(t) = n v_1(t)$ and $i_1(t) = -n i_2(t)$
where $n =$ coil turns ratio (N_2 / N_1)

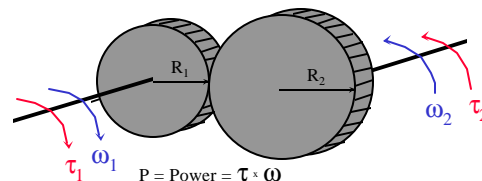Gears: $\tau_2(t) = -n \tau_1(t)$ and $\omega_1(t) = -n \omega_2(t)$
where $n =$ gear radii ratio (R_2 / R_1)



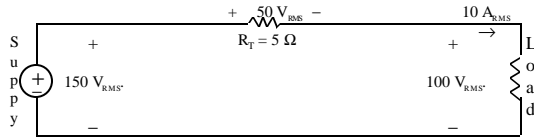4.4 Power Transformer Application: Electric Power Transmission Application

Case 1: Load supplied directly from source via a transmission line



$$P_{\text{loss}} = (10 \text{ A}_{\text{RMS}})^2 \cdot 5 \Omega = 0.5 \text{ kW (Half the load's power!)}$$


$$P_{\text{load}} = 100 \text{ V}_{\text{RMS}} \cdot 10 \text{ A}_{\text{RMS}} = 1 \text{ kW and } P_{\text{supply}} = 150 \text{ V}_{\text{RMS}} \cdot 10 \text{ A}_{\text{RMS}} = 1.5 \text{ kW}$$

$$\therefore \eta_{\%} = (1 \text{ kW} / 1.5 \text{ kW}) \cdot 100\% \approx 66.7\%$$

The voltage drop between the supply and the load is
 $150 \text{ V}_{\text{RMS}} - 100 \text{ V}_{\text{RMS}} = 50 \text{ V}_{\text{RMS}}$
 (A third of the supply's voltage!)

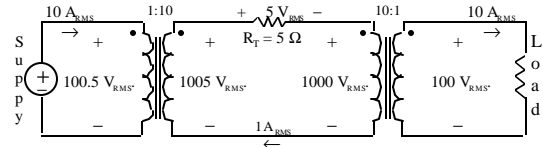4.4 Power Transformer Application: Electric Power Transmission Application cont.

Case 2: Load supplied from source via a transmission line and transformers



$$P_{\text{loss}} = (1 \text{ A}_{\text{RMS}})^2 \cdot 5 \Omega = 5 \text{ W. (Only 0.5% of the load's power!)}$$

$$P_{\text{load}} = 100 \text{ V}_{\text{RMS}} \cdot 10 \text{ A}_{\text{RMS}} = 1 \text{ kW and } P_{\text{supply}} = 100.5 \text{ V}_{\text{RMS}} \cdot 10 \text{ A}_{\text{RMS}} = 1.005 \text{ kW.}$$


$$\therefore \eta_{\%} = (1 \text{ kW} / 1.005 \text{ kW}) \cdot 100\% \approx 99.5\%$$

The effective voltage drop between the supply and the load is
 $100.5 \text{ V}_{\text{RMS}} - 100 \text{ V}_{\text{RMS}} = 0.5 \text{ V}_{\text{RMS}}$
 (Only about 0.5% of the supply's voltage!)

4.5 Circuit Differential Equations

With the addition of energy storage elements, the formerly algebraic circuit equations become differential equations. For example, consider text Problem 4.33 (p. 143) whose schematic is shown below—where the objective is to get the differential equation relating i_{out} to i_s .


Example 4-3 (Text Problem 4.33)

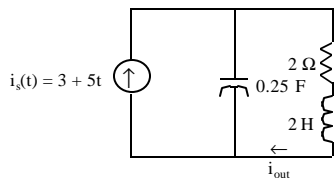

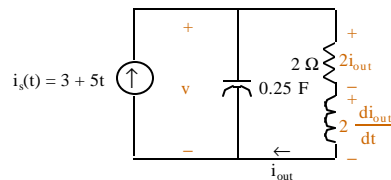4.5 Circuit Differential Equations cont.

After writing the voltage-current relationships on the schematic as shown below, KVL yields ...


$$v = 2(di_{\text{out}}/dt) + 2i_{\text{out}}$$



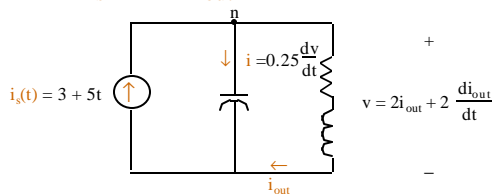4.5 Circuit Differential Equations cont.

After writing the voltage-current relationship for the capacitor on the schematic as shown below, KCL at node n yields ...


$$i_s(t) - i - i_{\text{out}} = 0 \text{ A. or ...}$$



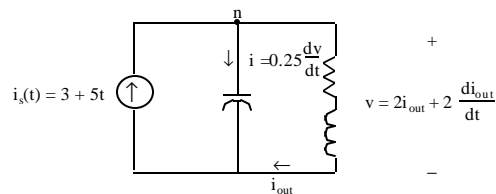4.5 Circuit Differential Equations cont.

$$i_s(t) - i - i_{\text{out}} = 0 \text{ A. or ...}$$

$$(3+5t) - 0.25 \frac{dv}{dt} - i_{\text{out}} = 0 \text{ A.}$$



4.5 Circuit Differential Equations cont.

$$(3+5t) - 0.25 \frac{dv}{dt} - i_{out} = 0 \text{ A.}$$

$$(3+5t) - 0.25 \frac{d}{dt} [2i_{out} + 2 \frac{di_{out}}{dt}] - i_{out} = 0 \text{ A.}$$

$$\frac{d^2 i_{out}}{dt^2} + \frac{di_{out}}{dt} + 2i_{out} = 6 + 10t$$

$i_s(t) = 3 + 5t$

$v = 2i_{out} + 2 \frac{di_{out}}{dt}$

Ohio University's Russ College of Engineering & Technology 55

4.5 Circuit Differential Equations cont.

Example 4-4

Determine the differential equation relating $v(t)$ to $v_s(t)$.

The equivalent circuit is

Ohio University's Russ College of Engineering & Technology 56

4.5 Circuit Differential Equations cont.

Example 4-4 cont.

KVL (left mesh): $v_s - 2 (di_1/dt) + di_2/dt = 0$ (A.)

KVL (right mesh): $di_1/dt - 3 di_2/dt - v = 0$ (B.)

Ohm's Law: $v = 0.5 \Omega \times i_2$ (C.)

Differentiate (C.) to obtain: $di_2/dt = 2 dv/dt$ (D.)

Substituting (D.) into (B.) yields: $di_1/dt = 6 dv/dt + v$ (E.)

Substituting (D.) & (E.) into (A.) yields:

$$dv/dt + 0.2 v = 0.1 v_s$$

Ohio University's Russ College of Engineering & Technology 57

4.6 Energy Storage Elements Under DC Steady-State Conditions

Bottom Line

Under DC steady-state conditions, *inductors are short circuits and capacitors are open circuits*

Ohio University's Russ College of Engineering & Technology 58

4.6 Energy Storage Elements Under DC Steady-State Conditions

Bottom Line

Under DC steady-state conditions, *inductors are short circuits and capacitors are open circuits*

Ohio University's Russ College of Engineering & Technology 59

4.6 Energy Storage Elements Under DC Steady-State Conditions cont.


Example 4-5 (Text Problem 4.37, p. 144)

Find v_{out} under DC steady-state conditions

Ohio University's Russ College of Engineering & Technology 60

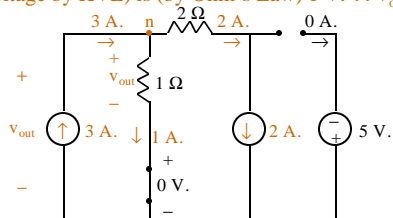4.6 Energy Storage Elements Under DC Steady-State Conditions cont.


With the capacitor opened and the inductor shorted, the current flowing down through the $1\ \Omega$ resistor is $1\ \text{A}$. (by KCL at node n) so v_{out} (which is the resistor's voltage by KVL) is (by Ohm's Law) $1\ \text{V}$. $\therefore v_{\text{out}} = 1\ \text{V}$.



Ohio University's Russ College of Engineering & Technology 61

Examination

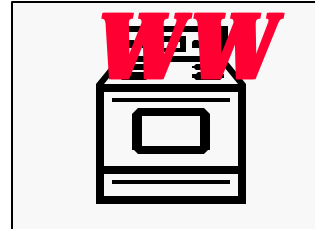Identify the EE tune (*theme song*) schema below



Ohio University's Russ College of Engineering & Technology 62

**H
O
M
E
K
R
O
W
N**



**E
x
a
m
P
a
y
o
f
f**

105 Problems \therefore \approx 11 per week

Teamwork!

Ohio University's Russ College of Engineering & Technology 63

Acknowledgement: Cartoons courtesy of



Ohio University's Russ College of Engineering & Technology 64

**We welcome your
questions with
Enthusiasm!!**



Ohio University's Russ College of Engineering & Technology 65