

EE 313: Basic EE
Chapter 5 Synopsis
© Copyright 1999 Brian Manhire



Ohio University's Russ College of Engineering & Technology 1

Chapter 5 Synopsis AC Circuits

- 5.1 Sinusoidal (AC) Sources
- 5.2 Response of Circuits to AC Sources
- 5.3 Complex Numbers and Complex Algebra
- 5.4 Use of the Complex Exponential Source
- 5.5 The Phasor Circuit
- 5.6 Average Power, Reactive Power and Power Factor
- 5.7 Frequency Response of Circuits

Ohio University's Russ College of Engineering & Technology

Chapter 5 Synopsis AC Circuits

Motivation


AC is the backbone of the electric power industry—also, about 80% of EE 315 (energy conversion) employs AC circuit analysis

Frequency response of electric circuits (to AC signals) is the conceptual “key” to understanding filters (tuners, graphic equalizers, etc.) found in consumer electronics, etc.

Ohio University's Russ College of Engineering & Technology

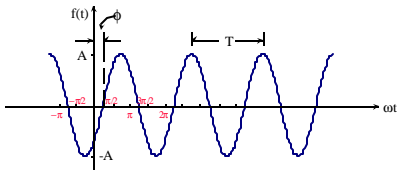
5.1 Sinusoidal (AC) Sources

Generic Sinusoid: $f(t) = A\sin(\omega t + \phi)$
 where A = Amplitude, ω = Radian Frequency (Rad./Sec.),
 f = Frequency (Hz., formerly cps) where $\omega = 2\pi f$,
 $T = 1/f$ = Period (in Sec., mSec., etc.) and
 ϕ = Phase angle (in Rad. or Degrees) where $f(t)$ is said to
 “Lag” (time delay) its $\phi = 0$ counterpart if $\phi < 0$
 and “lead” (time advance) if $\phi > 0$



Ohio University's Russ College of Engineering & Technology 4

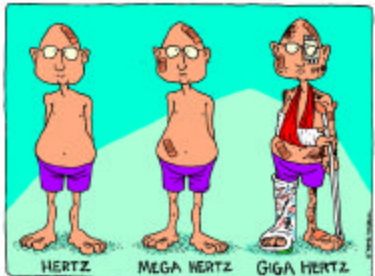
Remember: ω = radian frequency is in rad./sec. whereas f = frequency is in Hz.



Ohio University's Russ College of Engineering & Technology 5

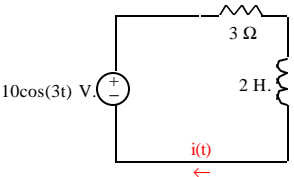5.2 Steady-State Response of Circuits to AC Sources

Below is a simple example of an AC circuit analysis problem.
 Note that the circuit is driven by an (ideal) AC voltage source
 The presumed objective is to find the steady-state current $i(t)$
 N.B.: Problems of this ilk are endemic to (inter alia)
 the electric power engineering field.



So how's it done?

Ohio University's Russ College of Engineering & Technology 6


5.2 Traditional Differential Equations Approach
KVL for the RL circuit below yields the differential equation:

$$2(di(t)/dt) + 3i(t) = 10\cos(3t)$$

The *mathematical* objective is to find a *particular solution* of the equation (i.e., *any* solution that will satisfy the equation)

The standard approach is to choose
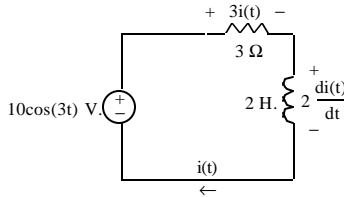
$$i(t) = I_C \cos 3t + I_S \sin 3t \text{ (an educated guess, but why?)}$$



5.2 Traditional Differential Equations Approach

Substituting $i(t) = I_C \cos 3t + I_S \sin 3t$ into the differential equation $2(di(t)/dt) + 3i(t) = 10\cos(3t)$ yields:

$$2(-3I_C \sin 3t + 3I_S \cos 3t) + 3(I_C \cos 3t + I_S \sin 3t) = 10\cos(3t) \text{ or } \dots$$

$$(3I_C + 6I_S) \cos 3t + (-6I_C + 3I_S) \sin 3t = 10 \cos 3t + 0 \sin 3t$$

Equating coefficients yields:

$$3I_C + 6I_S = 10 \text{ and } -6I_C + 3I_S = 0$$

Which have solution $I_C \approx 0.667$ and $I_S \approx 1.33$

So a particular solution is $i(t) \approx 0.667 \cos 3t + 1.33 \sin 3t$

However, $A \cos(\omega t) + B \sin(\omega t) =$

$$(A^2 + B^2)^{1/2} \cos(\omega t - \tan^{-1}(B/A))$$

$$\therefore i(t) \approx 1.491 \cos(3t - 63.43^\circ)$$

There's got to be a better way!




And there is, thanks to Charles Proteus Steinmetz (1865-1923)

5.2 Traditional Differential Equations Approach

However, before proceeding, note that the circuit's current response to the sinusoidal voltage source is $i(t) \approx 1.49 \cos(3t - 63.43^\circ)$ A.

How do the voltage source and current response differ mathematically?

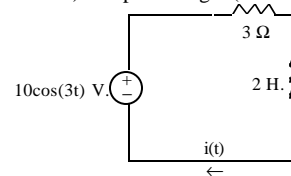They differ by only *two numbers*—magnitude (10 V. versus 1.49 A.) and phase angle (0° versus -63.43°)!



5.3 Complex Numbers and Complex Arithmetic


The *phasor method* (invented in 1893 by Charles Proteus Steinmetz, 1865-1923) is the backbone of AC steady-state circuit analysis

The principle benefit of the phasor method is that its concepts essentially render AC steady-state circuit analysis analogous to DC steady-state analysis—by way of complex arithmetic—so that the *entire differential-equations process is circumvented!*

However, in order to gainfully employ the phasor method, the electric circuit analyst must be proficient in working with complex numbers, complex arithmetic and complex algebra

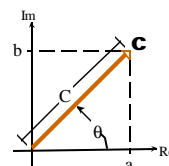5.3 Complex Numbers and Complex Arithmetic cont.

A complex number manifests itself in two forms—and consists of two numbers (per form) and presents itself as a vector in the complex plane as shown below



$$\mathbf{C} = a + jb \quad (\text{Rectangular form})$$

$$\mathbf{C} = C e^{j\theta} = C \underline{\theta} \quad (\text{Polar form})$$

where

$$j = (-1)^{1/2}, \quad a = \text{Re}(\mathbf{C}) = C \cos \theta, \quad b = \text{Im}(\mathbf{C}) = C \sin \theta$$

$$C = (a^2 + b^2)^{1/2} \text{ and } \theta = \tan^{-1}(b/a)$$

5.3 Complex Numbers and Complex Arithmetic cont.

Addition and subtraction of complex numbers is defined in rectangular form *only* as follows:

$$\begin{aligned} \text{If } \mathbf{A} &= a + jb \text{ and } \mathbf{B} = c + jd && \text{then} \\ \mathbf{A} + \mathbf{B} &= (a + c) + j(b + d) && \text{and} \\ \mathbf{A} - \mathbf{B} &= (a - c) + j(b - d) \end{aligned}$$

Multiplication and division is defined in polar form as follows:

$$\begin{aligned} \text{If } \mathbf{A} &= A/\theta_A \text{ and } \mathbf{B} = B/\theta_B && \text{then} \\ \mathbf{AB} &= AB/\theta_A + \theta_B && \text{and} \\ \mathbf{A/B} &= A/B/\theta_A - \theta_B \end{aligned}$$

and in rectangular form as follows ...

5.3 Complex Numbers and Complex Arithmetic cont.

Multiplication and division in rectangular form:

$$\begin{aligned} \text{If } \mathbf{A} &= a + jb \text{ and } \mathbf{B} = c + jd && \text{then} \\ \mathbf{AB} &= (a + jb)(c + jd) \\ &= (ac - bd) + j(ad + bc) && \text{and} \\ \mathbf{A/B} &= (a + jb)/(c + jd) \\ &= [(ac + bd) + j(bc - ad)]/(c^2 + d^2) \end{aligned}$$

Also, the *conjugate* of a phasor $\mathbf{A} = a + jb = C/\theta$ is $\mathbf{A}^* = a - jb = C/-\theta$ so that $\mathbf{AA}^* = (a + jb)(a - jb) = a^2 + b^2 = C^2$ also ...

$$\begin{aligned} 1 &= +1 + j0 = 1/\underline{0} ; -1 = -1 + j0 = 1/\underline{\pm 180^\circ} \\ \text{and } j &= 0 + j1 = 1/\underline{90^\circ} \end{aligned}$$

5.3 Complex Numbers and Complex Arithmetic cont.

Given: $\mathbf{A} = 1 - j3$ and $\mathbf{B} = 2/\underline{-30^\circ}$, the following complex arithmetic yields the following numerical results (see text Problem 5.7, p. 202):

$$\begin{aligned} \mathbf{A} + \mathbf{B} &= (1 - j3) + 2/\underline{-30^\circ} \approx (1 - j3) + (1.732 - j1) \\ &\approx 2.732 - j4 \approx 4.844/\underline{-55.67^\circ} \\ \mathbf{A} - \mathbf{B} &= (1 - j3) - 2/\underline{-30^\circ} \approx (1 - j3) - (1.732 - j1) \\ &\approx -0.732 - j2 \approx 2.130/\underline{-110.1^\circ} \\ \mathbf{AB} &= (1 - j3)(2/\underline{-30^\circ}) \approx (3.162/\underline{-71.57^\circ})(2/\underline{-30^\circ}) \\ &\approx 6.324/\underline{-101.57^\circ} \approx -1.268 - j6.195 \\ \mathbf{A/B} &\approx (3.162/\underline{-71.57^\circ})/(2/\underline{-30^\circ}) \approx 1.581/\underline{-41.57^\circ} \\ &\approx 1.183 - j1.049 \\ 1/\mathbf{A} &\approx 1/\underline{0^\circ}/(3.162/\underline{-71.57^\circ}) \approx 0.3163/\underline{+71.57^\circ} \\ &\approx 0.1 - j0.3 \text{ and } \mathbf{AA}^* \approx 3.162^2 \approx 10.0 \end{aligned}$$

5.4 Use of Complex Exponential Source

The complex-exponential-source technique is the *conceptual bridge* to the forthcoming phasor technique (which is ubiquitous in practice)

In AC steady-state circuit analysis, sinusoidal sources are mathematically related to complex exponential sources via Euler's Equation: $e^{jx} = \cos(x) + j\sin(x)$
(Euler's Equation provides the *mathematical bridge*)

Any particular solution for exponential source(s) is also a complex exponential, and is *much* easier to determine than its sinusoidal counterpart—in fact, it can be found using (complex) arithmetic alone!

Finally, the particular (trigonometric) solution for *any* AC circuit can be readily deduced from its complex exponential counterpart

5.4 Use of Complex Exponential Source cont.


Recapitulating, the exponential-source technique provides the *bridge* to the *phasor method*

To see this, consider the circuit analyzed earlier (using differential equations)—but now driven instead by the exponential counterpart of its original sinusoidal source, namely ...

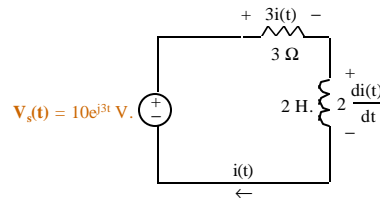5.4 Use of Complex Exponential Source cont.

The differential equation is: $2(di(t)/dt) + 3i(t) = \mathbf{V}_s(t)$

Let the particular solution *resemble* the source so that it too is a complex exponential differing from the source only in magnitude and phase angle; i.e., let $\mathbf{i}(t) = \mathbf{I}e^{j3t}$ where \mathbf{I} is an unknown *complex number*




5.4 Use of Complex Exponential Source cont.

Then $2(di(t)/dt) + 3i(t) = V_s(t)$ or ...

$$2(d(Ie^{j3t})/dt) + 3(Ie^{j3t}) = 10e^{j3t} \text{ V. or ...}$$

$$2(j3)Ie^{j3t} + 3(Ie^{j3t}) = 10e^{j3t} \text{ V. or ...}$$

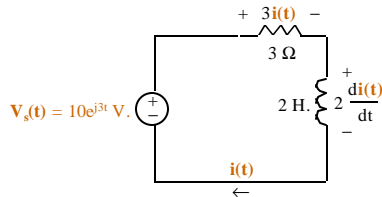$(3 + j6)Ie^{j3t} = 10e^{j3t} \text{ V.}$ and the e^{j3t} factors (time functions) cancel leaving ...




5.4 Use of Complex Exponential Source cont.

$I = 10/(3 + j6)$ —which is an equation in complex numbers *only* (no time functions at all) which yields the magnitude and phase angle unique to the current response, namely ...

$$I = 10\angle 0^\circ / (3 + j6) \approx (10\angle 0^\circ) / (6.71\angle 63.43^\circ)$$
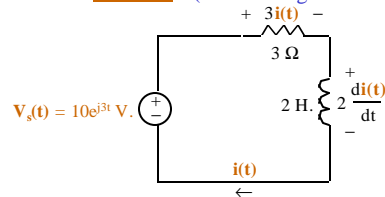
$$\approx 1.49\angle -63.43^\circ \text{ (Do these figures look familiar?)}$$



5.4 Use of Complex Exponential Source cont.

Therefore, $i(t) = Ie^{j3t} \approx 1.49\angle -63.43^\circ e^{j3t} \text{ A.}$

$$\approx 1.49e^{-j63.43^\circ} e^{j3t} \text{ A.} \approx 1.49e^{j(3t-63.43^\circ)} \text{ A.}$$

and ...

If $V_s(t) = 10\cos(3t) \text{ V.} = \text{Re}[10e^{j3t} \text{ V.}]$, what's $i(t)$?

$$i(t) \approx \text{Re}[1.49e^{j(3t-63.43^\circ)}] \approx 1.49\cos(3t - 63.43^\circ) \text{ A.}$$

Likewise

If $V_s(t) = 10\sin(3t) \text{ V.} = \text{Im}[10e^{j3t} \text{ V.}]$, what's $i(t)$?

$$i(t) \approx \text{Im}[1.49e^{j(3t-63.43^\circ)}] \approx 1.49\sin(3t - 63.43^\circ) \text{ A.}$$

The final task is to develop a method to streamline the calculations even further

This method is ...

5.5 The Phasor Circuit (Method)

Recall that, $I = 10/(3 + j6)$ which is an equation in complex numbers (no time functions at all!)


How does this compare with the calculation of

$$I = 10\angle 0^\circ / (3 + j6) \Omega \approx (10\angle 0^\circ \text{ V.}) / (6.71\angle 63.43^\circ \Omega)$$

$$\approx 1.49\angle -63.43^\circ \text{ A. for the conceptual circuit below;}$$

i.e., do these current results look familiar?

N.B.: Where's the differential equation?

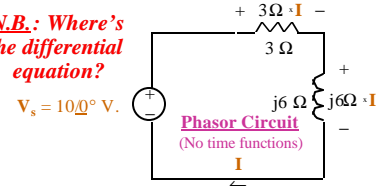


5.5 The Phasor Circuit cont.

The phasor circuit can be redrawn as shown below

Note that the phasor circuit provides a (*conceptual schematic tool*) for finding the magnitude and phase angle of the current (which are its only unique properties!)

Of the complex numbers V_s , Z and I , which do not correspond to time functions?

N.B.: Where's the differential equation?

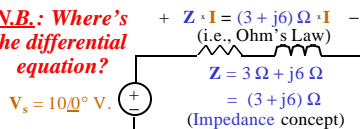

$$\text{By KVL, } I = V_s / Z = (10\angle 0^\circ \text{ V.}) / (3 + j6)\Omega \approx 1.49\angle -63.43^\circ \text{ A.}$$

5.5 The Phasor Circuit cont.


Only currents and voltages are phasors (i.e., have time-function counterparts)

Don't believe it? Then what's $Z(t)$ for the phasor circuit below if the phasors correspond to cosinusoids (so that $V_s(t) = 10\cos(3t) \text{ V.}$ and $i(t) \approx 1.49\cos(3t - 63.43^\circ) \text{ A.}$)?

$$\text{Since } Z = (3 + j6)\Omega \approx 6.71\angle 63.43^\circ \Omega,$$

$$\text{is } Z(t) \approx 6.71\cos(3t - 63.43^\circ) \Omega \text{ for example?!?}$$

N.B.: Where's the differential equation?

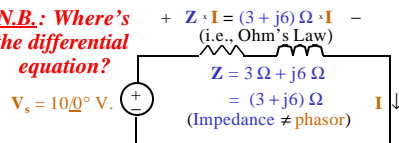

$$\text{By KVL, } I = V_s / Z = (10\angle 0^\circ \text{ V.}) / (3 + j6)\Omega \approx 1.49\angle -63.43^\circ \text{ A.}$$

5.5 The Phasor Circuit cont.

The "Rules and Regulations" for phasor sources and impedances are developed in text section 5.5 and are summarized below

$Z_C = 1/j\omega C = -j(1/\omega C)$ $V = (1/j\omega C)I = -j(1/\omega C)I$	
$Z_R = R$ $V = RI$	$Z_L = j\omega L$ $V = j\omega LI$
$V_s = V \angle \theta$ Can represent $V\sin(\omega t + \theta)$ or $V\cos(\omega t + \theta)$ —but <i>not</i> both at once!	$I_s = I \angle \theta$ Can represent $I\sin(\omega t + \theta)$ or $I\cos(\omega t + \theta)$ —but <i>not</i> both at once!

5.5 The Phasor Circuit cont.

The following equations from text p.171 are useful in reconciling situations where both sinusoidal and cosinusoidal sources are present

$$\sin(\omega t + \theta) = \cos(\omega t + \theta - 90^\circ)$$

$$\cos(\omega t + \theta) = \sin(\omega t + \theta + 90^\circ)$$

(see example below)

If $V\cos(\omega t + \theta)$'s phasor representation is $\Rightarrow V \angle \theta$

Then $E\sin(\omega t + \phi)$'s phasor representation is $\Rightarrow E \angle \phi - 90^\circ$

5.5 The Phasor Circuit cont.—Example 5-1

Find the AC steady-state current $i(t)$ —see text problem 5.26 (p.204)

Let the phasors represent cosinusoids so that the current source's phasor current is $3 \angle 30^\circ$ A.

Then the voltage source's phasor voltage is $10 \angle -90^\circ$ V.

The capacitor's impedance is $-j\{1/[(3 \text{ Rad./sec.})(1/9 \text{ F})]\} = -j3 \Omega$

So the phasor circuit becomes ...

5.5 The Phasor Circuit cont.—Example 5-1 cont.

KCL at node n:

$$(10 \angle -90^\circ \text{ V} - V_n) / 3 \Omega - V_n / (-j3 \Omega) + 3 \angle 30^\circ \text{ A} = 0 \text{ A.}$$

Which has solution $V_n \approx 6.745 \angle -80.21^\circ$ V.

Then $I = V_n / (-j3 \Omega) \approx 2.25 \angle 9.79^\circ$ A.

$\therefore i(t) \approx 2.25 \cos(3t + 9.79^\circ)$ A.

Voila!

5.6 Average Power, Reactive Power and Power Factor

What's the nature of power in AC steady-state circuits? Consider the following RL circuit ...

What's the circuit's *instantaneous* power $P(t)$?

5.6 Average Power, Reactive Power and Power Factor cont.

Applying KVL to the phasor circuit below yields the current's phasor from which $i(t)$ is deduced

Then the *instantaneous* power is $P(t) = v(t)i(t)$

$$I = \frac{V_p \angle 0^\circ}{R + j\omega L} = \frac{V_p \angle 0^\circ}{Z \angle \theta} = \frac{V_p}{Z} \angle -\theta = I_p \angle -\theta \therefore i(t) = I_p \cos(\omega t - \theta) \text{ A.}$$

Where $Z = [R^2 + (\omega L)^2]^{1/2}$ and $\theta = \tan^{-1}(\omega L/R)$

5.6 Average Power, Reactive Power and Power Factor cont.

$$P(t) = v(t)i(t) = V_p \cos(\omega t) I_p \cos(\omega t - \theta)$$

$$= 0.5 V_p I_p \cos(\theta) \{1 + \cos(2\omega t)\} + 0.5 V_p I_p \sin(\theta) \{-\sin(2\omega t)\}$$

Recall from text p. 39 that $X_{RMS} = X_{PEAK} / \sqrt{2} \therefore$ since $2 = \sqrt{2}\sqrt{2}$,

$$P(t) = V_{RMS} I_{RMS} \cos(\theta) \{1 + \cos(2\omega t)\} + V_{RMS} I_{RMS} \sin(\theta) \{-\sin(2\omega t)\}$$

$$\therefore P(t) = P_f(t) + Q_f(t), \text{ where } \dots$$

$$P = V_{RMS} I_{RMS} \cos(\theta) \text{ \& } Q = V_{RMS} I_{RMS} \sin(\theta)$$


are *constants* and

$$f_p(t) = \{1 + \cos(2\omega t)\} \text{ and } f_Q(t) = -\sin(2\omega t)$$

are *time functions*

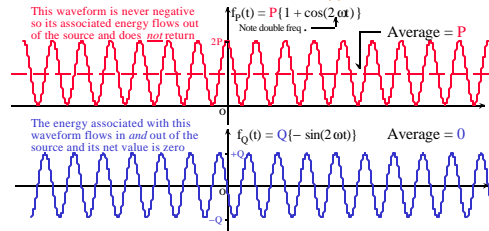5.6 Average Power, Reactive Power and Power Factor cont.

What's the physical meaning of the plots shown below of each of the two terms in P(t)'s sum?



N.B.: The average of $P(t) = P_f(t) + Q_f(t)$ is $P \therefore P$ is *average power*


Q: Remember what P is?



A: It's why Mr. DVM is upset!

N.B.: Given the CB hasn't tripped, estimate the maximum power (in hp) Mr. DVM is absorbing.

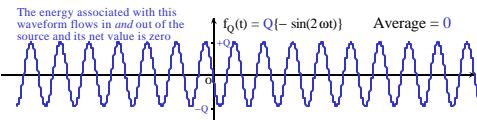
Q is "sloshing back & forth" power which occurs as a consequence of LC energy storage charging & discharging in the AC environment



P is the *business end* of AC power, whereas, although Q is a part of the AC power *package*, it's not particularly useful power (in fact, it can be a problem, e.g.; see power factor correction)

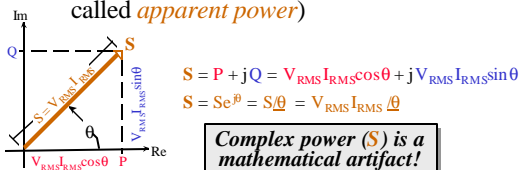5.6 Average Power, Reactive Power and Power Factor cont.

P and Q as sides of the *Power Triangle* and P and Q as the real and imaginary parts of *complex power S* (whose magnitude S is called *apparent power*)



Complex power (S) is a mathematical artifact!

N.B.: θ is called the *power factor angle* where the *power factor* is either $\cos(\theta)$ lag if $\theta > 0$, $\cos(\theta)$ lead if $\theta < 0$ or unity ($\theta = 0$)

5.6 Average Power, Reactive Power and Power Factor cont.

What's *complex power S* in terms of RMS voltage and current phasors?

What are *RMS phasors*?

An *RMS phasor* is it's traditional (peak) phasor counterpart divided by $\sqrt{2}$ (see text p. 39)

Then *complex power S* = $V_{RMS} I_{RMS}^*$


Where $V_{RMS} = V / \sqrt{2}$ and $I_{RMS} = I / \sqrt{2}$

5.6 Average Power, Reactive Power and Power Factor—**Example 5-2 cont.**

Then the source's complex power is $V_{RMS} (1.414 \angle 0^\circ \text{ A})^*$
 $\approx 15.31 \angle -51.1^\circ \text{ VA}$, $\approx 9.61 \text{ W} - j11.91 \text{ VAR}$

The complex power of the resistor, inductor and capacitor are respectively $(I_{RMS})^2 R = (1.387 \text{ A})^2 (5 \Omega) \approx 9.61 \text{ W}$,
 $j(I_{RMS})^2 X_L = j(1.387 \text{ A})^2 (6 \Omega) \approx j11.52 \text{ VAR}$ and
 $-j(V_{RMS})^2 / X_C = -j(10.83 \text{ V})^2 / 5 \Omega \approx -j23.46 \text{ VAR}$

Is complex power conserved here?

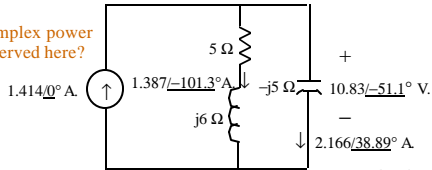

5.6 Average Power, Reactive Power and **Power Factor Correction: An Application**


$$S = P / \cos(\theta) = 12 \text{ KW} / 0.6 = 20 \text{ KVA} = V_{RMS} I_{RMS}$$

$$\therefore I_{RMS} = 20 \text{ KVA} / 120 \text{ V} \approx 167 \text{ A. (RMS)}$$

$$\text{Ergo, Line losses} = P_{RMS} R_{Line} \approx 2.78 \text{ KW}$$

$$(\approx 23\% \text{ of load power})$$

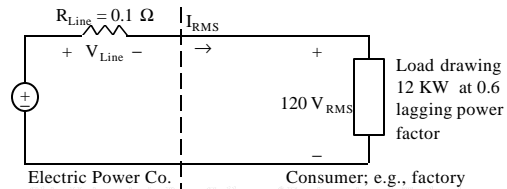
$$\text{and } V_{Line} = R_{Line} I_{RMS} \approx 16.7 \text{ V} (\approx 14\% \text{ of load voltage})$$



5.6 Average Power, Reactive Power and **Power Factor Correction: An Application cont.**

The load's complex power is $S_{Load} = P + jQ$
 $= 12 \text{ KW} + j |S_{Load}| \sin(\theta) = 12 \text{ KW} + j20 \text{ KVA} \times 0.8$
 $= 12 \text{ KW} + j16 \text{ KVAR}$

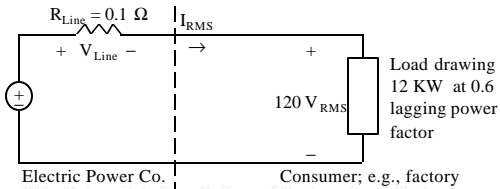Next, add $-j7 \text{ KVAR}$ of capacitance in parallel with the load to obtain ...




5.6 Average Power, Reactive Power and **Power Factor Correction: An Application cont.**

The net (load and capacitor) complex power is:

$$S_{NET} = S_{Load} - j7 \text{ KVAR} = 12 \text{ KW} + j16 \text{ KVAR} - j7 \text{ KVAR}$$

$$= 12 \text{ KW} + j9 \text{ KVAR} \approx 15 \angle 36.87^\circ \text{ KVA}$$

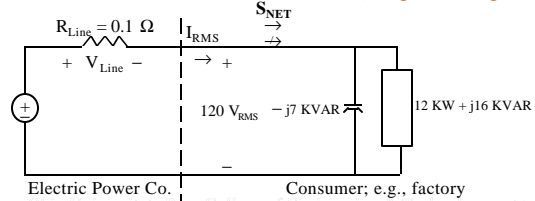N.B.: Net Power Factor = $\cos(36.87^\circ)$ Lag = 0.8 Lag




5.6 Average Power, Reactive Power and **Power Factor Correction: An Application cont.**

Then $S_{NET} = 15 \text{ KVA} = V_{RMS} I_{RMS} = (120 \text{ V}_{RMS}) I_{RMS}$ yields
 $I_{RMS} = 15 \text{ KVA} / 120 \text{ V} = 125 \text{ A. (RMS)}$ Ergo, ...

Line losses = $I_{RMS}^2 R_{Line} \approx 1.56 \text{ KW}$ ($\approx 13\%$ of load power)

and $V_{Line} = R_{Line} I_{RMS} \approx 12.5 \text{ V}$ ($\approx 10.4\%$ of load voltage)

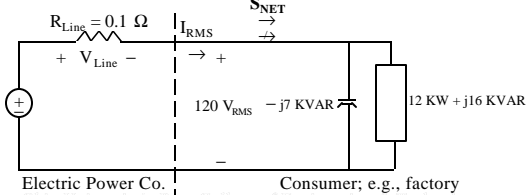
Who saves how much (annually) if electricity costs 10¢ per KWh?



5.6 Average Power, Reactive Power and **Power Factor Correction: An Application**

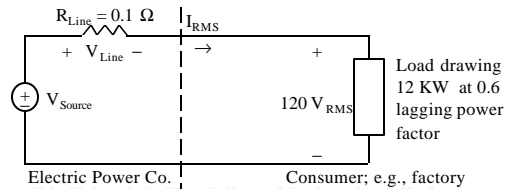Example 5-3


For the previous power factor correction application, what's the source's apparent power, power factor and voltage magnitude with and without the power factor correction?



5.6 Average Power, Reactive Power and **Power Factor Correction: An Application**

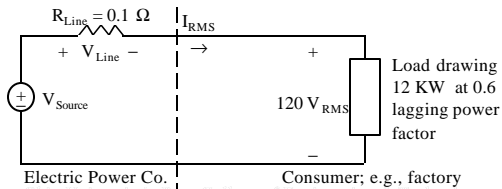Example 5-3 cont.


Without correction, the source produces $S_{Source} = S_{Load} + S_{Line} = (12 \text{ KW} + j16 \text{ KVAR}) + (2.78 \text{ KW} + j0 \text{ KVAR}) = 14.78 \text{ KW} + j16 \text{ KVAR} = 21.78 \angle 42.27^\circ \text{ KVA}$
 \therefore the apparent power is 21.78 KVA and the power factor is $\cos(42.27^\circ) \text{ Lag} = 0.74 \text{ Lag}$



5.6 Average Power, Reactive Power and **Power Factor Correction: An Application**

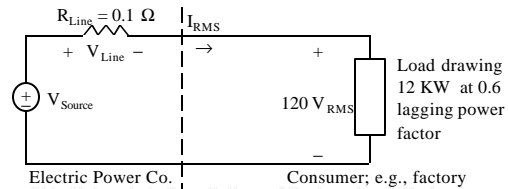Example 5-3 cont.


The current is $I_{RMS} = 167 \text{ A}$. and the apparent power ($V_{Source} \times I_{RMS}$) is 21.78 KVA
 $\therefore V_{Source} = 21.78 \text{ KVA} / 167 \text{ A} = 130 \text{ V} \text{ (RMS)}$



5.6 Average Power, Reactive Power and **Power Factor Correction: An Application**

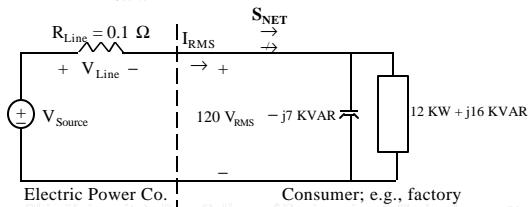Example 5-3 cont.

With correction, the source produces $S_{Source} = S_{Net} + S_{Line} = (12 \text{ KW} + j9 \text{ KVAR}) + (1.56 \text{ KW} + j0 \text{ KVAR}) = 13.56 \text{ KW} + j9 \text{ KVAR} = 16.27 \angle 33.57^\circ \text{ KVA}$
 \therefore the apparent power is 16.27 KVA, the power factor is $\cos(33.57^\circ) \text{ Lag} = 0.83 \text{ Lag}$ and $I_{RMS} = 125 \text{ A}$. so that $V_{Source} = 16.27 \text{ KVA} / 125 \text{ A} = 130 \text{ V} \text{ (RMS)}$



5.6 Average Power, Reactive Power and **Power Factor Correction: An Application**

Example 5-3 cont.

Summary

PF Correction	Apparent Power ¹	Power Factor ²	Source Voltage ³
Without	21.78 KVA	0.74 Lag	130 V.
With	16.27 KVA	0.83 Lag	130 V.

¹ Apparent power is germane to the source's size (rating) and therefore its capital cost

² The power factor indicates the percentage of the source's apparent power that is real power (83% versus 74%) and thus is a measure of the source's efficacy


³ Although this voltage is invariant across cases here, in practice, voltage regulation is usually improved by power-factor correction

5.6 Average Power, Reactive Power and Power Factor—**Maximum Power Transfer**

The steady-state AC version of the maximum power transfer theorem is similar to its DC counterpart (but the numbers are complex) and is shown below—see text pp. 183-185 for its (calculus) derivation


Note that both the (Thevenin) phasor circuit's voltage V_{Th} and impedance Z_{Th} are complex numbers

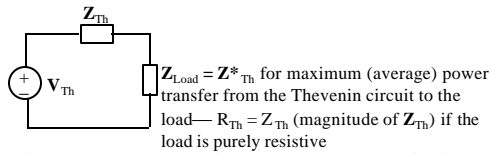The rules for obtaining the Thevenin circuit remain: $V_{Th} = V_{open \text{ circuit}}$ and Z_{Th} = circuit impedance remaining after all independent sources are deactivated




5.6 Average Power, Reactive Power and Power Factor—**Maximum Power Transfer** cont.

Example 5-4

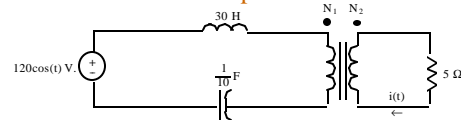


Calculate the turns ratio N_1/N_2 which will maximize the average power consumed by the resistor, the corresponding maximum average power and the resistor current $i(t)$

The phasor circuit is:

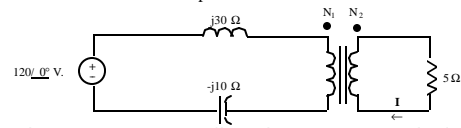


5.6 Average Power, Reactive Power and Power Factor—**Maximum Power Transfer** cont.

Example 5-4 cont.

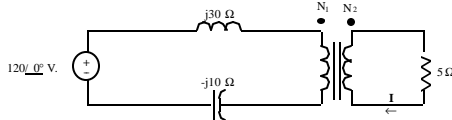


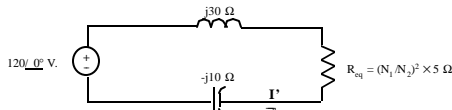Reflecting the resistor across the transformer yields:




5.6 Average Power, Reactive Power and Power Factor—**Maximum Power Transfer** cont.

Example 5-4 cont.

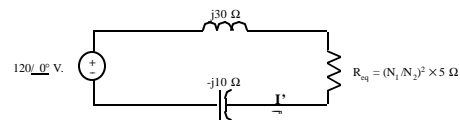


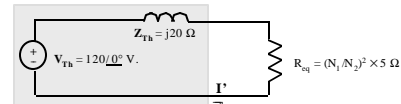Combining the two series reactances yields the (resistance-loaded) Thevenin circuit:



5.6 Average Power, Reactive Power and Power Factor—**Maximum Power Transfer** cont.

Example 5-4 cont.

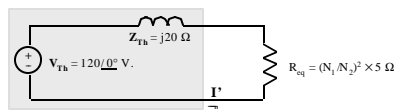


For maximum average power, $R_{eq} = (N_1/N_2)^2 \times 5 \Omega = |Z_{Th}| = 20 \Omega$

$$\therefore N_1/N_2 = 2$$

Then $I' = [V_{Th} = 120\angle 0^\circ \text{ V.}] / [Z_{Th} + R_{eq} = (20 + j20) \Omega] = 3\sqrt{2} \angle -45^\circ \text{ A.}$

5.6 Average Power, Reactive Power and Power Factor—**Maximum Power Transfer** cont.

Example 5-4 cont.

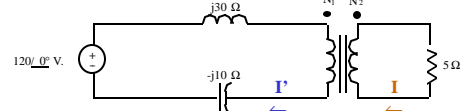

As a result of the transformer's turns ratio, $I = (N_1/N_2) I'$
 $\therefore I = (N_1/N_2) I' = 2 \times 3\sqrt{2} \angle -45^\circ \text{ A.} = (6\sqrt{2}) \angle -45^\circ \text{ A.}$ so that


$i(t) = (6\sqrt{2}) \cos(t - 45^\circ) \text{ A.} \rightarrow 8.485 \cos(t - 45^\circ) \text{ A.}$
 and $I_{RMS} = |I|/\sqrt{2} = 6 \text{ A.}$ so that $P_{ave., max.} = (I_{RMS})^2 \times 5 \Omega$ yields:


$$P_{ave., max.} = 180 \text{ W.}$$

5.7 Frequency Response of Circuits

- Time-domain signals have a frequency-domain counterpart, e.g.; music is a time varying sound signal with, inter alia, bass, mid-range and treble characteristics (components)
- The concomitant mathematical relationships were discovered in 1822 by Jean Baptiste Joseph Fourier (1768-1830)
- See text equation 5.129 (p. 185) and its accompanying Figure 5.20 (p. 186) = next slide, as well as text Appendix C (p. 753)
- Signals of all sorts (e.g., sound) can be converted to electrical signals (voltage and current waveforms) via transducers
- Electrical signals can be “processed” by electric circuits because electric circuit behavior is frequency dependent

5.7 Frequency Response of Circuits cont.

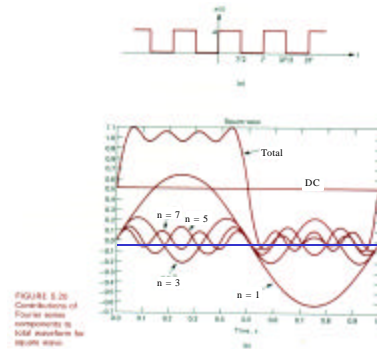

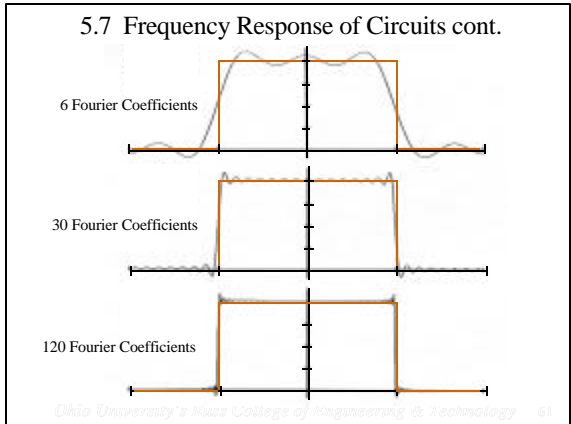

5.7 Frequency Response of Circuits cont.

- Consider the circuit of text Figure P5.39 (p. 207) whose phasor circuit is shown below
- Voltage division produces the ratio (*transfer function*) $H(j\omega) = V/V_s = (-j15/\omega)/(5 - j15/\omega) = 1/(1 + j\omega/3)$ which in this case is *gain* (i.e., what are **H**'s units?)

$V_s = V_s \angle 0^\circ V$

5Ω

$-j15/\omega \Omega$

V

Ohio University's Russ College of Engineering & Technology 62

5.7 Frequency Response of Circuits cont.


- This *transfer function* can be written in polar form as $H(j\omega) = M(\omega)/\theta(\omega)$ where:
 - $M(\omega) = \{1/[1 + (\omega/3)^2]^{1/2}\}$ and $\theta(\omega) = -\tan^{-1}(\omega/3)$
- So both the gain's magnitude and phase angle depend on frequency; i.e., $M(0) = 1$ (which is also M 's maximum) and $\theta(0) = 0^\circ$ whereas $\text{Lim}[M(\omega)]$ and $\text{Lim}[\theta(\omega)]$ as $\omega \rightarrow \infty$ are 0 and -90° respectively
- Note also that for $(\omega/3) \gg 1$, $M(\omega) \approx 3/\omega$ (which means higher gain for lower frequencies)
- What's $M(\omega)$ and $\theta(\omega)$ when $\omega = 3$ Rad./Sec.?

Ohio University's Russ College of Engineering & Technology 63

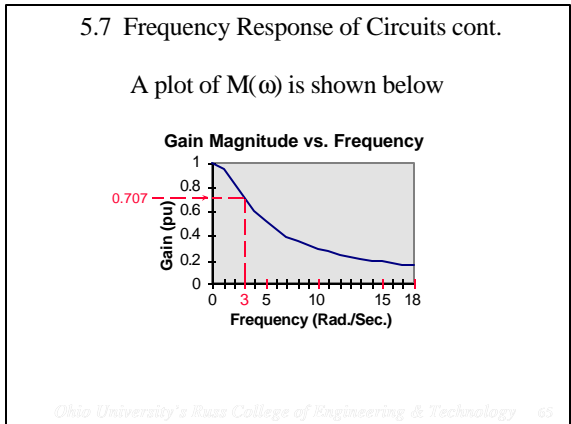5.7 Frequency Response of Circuits cont.

- $M(3) = \{1/[1 + (3/3)^2]^{1/2}\} = 1/\sqrt{2}$ and $\theta(\omega) = -45^\circ$ which is the transfer function's *half-power point*
- Why the moniker *half-power point*?
- Suppose $V_s = V_s \angle 0^\circ V$ for all frequencies (i.e., all ω)
- Then the maximum output voltage $V_{\text{max}} = V_s$ occurs at $\omega = 0$ since $V = M(\omega)V_s$ and $M_{\text{max}} = M(0) = 1$
- Impressing this voltage across a load resistor yields the maximum output power $P_{\text{max}} = V_s^2/R_L$
- The *output* voltage at $\omega = 3$ Rad./Sec. is $M(3)V_s = V_s/\sqrt{2}$ and the corresponding power is $(V_s/\sqrt{2})^2/R_L = [V_s^2/R_L]/2 = P_{\text{max}}/2$ (*half of P_{max}*)

Ohio University's Russ College of Engineering & Technology 64



Remember: ω = *radian frequency* is in rad./sec. whereas f = *frequency* is in Hz.


HERTZ MEGA HERTZ GIGA HERTZ

Ohio University's Russ College of Engineering & Technology 66

5.7 Frequency Response of Circuits cont.


A plot of $\theta(\omega)$ is shown below

Gain's Phase Angle vs. Frequency

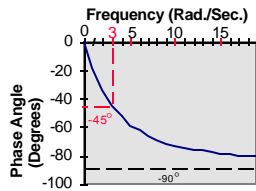

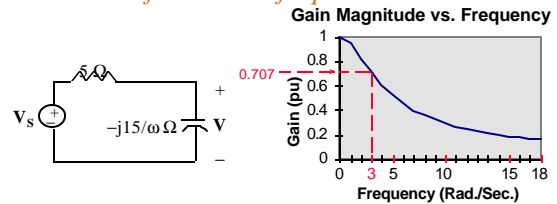5.7.2 Filters

The RC circuit just considered is a *low-pass filter* because the magnitude of its gain $M(\omega)$ favors lower frequencies




Transfer function's gain magnitude = $|H(j\omega)| = |V/V_s| = V/V_s = M(\omega)$
 N.B.: If the capacitor's voltage favors low frequencies, one can intuit that the resistor's voltage favors high frequencies (why?)

5.7.2 Filters cont.


Other types of filters are possible and are developed in text section 5.7.2 (pp. 190-200) using the generic prototype shown below

The *results* for each filter are ...

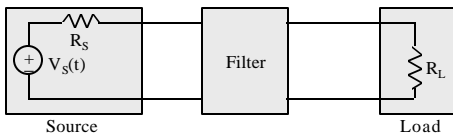

5.7.2 Filters cont.

Low-pass filter

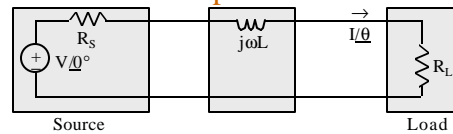

$$H(j\omega) = I_\theta / V_{0^\circ} = \{ V_{0^\circ} / (R_s + R_L + j\omega L) \} / V_{0^\circ}$$



for which

$$M(\omega) = \frac{1}{R_s + R_L} \cdot \frac{1}{(1 + [\omega L / (R_s + R_L)]^2)^{1/2}}$$

Which has a cut-off (half-power) frequency of $\omega_c = (R_s + R_L)/L$


5.7.2 Filters cont.

Low-pass filter

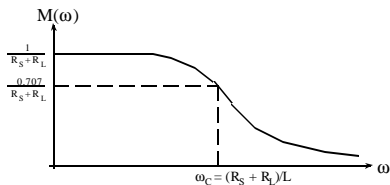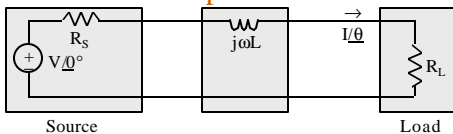

5.7.2 Filters cont.

High-pass filter

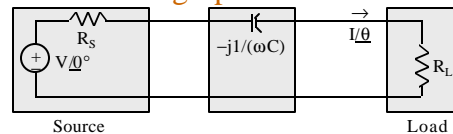

$$H(j\omega) = I_\theta / V_{0^\circ} = \{ V_{0^\circ} / [R_s + R_L - j1/(\omega C)] \} / V_{0^\circ}$$



for which

$$M(\omega) = \frac{1}{R_s + R_L} \cdot \frac{1}{\{1 + [1/(\omega C (R_s + R_L))]^2\}^{1/2}}$$

Which has a cut-off (half-power) frequency of $\omega_c = 1/[C(R_s + R_L)]$


5.7.2 Filters cont.

High-pass filter

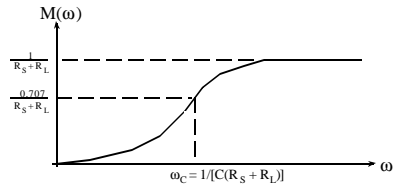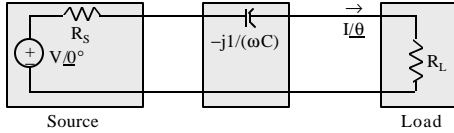

5.7.2 Filters cont.

Band-pass filter

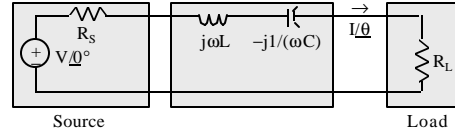


$$H(j\omega) = I(t) / V_s(t) = \{ V_s(t) / [R_s + R_L + j\omega L - j(1/\omega C)] \} / V_s(t)$$

for which

$$M(\omega) = \frac{1}{R_s + R_L} \cdot \frac{1}{\{1 + \{[1 - \omega^2 LC] / [\omega C(R_s + R_L)]\}^2\}^{1/2}}$$


5.7.2 Filters cont.

Band-pass filter

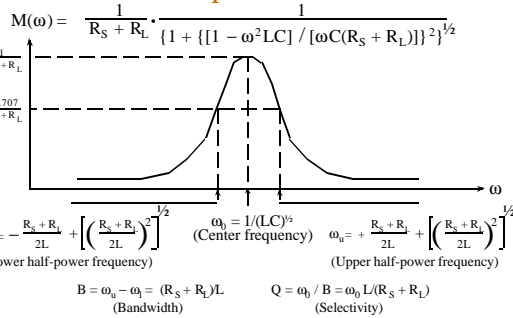

5.7.2 Filters cont.

Band-reject filter

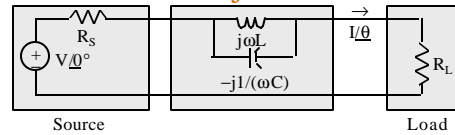


$$H(j\omega) = I(t) / V_s(t) = V_s(t) / [R_s + R_L + (j\omega L) \parallel (-j1/\omega C)]$$

for which

$$M(\omega) = \frac{1}{R_s + R_L} \cdot \frac{1}{\{1 + \{[\omega L / (R_s + R_L)] / [1 - \omega^2 LC]\}^2\}^{1/2}}$$


5.7.2 Filters cont.

Band-reject filter

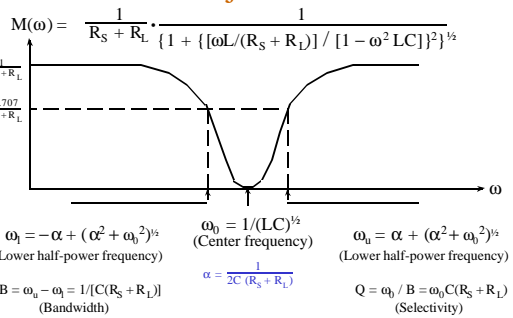

5.7.2 Filters cont.

Example 5-5

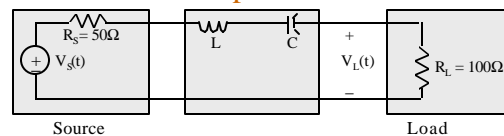

Design the band-pass filter to have a center frequency of 1 MHz. and a bandwidth of 10 kHz. What's this filter's Q?

$$\omega_0 = 2\pi f_0 = 2\pi \times 10^6 \text{ Rad./Sec.} = 1/(LC)^{1/2} = (\text{Center frequency})$$

$$B = 2\pi f_{BW} = 2\pi \times 10^4 \text{ Rad./Sec.} = (R_s + R_L)/L = 150\Omega/L \text{ (Bandwidth)}$$

$$\therefore L = 150\Omega / (2\pi \times 10^4 \text{ Rad./Sec.}) \approx 2.39 \text{ mH}$$

$$\text{and } C = 1 / (\omega_0^2 L) \approx 1 / [(2\pi \times 10^6 \text{ Rad./Sec.})^2 \times 2.39 \text{ mH}] \approx 10.6 \text{ pF}$$


$$\text{and } Q = \omega_0 / B = (2\pi \times 10^6 \text{ Rad./Sec.}) / (2\pi \times 10^4 \text{ Rad./Sec.}) = 100$$

Recommendation: Use *spreadsheet software* to solve homework problem 5.47



Examination

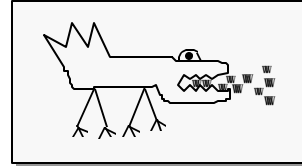Identify the EE *instrumentation* shown below



**H
O
M
E
W
O
R
K**



105 Problems \therefore \approx 11 per week

Teamwork!

**E
x
a
m
P
a
y
o
f
f**

Acknowledgement: Cartoons courtesy of

Test & Measurement
Educator's Corner

Search
Hewlett-Packard
Test & Measurement

Sharing Hewlett-Packard's Resources
With Engineering Educators
<http://www.EducatorsCorner.com>

**We welcome your
questions with
Enthusiasm!!**



OHIO UNIVERSITY

School of Electrical Engineering
& Computer Science
Stocker Center
Athens OH 45703-2879

Brian Manhire, Ph.D.
Professor of Electrical
Engineering
740-593-1179 phone
740-593-0027 fax
bmanhire1@ohio.edu